



EEE270

Introduction to Electrical Energy Systems

Chapter 7 – Voltage Drop and Power Loss Calculations

Prof. Dr. A. Mete VURAL

mvural@gantep.edu.tr


Assist. Prof. Dr. Ali Osman ARSLAN

aoarslan@gantep.edu.tr

CABLE SIZE SELECTION


The proper cable size is found for a given load by the following analysis:

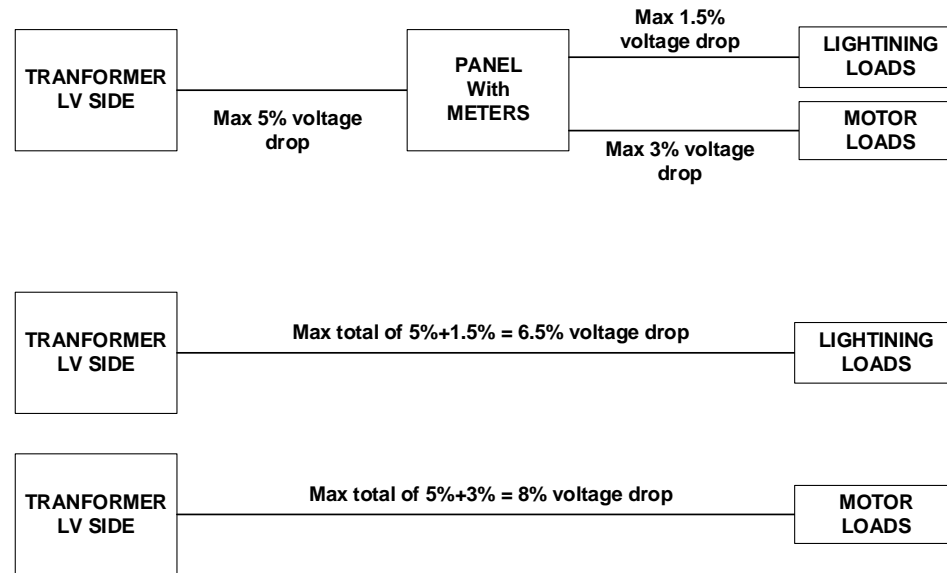- The **current rating (ampacity)** of the cable should be sufficient to carry the required amount of current safely under the installation conditions
- There appears a **voltage drop** on the conductor due to the resistance and inductive reactance. The conductor size should satisfy the **voltage drop** criteria as follows for LV systems in general



- If voltage drop criteria is not clear or not given, then the choice of cable size is done according to the magnitude of load current. This is known as "*Isı Tahkiki (thermal investigation)*" in electrical projects.

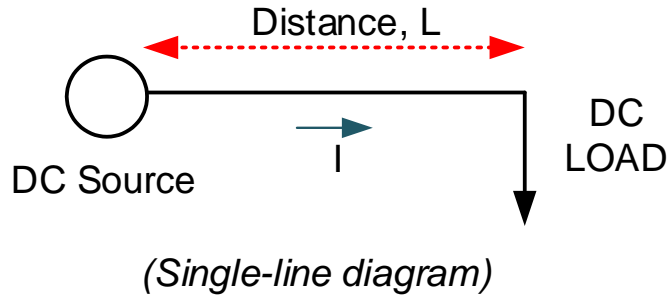
Voltage Drop Calculation in DC Distribution Systems



$$R = rL$$

$$R = \frac{L}{\sigma A}$$

$$\sigma \cdot \rho = 1$$

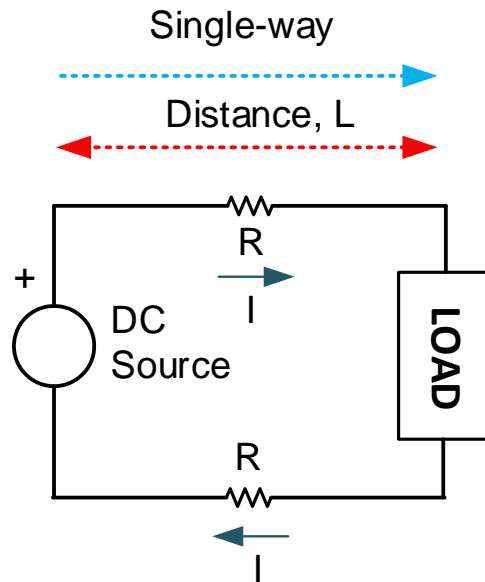

where

R is DC resistance of the overhead-line or cable (**single-way**)

r is the per meter DC resistance of the overhead-line or cable (Ω/m)


L is the distance between source and load (**m**)

σ is the conductivity of the conductor ($\text{m}/\Omega \cdot \text{mm}^2$)

(Conductivity is generally represented with letter "k" in Turkish sources)

A is the cross-sectional area of the conductor (mm^2)

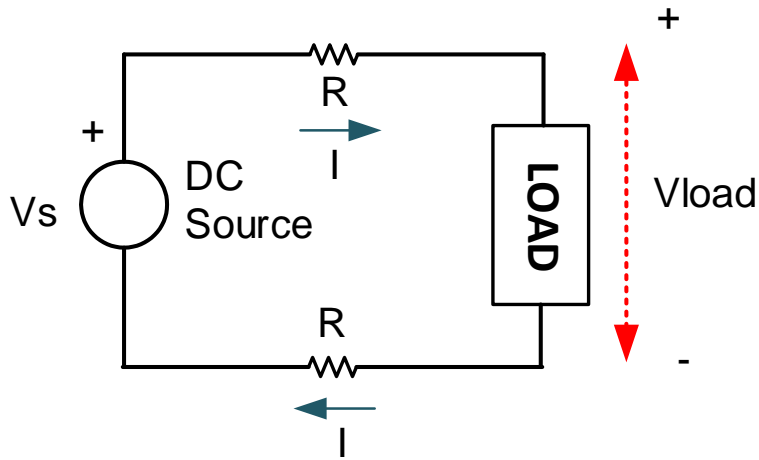ρ is the resistivity of the conductor ($\Omega \cdot \text{mm}^2/\text{m}$)



From KVL:

$$V_s - RI - V_{load} - RI = 0$$

$$V_s - 2RI - V_{load} = 0$$

$$\Delta V = V_s - V_{load}$$

$$\Delta V = 2RI \text{ (voltage drop on the line, 2-way)}$$

$$P_{in} = V_s \cdot I \text{ (input power, W)}$$

$$P_{out} = P_{load} = V_{load} \cdot I \text{ (output power, W)}$$

$$P_{loss} = 2RI^2 \text{ (power loss, W) (R is one-way resistance)}$$

$$P_{in} = P_{out} + P_{loss}$$

$$\Delta V = 2RI \text{ (voltage drop)}$$

$$\%e = \frac{\Delta V}{V_n} \times 100\% \text{ (percentage voltage drop)}$$

where

V_n is the nominal system voltage

- ✓ V_n can be equal to V_s or
- ✓ V_n can be equal to V_{load} or
- ✓ V_n can be equal to a voltage, close to V_s or V_{load}

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% \text{ (percentage efficiency)}$$

$$\%P_{loss} = \frac{2RI^2}{P_{load}} \times 100\% \text{ (percentage power loss)}$$

Let's find a useful equation for **percentage voltage drop**;

$$\%e = \frac{\Delta V}{V_n} \times 100\% \quad (\text{percentage voltage drop})$$

$$\%e = \frac{\Delta V}{V_n} \times 100\% = \frac{2RI}{V_n} \times 100\%$$

Since $I = P_{load} / V_{load}$

$$\%e = \frac{2RP_{load}}{V_n.V_{load}} \times 100\%$$

If we assume $V_n = V_{load}$

$$\%e = \frac{2RP_{load}}{V_{load}^2} \times 100\%$$


$$\%e = \frac{2RP_{load}}{V_{load}^2} \times 100\%$$

Since $\rightarrow R = \frac{L}{\sigma A}$

$$\%e = \frac{2.P_{load}.L}{V_{load}^2 .\sigma.A} \times 100\%$$

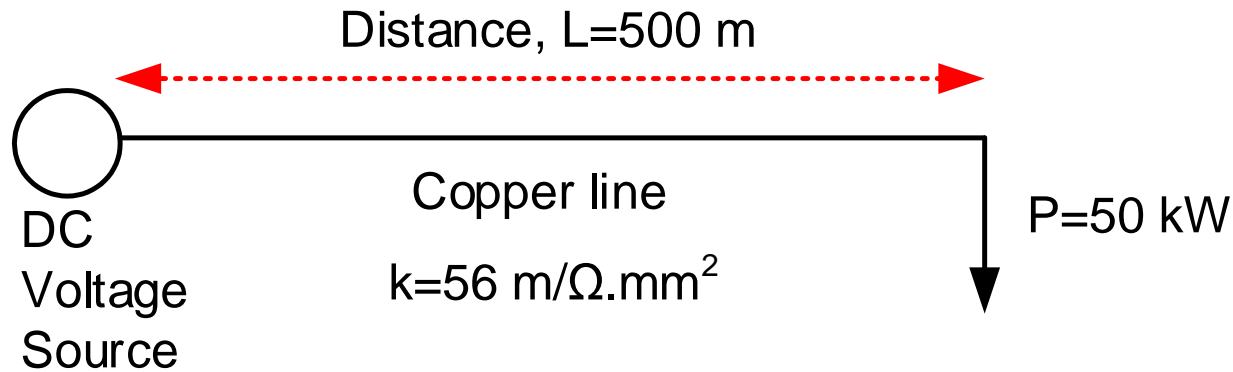Example: Single-line diagram of a DC distribution line is shown in the figure. If copper conductor is used, load power is 50 kW, and load voltage is 600 V (DC), answer the following questions:

- Find the cross-section of the copper conductor so that maximum percentage voltage drop becomes 5 % ($e \leq 5\%$)
- Find the voltage drop on the line
- Find the voltage of the DC source
- Find the power loss and the efficiency of this distribution line



İLETKENLERİN KORUNMASINDA SİGORTA SEÇİMİ

Yalıtılmış Bakır İletkenlerin Aşırı Yükleme Sınırları ve Sigortaların Seçimi
VDE 0100 Teil 523, Teil 430

Grup 1) Boru içinde üç veya dört hatta kadar

Grup 2) Nemli yer hatları seyyar alıcılara bağlanan ve açıkta döşenen yuvarlak telli çok damarlı hatlar


Grup 3) Açıkta döşenen tek damarlı hatlar, dağıtım kutuları ve panolarda kullanılan tek damarlı hatlar.

Kesit mm ²	Grup 1		Grup 2		Grup 3	
	İletken A	Sigorta A	İletken A	Sigorta A	İletken A	Sigorta A
0.75	-	-	12	6	15	10
1	11	6	15	10	19	10
1.5	15	10	18	10	24	20
2.5	20	16	26	20	32	25
4	25	20	34	25	42	35
6	33	25	44	35	54	50
10	45	35	61	50	73	63
16	61	50	82	63	98	80
25	83	63	108	80	129	100
35	103	80	135	100	158	125
50	132	100	168	125	198	160
70	165	125	207	160	245	200
95	197	160	250	200	292	250
120	235	200	292	250	344	315
150	-	-	335	250	391	315
185	-	-	382	315	448	400
240	-	-	453	400	528	400

Example: A 300 meter DC underground feeder has two sections feeding two loads, as shown in the figure.

Answer the following questions:

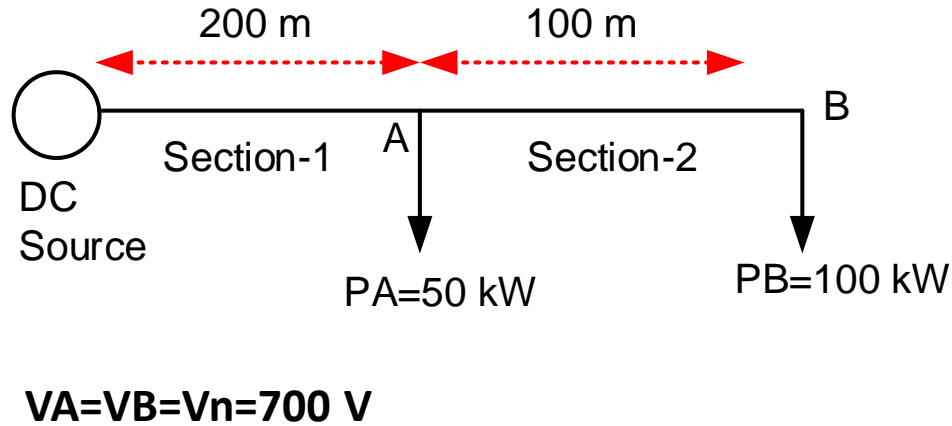- a) For a maximum of **10 %** power loss in the feeder, what should be the value of the cross-sectional area of the copper underground conductor ?
- b) Is the cross-section found in (a) suitable for this condition, $\%e \leq 5\%$? If not then choose a suitable one.



İLETKENLERİN KORUNMASINDA SİGORTA SEÇİMİ

Yalıtılmış Bakır İletkenlerin Aşırı Yükleme Sınırları ve Sigortaların Seçimi
VDE 0100 Teil 523, Teil 430



Grup 1) Boru içinde üç veya dört hatta kadar

Grup 2) Nemli yer hatları seyyar alıcılara bağlanan ve açıkta döşenen yuvarlak telli çok damarlı hatlar

Grup 3) Açıkta döşenen tek damarlı hatlar, dağıtım kutuları ve panolarda kullanılan tek damarlı hatlar.

Kesit mm ²	Grup 1		Grup 2		Grup 3	
	İletken A	Sigorta A	İletken A	Sigorta A	İletken A	Sigorta A
0.75	-	-	12	6	15	10
1	11	6	15	10	19	10
1.5	15	10	18	10	24	20
2.5	20	16	26	20	32	25
4	25	20	34	25	42	35
6	33	25	44	35	54	50
10	45	35	61	50	73	63
16	61	50	82	63	98	80
25	83	63	108	80	129	100
35	103	80	135	100	158	125
50	132	100	168	125	198	160
70	165	125	207	160	245	200
95	197	160	250	200	292	250
120	235	200	292	250	344	315
150	-	-	335	250	391	315
185	-	-	382	315	448	400
240	-	-	453	400	528	400

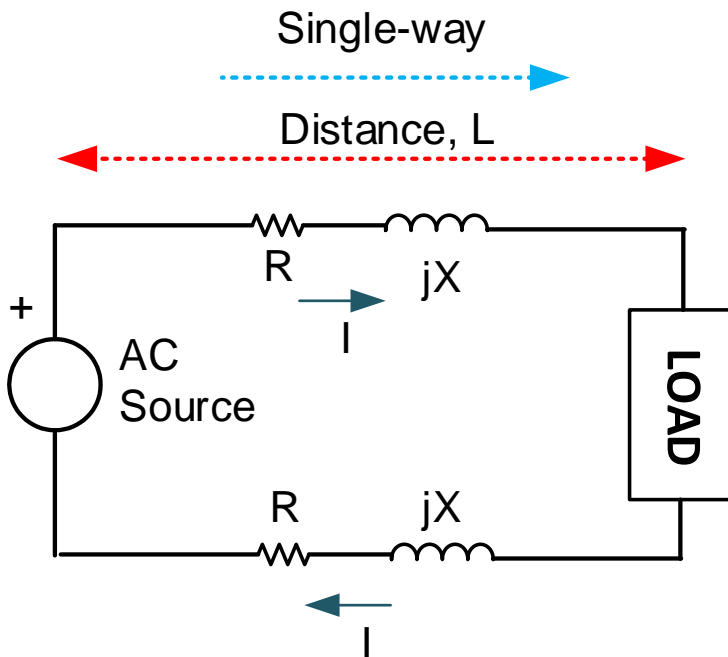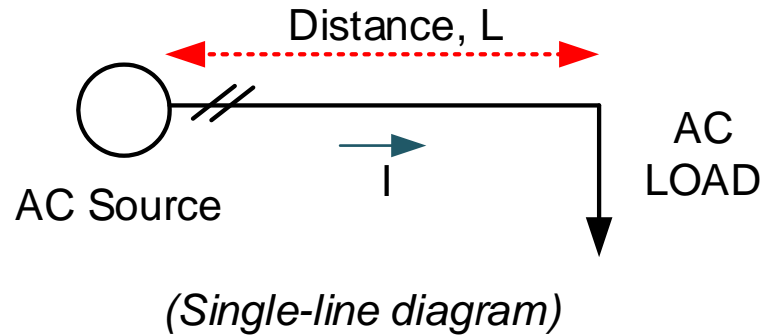Voltage Drop Calculation in Single-phase Systems



$$R = rL$$

$$X = xL$$

$$Z = R + jX$$

$$R = \frac{L}{\sigma A}$$


In distribution systems, we generally ignore the capacitive effect of the lines

$$\sigma \cdot \rho = 1$$

For **underground cables** capacitive effect may not be ignored

where

- R is AC resistance of the overhead-line or cable (**single-way**)
- X is the reactance of the overhead-line or cable (**single-way**)
- r is the per meter AC resistance of the overhead-line or cable (**Ω/m**)
- x is the per meter reactance of the overhead-line or cable (**Ω/m**)
- Z is the impedance of the overhead-line or cable (**single-way**)
- L is the distance between source and load (**m**)
- σ is the conductivity of the conductor (**$m/\Omega \cdot mm^2$**)
- A is the cross-sectional area of the conductor (**mm^2**)
- ρ is the resistivity of the conductor (**$\Omega \cdot mm^2/m$**)

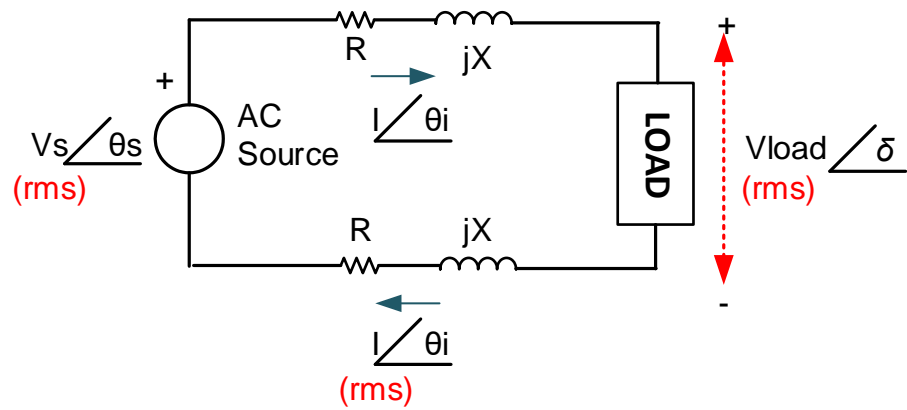

From KVL:

$$V_s / \angle \theta_s - (I / \angle \theta_i)(R + jX) - (V_{load} / \angle \delta) - (I / \angle \theta_i)(R + jX) = 0$$


$$V_s / \angle \theta_s - 2(I / \angle \theta_i)(R + jX) - (V_{load} / \angle \delta) = 0$$

$$\Delta V = V_s / \angle \theta_s - V_{load} / \angle \delta$$

$$\Delta V = 2(I / \angle \theta_i)(R + jX) \text{ (voltage drop on the line, 2-way)}$$


$$\Delta V = 2(I / \angle \theta_i)Z \text{ (voltage drop on the line, 2-way)}$$

Case2: Leading Load ($\theta_i > 0$)

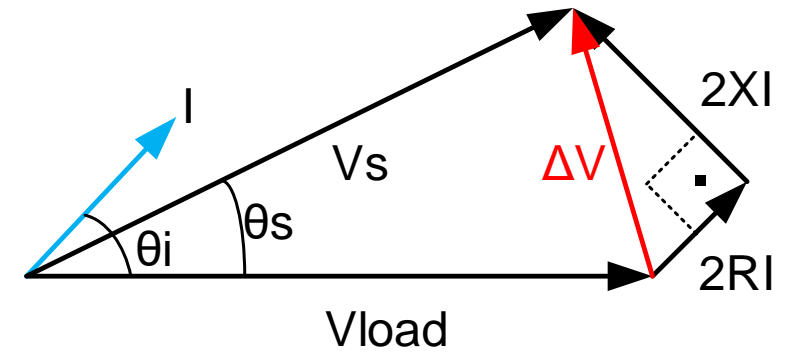


(Assuming $\delta=0$)

Case1: Lagging Load ($\theta_i < 0$)

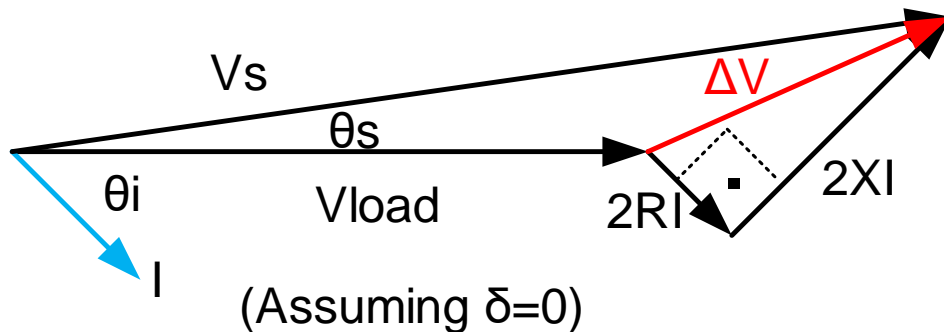

(Assuming $\delta=0$)


Case3: Unity PF Load ($\theta_i=0$)

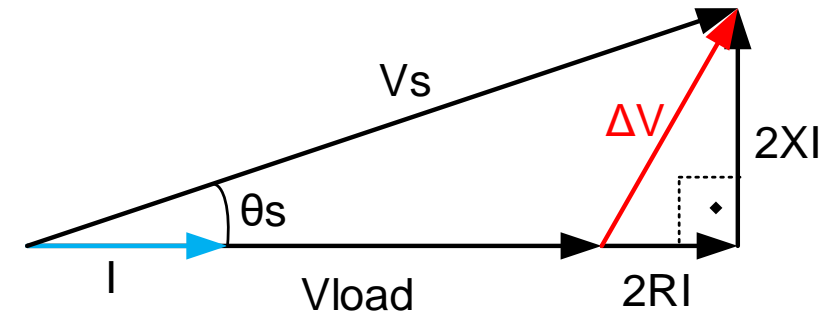


(Assuming $\delta=0$)

Approximate Voltage Drop Equations


Case1: Lagging Load ($\theta_i < 0$)

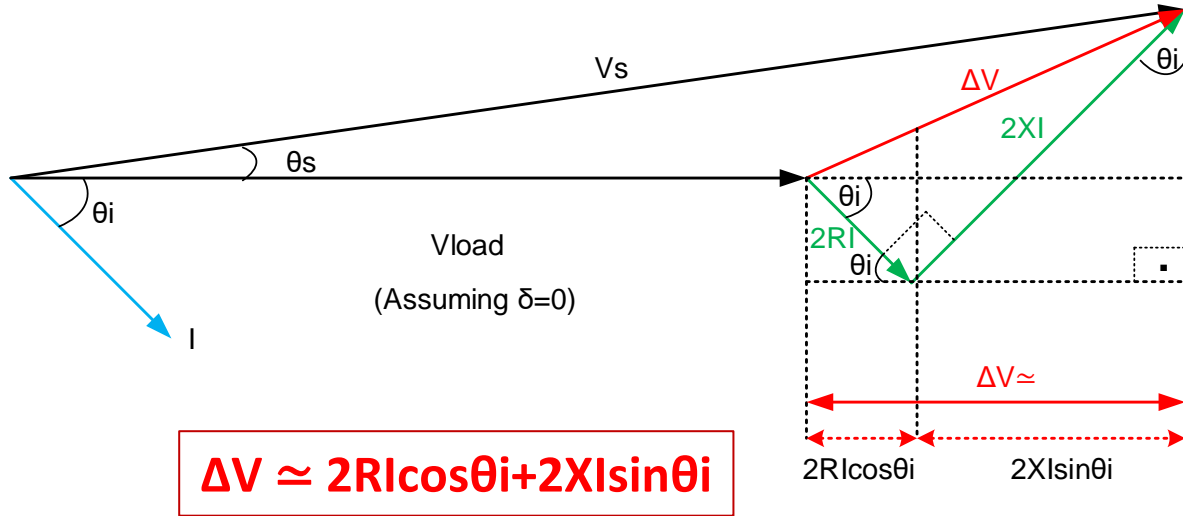

Case3: Unity PF Load ($\theta_i=0$)

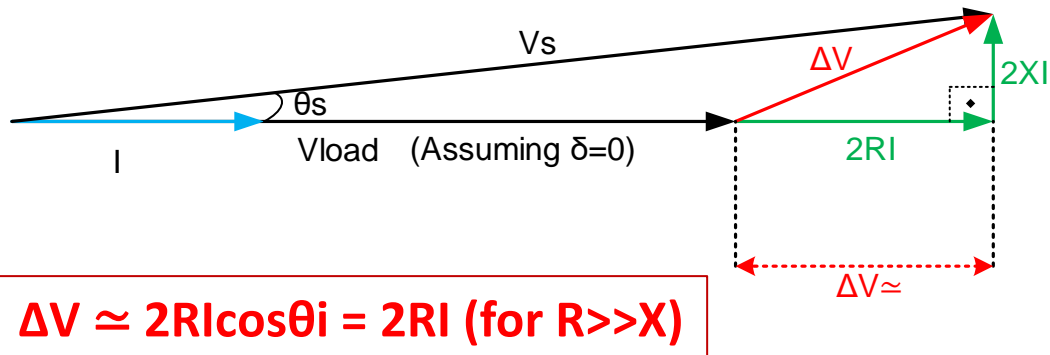

Case2: Leading Load ($\theta_i > 0$)

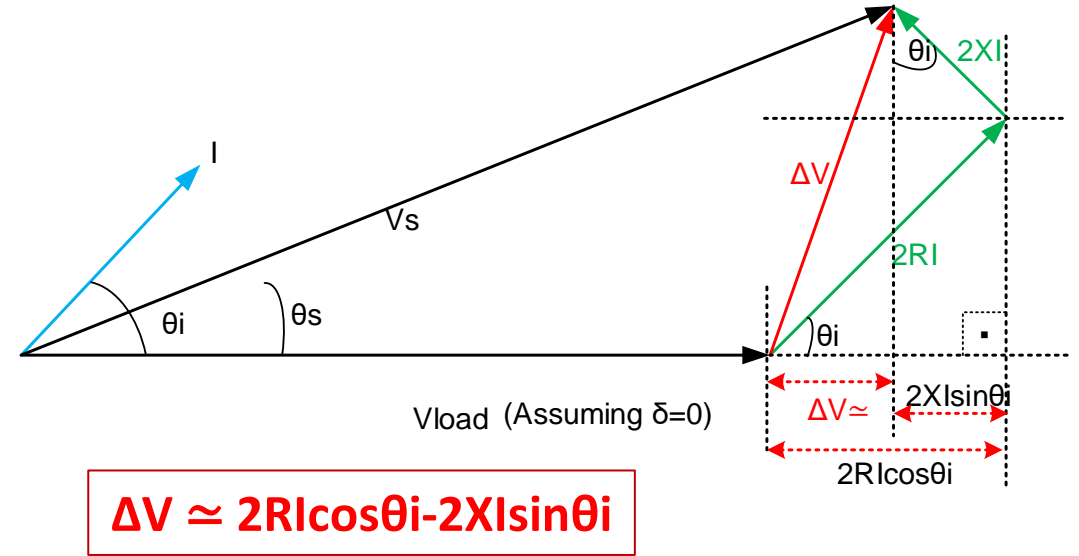

$$\%e = \frac{\Delta V}{V_n} \times 100\% \quad \text{(percentage voltage drop)}$$

where

V_n is the nominal (rated) rms system voltage

- ✓ V_n can be equal to V_s or
- ✓ V_n can be equal to V_{load} or
- ✓ V_n can be equal to a voltage, close to V_s or V_{load}

Let's find a useful equation for percentage voltage drop in **single-phase systems**;

$$\%e = \frac{\Delta V}{V_n} \times 100\% \text{ (percentage voltage drop)}$$

$$\%e = \frac{\Delta V}{V_n} \times 100\% = \frac{2RI \cos \theta_i \pm 2XI \sin \theta_i}{V_n} \times 100\%$$

Since $I = P_{load} / (V_{load} \times \cos(\delta - \theta_i))$, (assuming $\delta = 0$)

$$\%e = \frac{2(R \cos \theta_i \pm X \sin \theta_i) P_{load}}{V_n \cdot V_{load} \cdot \cos \theta_i} \times 100\%$$

If we assume $V_n = V_{load}$

$$\%e = \frac{2(R \cos \theta_i \pm X \sin \theta_i) P_{load}}{V_{load}^2 \cdot \cos \theta_i} \times 100\%$$

$$\%e = \frac{2(R \cos \theta_i \pm X \sin \theta_i) Pload}{Vload^2 \cdot \cos \theta_i} \times 100\%$$

Or

$$\%e = \frac{2.(R \pm X \tan \theta_i) Pload}{Vload^2} \times 100\%$$

Or

$$\%e = \frac{(1 \pm \frac{X}{R} \tan \theta_i).2.R.Pload}{Vload^2} \times 100\%$$

Let Inductive (lagging PF)


$$f(\varphi) = (1 \pm \frac{X}{R} \tan \theta_i)$$

Capacitive (leading PF)

$$\%e = \frac{2.R.Pload}{Vload^2} \cdot f(\varphi) \times 100\%$$

Since $\rightarrow R = \frac{L}{\sigma A}$
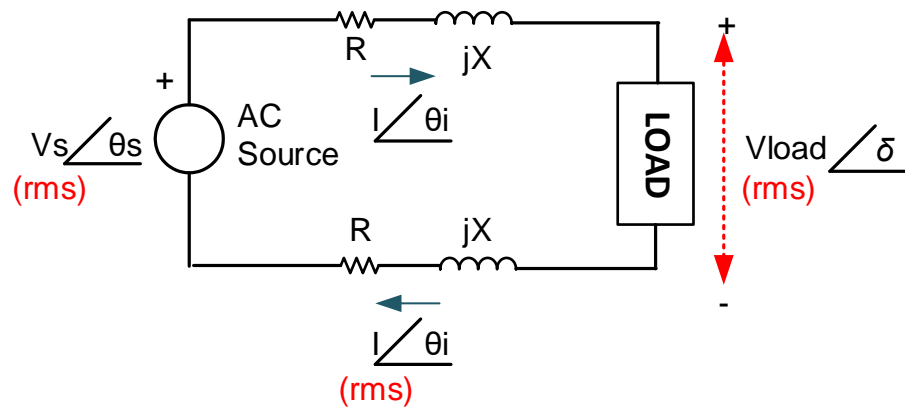
$$\%e = \frac{2.Pload.L}{Vload^2 \cdot \sigma.A} \times f(\varphi) \times 100\%$$



$$P_{in} = V_s \cdot I \cdot \cos(\theta_s - \theta_i) \quad (\text{input active power, W})$$

$$P_{out} = P_{load} = V_{load} \cdot I \cdot \cos(\delta - \theta_i) \quad (\text{output active power, W})$$

$$P_{loss} = 2RI^2 \quad (\text{active power loss, W})$$

(R is one-way resistance)

$$P_{in} = P_{out} + P_{loss}$$

$$Q_{in} = V_s \cdot I \cdot \sin(\theta_s - \theta_i) \quad (\text{input reactive power, VAR})$$

$$Q_{out} = Q_{load} = V_{load} \cdot I \cdot \sin(\delta - \theta_i) \quad (\text{output reactive power, VAR})$$

$$Q_{loss} = 2XI^2 \quad (\text{reactive power loss, VAR})$$

(X is one-way reactance)

$$Q_{in} = Q_{out} + Q_{loss}$$



$$\eta = \frac{P_{out}}{P_{in}} \times 100\% \quad (\text{percentage efficiency})$$

$$\% P_{loss} = \frac{2RI^2}{P_{load}} \times 100\%$$

(percentage (active) power loss)

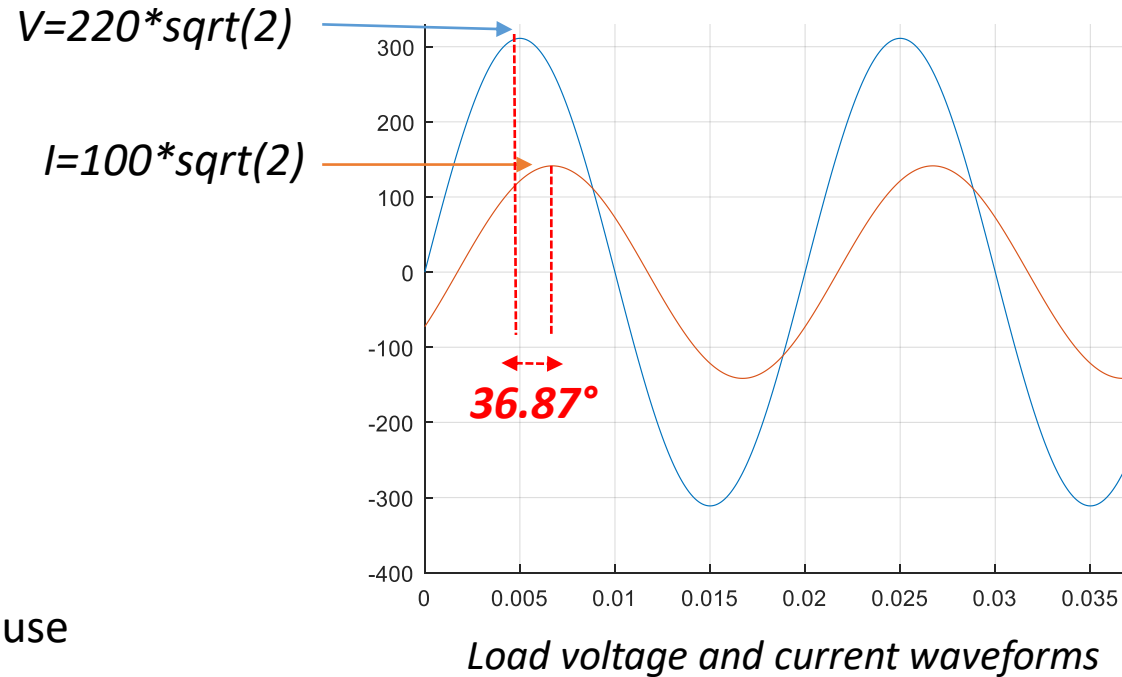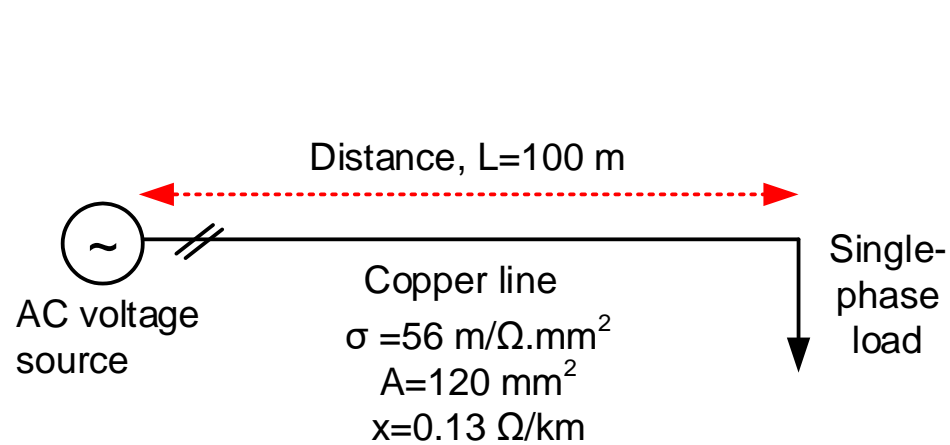Example: A 100 meter single-phase line feeds a load as shown in the figure. Answer the following questions:


- For a maximum of 3 % voltage drop on the line, is given value for $A=120 \text{ mm}^2$ suitable or not ?
- Find the voltage drop on the line.
- Find the value of the AC voltage source, active-reactive power loss, and input active power.




Important Note: Since X is not ignored, we can not use percentage voltage drop equation as the given form

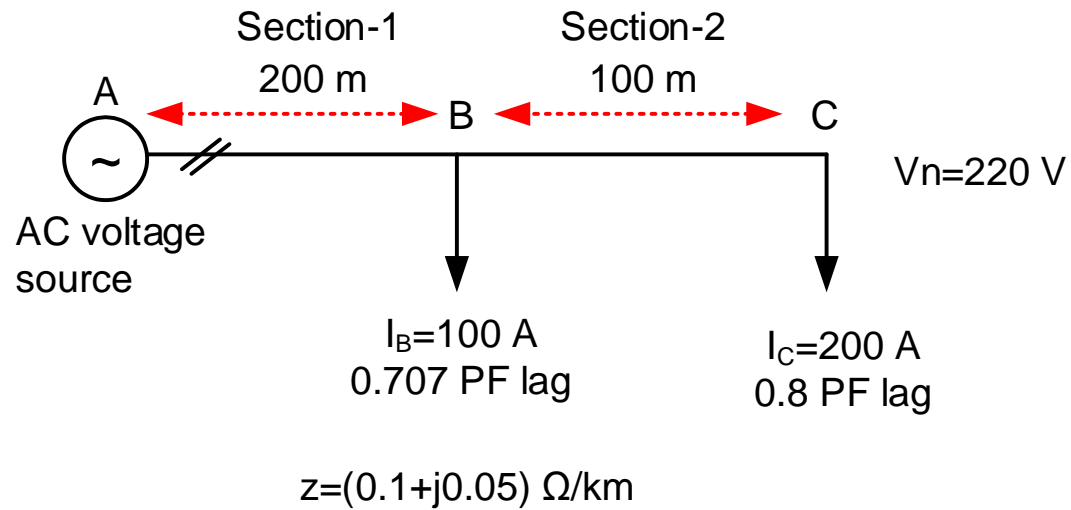Example: For the given single-phase radial distribution line, answer the following questions:

- Find the current in each section.
- Find the voltage drop on each section and on overall line (A-C).
- Find the percentage voltage drop on each section and on overall line (A-C).
- Find the voltage of the AC voltage source.



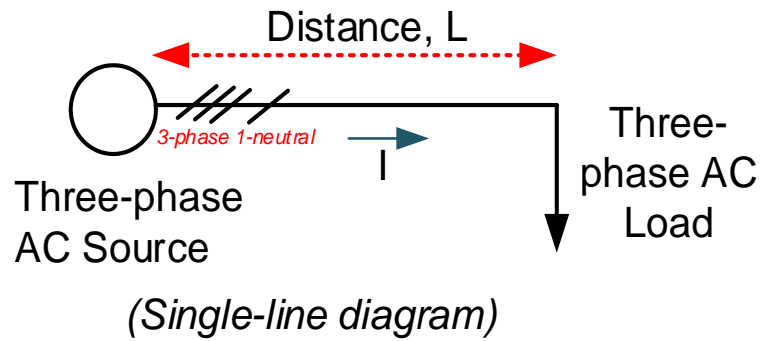Voltage Drop Calculation in Three-phase Systems




$$R = rL$$

$$X = xL$$

$$Z = R + jX$$

$$R = \frac{L}{\sigma A}$$

$$\sigma \cdot \rho = 1$$

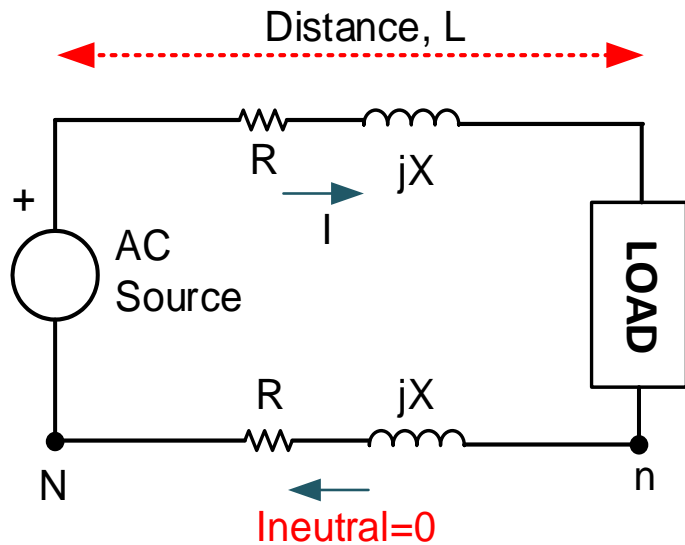

where

R is the **per-phase** AC resistance of the overhead-line or cable

X is the **per-phase** reactance of the overhead-line or cable

r is the **per-phase** per meter AC resistance of the overhead-line or cable (**Ω/m**)

x is the **per-phase** per meter reactance of the overhead-line or cable (**Ω/m**)


Z is the **per-phase** impedance of the overhead-line or cable

L is the distance between source and load (**m**)

σ is the conductivity of the conductor (**$m/\Omega.mm^2$**)

A is the cross-sectional area of the conductor (**mm^2**)

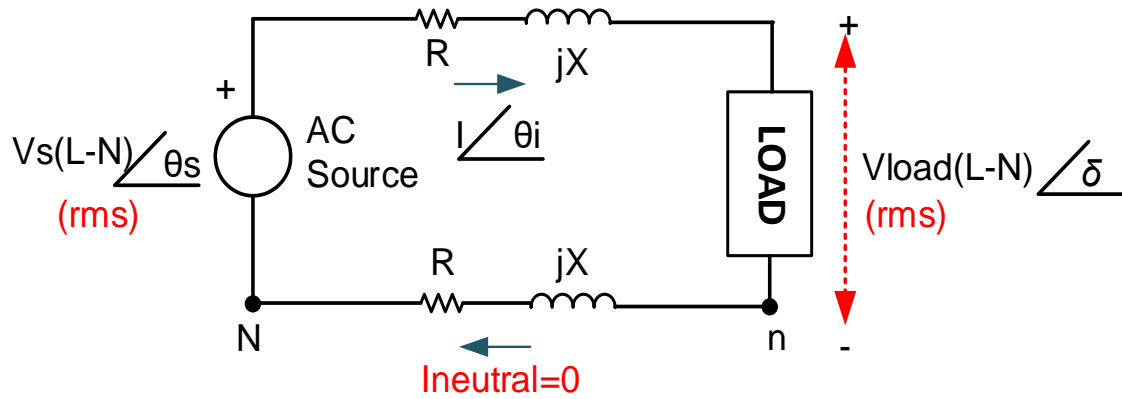ρ is the resistivity of the conductor (**$\Omega.mm^2/m$**)



From KVL:

$$V_s(L-N) \angle \theta_s - (I \angle \theta_i)(R+jX) - (V_{load}(L-N) \angle \delta) = 0$$


$$\Delta V = V_s(L-N) \angle \theta_s - V_{load}(L-N) \angle \delta$$

$$\Delta V = (I \angle \theta_i)(R+jX) \text{ (per phase voltage drop on the line)}$$


$$\Delta V = (I \angle \theta_i)Z \text{ (per phase voltage drop on the line)}$$

Since for balanced three-phase systems, neutral current is zero, multiplication factor **2** disappears from voltage drop equation


Case1: Lagging Load ($\theta_i < 0$)

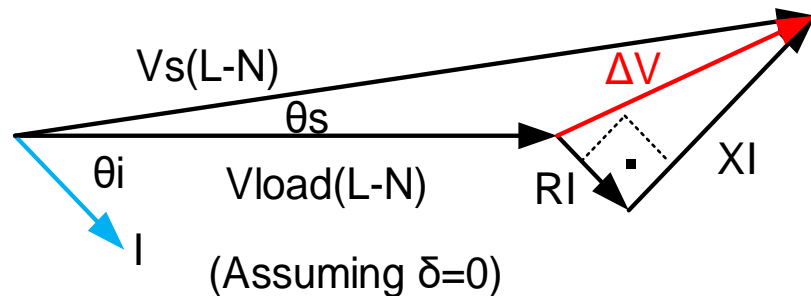

Case2: Leading Load ($\theta_i > 0$)

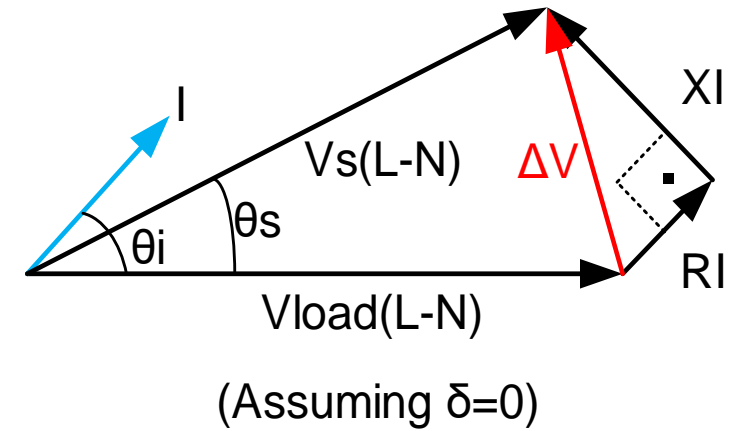


Case3: Unity PF Load ($\theta_i=0$)

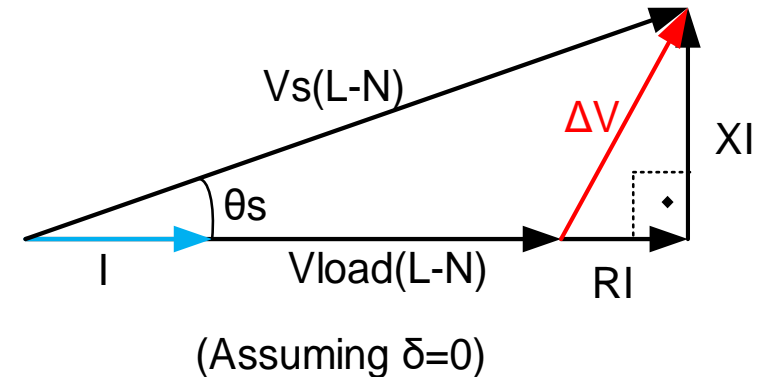


Approximate Voltage Drop Equations

Case1: Lagging Load ($\theta_i < 0$)

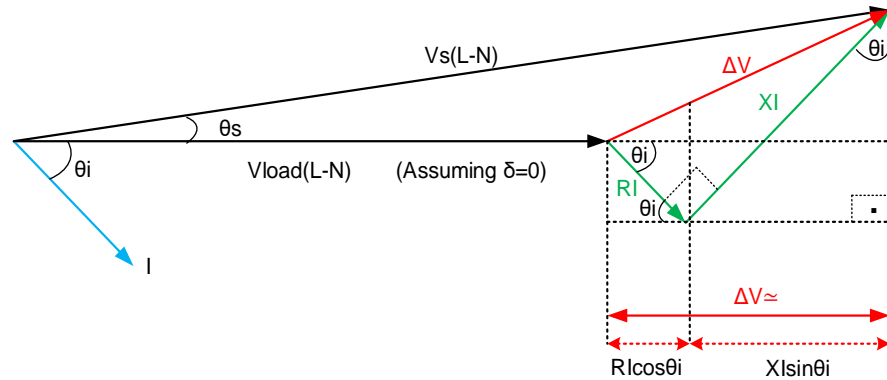


$$\Delta V \approx RI \cos \theta_i + XI \sin \theta_i$$

Case3: Unity PF Load ($\theta_i = 0$)

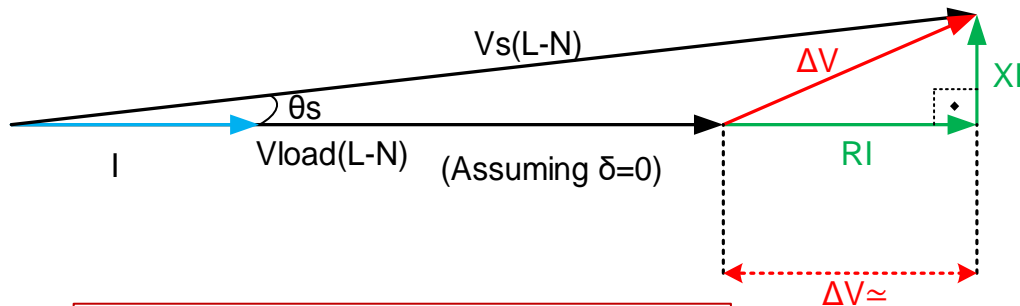

$$\Delta V \approx RI \cos \theta_i = RI \text{ (for } R \gg X \text{)}$$

Case2: Leading Load ($\theta_i > 0$)

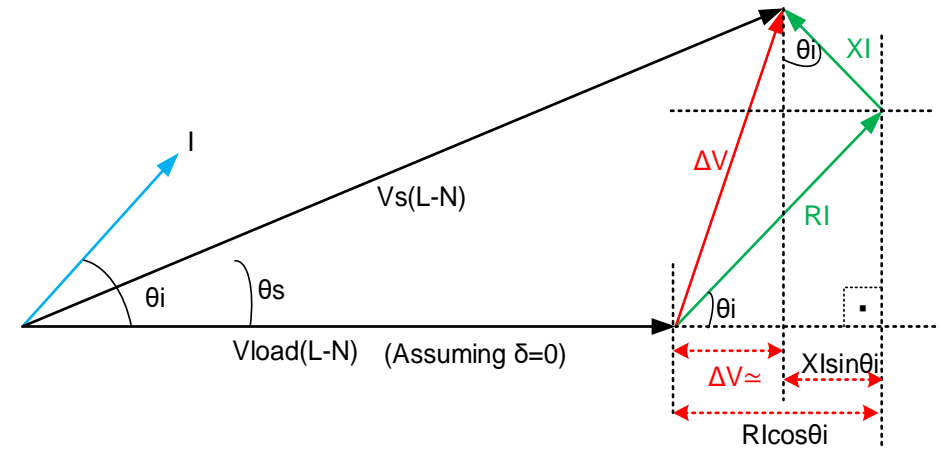

$$\Delta V \approx RI \cos \theta_i - XI \sin \theta_i$$

$$\% e = \frac{\Delta V}{V_n} \times 100\%$$

(per phase percentage voltage drop)

where

V_n is the nominal (rated) rms (L-N) system voltage

- ✓ V_n can be equal to $V_s(L-N)$ or
- ✓ V_n can be equal to $V_{load}(L-N)$ or
- ✓ V_n can be equal to a voltage, close to $V_s(L-N)$ or $V_{load}(L-N)$

Let's find a useful equation for percentage **per-phase** voltage drop in **three-phase systems**;

$$\%e = \frac{\Delta V}{V_n} \times 100\% \quad (\text{per-phase percentage voltage drop})$$

For Y-connection

$$\%e = \frac{\Delta V}{V_n} \times 100\% = \frac{RI \cos \theta_i \pm XI \sin \theta_i}{V_n} \times 100\%$$

Since \rightarrow $I = \frac{Pload}{3.Vload(LN) \cdot \cos(\delta - \theta_i)}$ (assuming $\delta=0$)

$$\%e = \frac{(R \cos \theta_i \pm X \sin \theta_i) Pload}{3.V_n.Vload(LN) \cdot \cos \theta_i} \times 100\%$$

If we assume $V_n = Vload(LN)$

$$\%e = \frac{(R \cos \theta_i \pm X \sin \theta_i) Pload}{3.Vload(LN)^2 \cdot \cos \theta_i} \times 100\%$$

$$\%e = \frac{(R \cos \theta_i \pm X \sin \theta_i) Pload}{3.Vload(LN)^2 \cdot \cos \theta_i} \times 100\%$$

or

$$\%e = \frac{(R \pm X \tan \theta_i) Pload}{3.Vload(LN)^2} \times 100\%$$

or

$$\%e = \frac{(1 \pm \frac{X}{R} \tan \theta_i) \cdot R \cdot Pload}{3.Vload(LN)^2} \times 100\%$$

Let Inductive (lagging PF)

$$f(\varphi) = (1 \pm \frac{X}{R} \tan \theta_i)$$

Capacitive (leading PF)

$$\%e = \frac{R \cdot Pload}{3.Vload(LN)^2 \cdot \sigma A} \cdot f(\varphi) \times 100\%$$


Since $\rightarrow R = \frac{L}{\sigma A}$

$$\%e = \frac{Pload \cdot L \cdot f(\varphi)}{3.Vload(LN)^2 \cdot \sigma \cdot A} \times 100\%$$

Since $\rightarrow Vload(LN) = \frac{VLoad(LL)}{\sqrt{3}}$

$$\%e = \frac{Pload \cdot L \cdot f(\varphi)}{Vload(LL)^2 \cdot \sigma \cdot A} \times 100\%$$

For Y-connected load

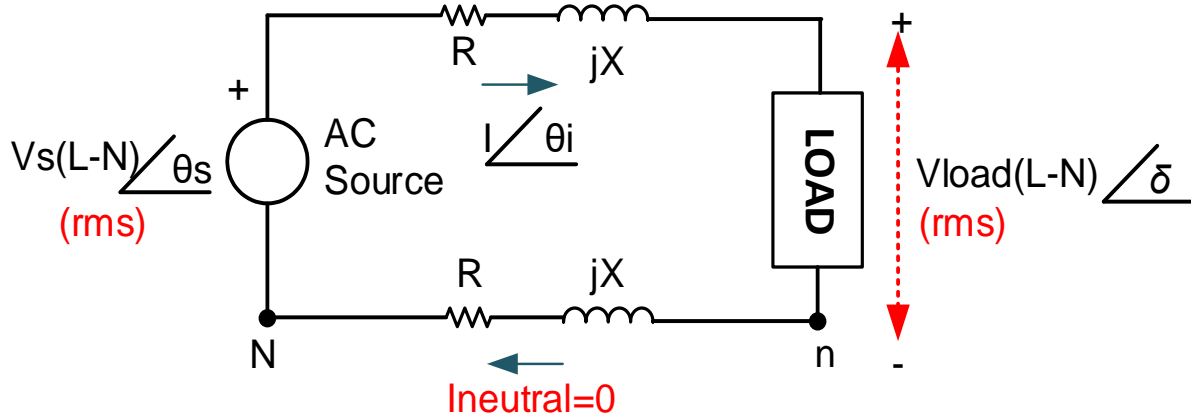

$$P_{in} = 3.V_s(LN).I.\cos(\theta_s - \theta_i) \text{ (input active power, W)}$$

$$P_{in} = \sqrt{3}.V_s(LL).I.\cos(\theta_s - \theta_i)$$

$$P_{out} = P_{load} = 3.V_{load}(LN).I.\cos(\delta - \theta_i)$$

$$P_{out} = P_{load} = \sqrt{3}.V_{load}(LL).I.\cos(\delta - \theta_i) \text{ (output active power, W)}$$

(active power loss, W)

$$P_{loss} = 3RI^2 \text{ (R is per-phase resistance)}$$

$$P_{in} = P_{out} + P_{loss}$$

$$Q_{in} = 3.V_s(LN).I.\sin(\theta_s - \theta_i)$$

$$Q_{in} = \sqrt{3}.V_s(LL).I.\sin(\theta_s - \theta_i) \text{ (input reactive power, VAR)}$$

$$Q_{out} = Q_{load} = 3.V_{load}(LN).I.\sin(\delta - \theta_i)$$

$$Q_{out} = Q_{load} = \sqrt{3}.V_{load}(LL).I.\sin(\delta - \theta_i) \text{ (output reactive power, VAR)}$$

$$Q_{loss} = 3XI^2 \text{ (reactive power loss, VAR)}$$

(X is per phase reactance)

$$Q_{in} = Q_{out} + Q_{loss}$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% \text{ (percentage efficiency)}$$

$$\% P_{loss} = \frac{3RI^2}{P_{load}} \times 100\%$$

(percentage (active) power loss)

For Δ -connected load

$$P_{in} = 3.V_s(LL). \frac{I}{\sqrt{3}} . \cos(\theta_s - \theta_i)$$

$$P_{in} = \sqrt{3}.V_s(LL).I. \cos(\theta_s - \theta_i) \quad (\text{input active power, W})$$

$$P_{out} = P_{load} = 3.V_{load}(LL). \frac{I}{\sqrt{3}} . \cos(\delta - \theta_i)$$

$$P_{out} = P_{load} = \sqrt{3}.V_{load}(LL).I. \cos(\delta - \theta_i) \quad (\text{output active power, W})$$

$$P_{loss} = 3RI^2 \quad (\text{active power loss, W}) \\ (\mathbf{R \text{ is per-phase resistance}})$$

$$P_{in} = P_{out} + P_{loss}$$

$$Q_{in} = 3.V_s(LL). \frac{I}{\sqrt{3}} . \sin(\theta_s - \theta_i)$$

$$Q_{in} = \sqrt{3}.V_s(LL).I. \sin(\theta_s - \theta_i) \quad (\text{input reactive power, VAR})$$

$$Q_{out} = Q_{load} = 3.V_{load}(LL). \frac{I}{\sqrt{3}} . \sin(\delta - \theta_i)$$

$$Q_{out} = Q_{load} = \sqrt{3}.V_{load}(LL).I. \sin(\delta - \theta_i) \quad (\text{output reactive power, VAR})$$

$$Q_{loss} = 3XI^2 \quad (\text{reactive power loss, VAR}) \\ (\mathbf{X \text{ is per-phase reactance}})$$

$$Q_{in} = Q_{out} + Q_{loss}$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% \quad (\text{percentage efficiency})$$

$$\% P_{loss} = \frac{3RI^2}{P_{load}} \times 100\%$$

(percentage (active) power loss)

Example: For $\%e \leq 5$, calculate the **maximum length** of the **Rose conductor** when it carries its **maximum apparent power** in a three-phase system. Take power factor as **0.8 lagging**, $V_n = 220 \text{ V (L-N)}$, and $\sigma = 35 \text{ m}/\Omega.\text{mm}^2$

Solution: $S_{\text{max}} = 72.6 \text{ kVA}$ (using table data)
 $P_{\text{max}} = S_{\text{max}} \cdot \cos\theta = (72.6)(0.8) = 58.08 \text{ kW}$

$$\%e = \frac{P_{\text{load}} \cdot L}{3 \cdot V_{\text{load}}(LN)^2 \cdot \sigma \cdot A} \cdot f(\varphi) \times 100\%$$

Substituting the parameters into the equation:

$$5 = \frac{(58.08 \times 10^3) \cdot L}{3 \cdot 220^2 \cdot 35 \cdot (21.14)} \cdot (1.191) \times 100\%$$


$L(\text{max}) = 77.655 \text{ m}$

Alçak Gerilimli Hava Hatlarında Kullanılan Alüminyum İletkenler ve Özellikleri

K. Standartı Arma Adı	Kesit mm^2	Çap mm	Kopma Kuvveti kgk	Ağırlık kgk/m	DC Direnci 20°C'da $\Omega/\text{km} \cdot \text{f}$	End. Reakt. $f=50\text{Hz}$ $\Omega/\text{km} \cdot \text{f}$	$f(\varphi)$ Fakt. (%) End 1	γ $f(\varphi)/3\text{kV}$ $\times 10^{-6}$ $1/\text{A} \cdot \text{m}$	Yükl. Akımı (Tasima Kapasitesi) A
Rose	21,14	5,88	415	58	1,3510	0,345	1,191	2,44	110
Lily	26,66	6,61	515	73	1,0720	0,337	1,235	2,01	125
İris	33,65	7,42	640	92	0,8498	0,330	1,291	1,66	143
Pansy	42,37	8,33	775	116	0,6739	0,322	1,358	1,39	165
Poppy	53,49	9,36	940	146	0,5341	0,315	1,442	1,17	193
Aster	67,45	10,51	1185	184	0,4236	0,307	1,543	0,99	225
Phlox	84,99	11,80	1435	232	0,3360	0,300	1,669	0,85	262
Oxlip	107,30	13,25	1810	293	0,2664	0,293	1,824	0,74	306

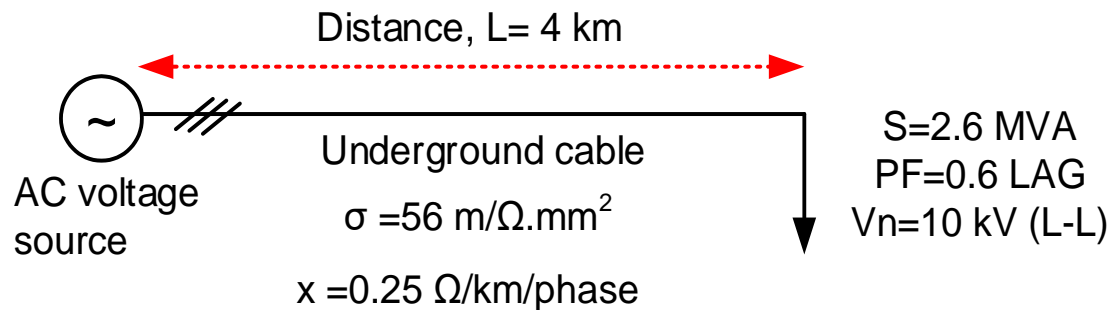Example: For the given three-phase underground distribution, answer the following questions:

- For a maximum of **6 % Ploss**, what should be the value for cross-section of the conductor, **A=?**
- Find the real and the imaginary parts of the line current.
- Find the per-phase voltage drop on the cable.
- Find the percentage per-phase voltage drop on the cable.
- Find L-L voltage, input active power, and power factor of the three-phase voltage source.




P.S1: For medium voltage distribution, there is **no neutral line**

P.S2: All voltages in medium voltage systems ($>1\text{kV}$) are **Line-to-Line (L-L)** voltages if otherwise is not specified

P.S3: For medium voltage distribution, conductor cross-sections are starting from **50 mm²**

P.S4: If there is **more than one condition** to choose a cross-section, always choose **the biggest one** who satisfies all conditions

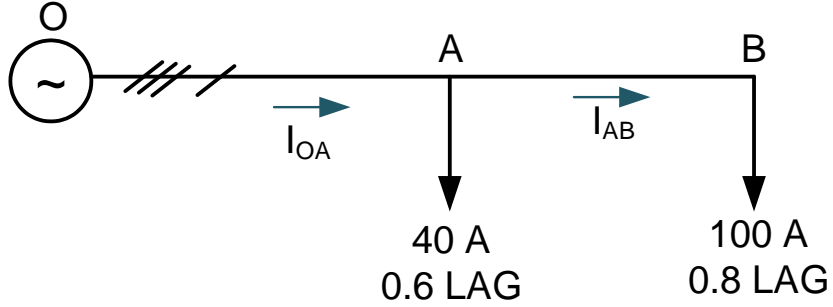Example: For the given low-voltage three-phase radial distribution line, find the current in each section and choose suitable conductors from the given table according to the current carrying capacities. Note that required percentage voltage drop and the distances are not given.




Alçak Gerilimli Hava Hatlarında Kullanılan Alüminyum İletkenler ve Özellikleri

K. Standartı Anam Adı	Kesit mm ²	Çap mm	Kopma Kuvveti kgk	Ağırlık kgk/m	DC Direnci 20°C'da Ω/km.f	End. Reakt. f=50Hz Ω/km.f	f(φ) Fakt. (0,8)end 1	γ f(φ)/3kqV x10 ⁻⁶ 1/A.m	Yükl. Akımı (Taşıma Kapasitesi) A
Rose	21,44	5,88	415	58	1,3510	0,345	1,191	2,44	110
Lily	26,66	6,61	515	73	1,0720	0,337	1,235	2,01	125
İris	33,65	7,42	640	92	0,8498	0,330	1,291	1,66	143
Pansy	42,37	8,33	775	116	0,6739	0,322	1,358	1,39	165
Poppy	53,49	9,36	940	146	0,5341	0,315	1,442	1,17	193
Aster	67,45	10,51	1185	184	0,4236	0,307	1,543	0,99	225
Phlox	84,99	11,80	1435	232	0,3360	0,300	1,669	0,85	262
Oxlip	107,30	13,25	1810	293	0,2664	0,293	1,824	0,74	306

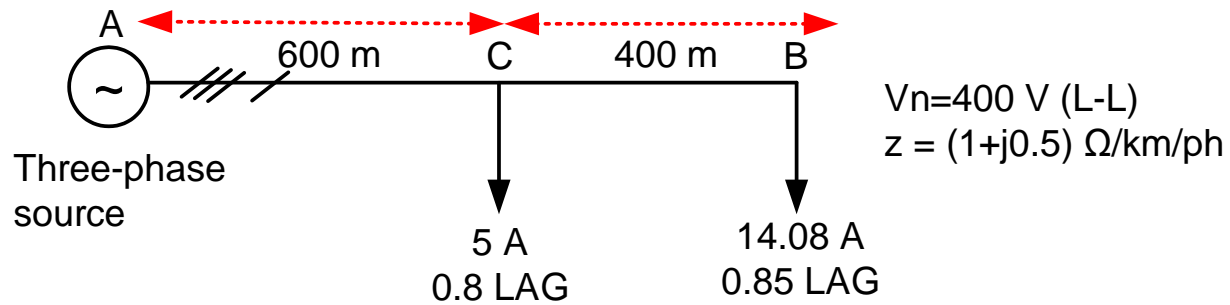Example: For the three-phase low voltage distribution, answer the following questions:

- Find the current distributions on the line.
- Find the rms (L-L) voltage of the points A and C, if $V_n=400$ V (L-L) at point B.
- Does the available cross-section satisfy the condition: $\%e \leq 5$?
- Does the available cross-section satisfy the condition: $\%P_{loss} \leq 6$?



END OF THE LECTURE

Any questions ?