1

2



### **Electromechanical Energy Conversion – I**

Ву

Prof. Dr. A. Mete VURAL mvural@gantep.edu.tr

### **CHAPTER 2**

TRANSFORMERS

### Introduction

• **Transformer** is an electrical machine that converts ac electrical energy/power at **one voltage level** to ac electrical energy/power at **another voltage level** through the action of magnetic field.



# <section-header>

The original 1885 Stanley prototype transformer at the Berkshire Museum. Source: http://edisontechcenter.org/Transformers.html



# Introduction

### Why are transformers important?

- Transformer is also widely used in low-power, low-current electronic and control circuits for performing such functions:
  - Matching the impedances of a source and its load for maximum power transfer
  - Isolating one circuit from another
  - > Isolating direct current while maintaining ac continuity between two circuits



### Introduction

- Transformer consists of two or more coils of wire wrapped around a common ferromagnetic core.
- These coils are (usually) not directly (electrically) connected.
- The only connection between the coils is the common magnetic flux present within the core.



## **Construction Of Transformers**

- · Power transformers are constructed by two types of cores.
- These are «core form» and «shell form».
- In core form, there is a simple rectangular laminated piece of steel with the transformer windings wrapped around two sides of the rectangle.
- In shell form, there is a three-legged laminated core with the windings wrapped around the center leg.
- In either case, the core is constructed of <u>thin laminations</u> electrically isolated from each other in order to minimize eddy currents.





## **Construction Of Transformers**

- The primary and secondary windings in a physical transformer are wrapped one on top of the other with the <u>low-</u> voltage winding innermost. Such an arrangement serves two purposes:
- > It simplifies the problem of insulating the high-voltage winding from the core.
- It results in much less leakage flux than would be the case if the two windings were separated by a distance on the core.







### **Transformer Types** • Substation transformer: This transformer is a step-down transformer and connected to the end of a transmission line in a substation and used to step the transmission voltage from (110 kV or more) down to distribution levels (36 kV or less). Color Key: Blue: Transmission Subtransmission Green: Distribution Customer Transmission Lines Black: Generation 26kV and 69kV 765, 500, 345, 230, and 138 kV Substation Primary Customer Step-Down 13kV and 4kV Transformer Secondary Customer Generating Station Transmission 120V and 240V Generator Step Customer 138kV or 230kV Up Transformer 13



# <text><text><image>





### Transformer Analysis: No-load Condition

 If R1 is the resistance of the primary winding, this resistance causes a <u>small voltage drop</u> and the following voltage equation can be written:

$$v_1 = R_1 i_{\varphi} + e_1$$

Under no-load conditions:

- we can neglect the effects of primary leakage flux
- Resistive voltage drop is too small
- The waveforms of voltage and flux are very nearly sinusoidal











23

## Transformer Analysis: No-load Condition

### **Core loss calculation:**

 The core loss (Pc) (hysteresis + eddy current losses) is calculated as follows:

 $P_{\rm c} = E_1 I_{\varphi} \cos \theta_{\rm c}$ 

where

 $P_c$  is the core loss of the transformer (Watt)  $E_1$  is the rms value of the induced voltage (V)  $\theta_c$  is the power factor angle of exciting current

*Pc* must be **multiplied by 3** if the transformer is a **three-phase transformer**.





# Ideal Transformer

• The "turns ratio" of a transformer is defined as

$$a = \frac{N_1}{N_2} = \frac{V_1}{V_2}$$
  $a = \frac{N_1}{N_2} = \frac{I_2}{I_1}$ 

- Since "a" is a <u>real number</u> for ideal transformer:
   The phase angles of V<sub>1</sub> and V<sub>2</sub> are <u>same</u>.
   The phase angles of I<sub>1</sub> and I<sub>2</sub> are <u>same</u>.
- For a step-up transformer → a < 1
- For a step-down transformer → a > 1
- For an insulating transformer → a = 1
- For an ideal transformer, instantaneous power at both sides are same:

$$\frac{V_1}{V_2} = a$$
  $\frac{I_2}{I_1} = a$   $v_1i_1 = av_2\left(\frac{1}{a}\right)i_2 = v_2i_2$  Because ideal transformer is an ideal device having no loss





### Ideal Transformer

### **Dot Convention:**

- If the primary voltage is positive at the dotted end of the winding with respect to the undotted end, then the secondary voltage will be positive at the dotted end also.
- If the primary current of the transformer flows into the dotted end of the primary winding, the secondary current will flow out of the dotted end of the secondary winding.





### Impedance Transformation in a Transformer

• An **impedance (ZL)** at the **secondary side** of a transformer can be transferred to the **primary side** or vice-versa:

$$Z_L = \frac{V_S}{I_S} = \frac{V_P/a}{aI_P} = \frac{1}{a^2} \frac{V_P}{I_P}$$

• If we call  $Z_L' = V_P / I_P$ 

 $Z_L' = a^2 Z_L$  (Referred impedance to the primary side)

• In reality, there is **no actual movement** of this impedance. This is just **in theory** which simplifies our calculations.









### Theory of Real Single-Phase Transformers

• Similarly, the total flux ( $\phi_S$ ) linking the secondary winding is divided into two components:





### Theory of Real Single-Phase Transformers

- Applying Faraday's Law to the primary side:
- Applying Faraday's Law to the secondary side:



37

# Theory of Real Single-Phase Transformers

### **Turns Ratio:**

$$e_{p}(t) = N_{p} \frac{d\phi_{M}}{dt}$$

$$e_{S}(t) = N_{S} \frac{d\phi_{M}}{dt}$$

$$\boxed{\frac{e_{p}(t)}{e_{S}(t)} = \frac{N_{p}}{N_{S}} = a}$$

- The above equation means that the ratio of the primary voltage caused by the mutual flux to the secondary voltage caused by the mutual flux is equal to the turns ratio of the transformer.
- In a well-designed transformer,

$$\begin{array}{c|c} \phi_M >> \phi_{\mathsf{LP}} \\ \phi_M >> \phi_{\mathsf{LS}}, \end{array} \qquad \begin{array}{c} v_P(t) \\ v_S(t) \end{array} \cong \frac{N_P}{N_S} = a \end{array}$$



# **The Exact Equivalent Circuit of a Transformer**. We have to consider the following points when modelling a real transformer: 1. <u>Copper losses:</u> Copper losses are the resistive heating losses in the primary and secondary windings of the transformer. They are proportional to the square of the current in the windings. 2. <u>Eddy current losses:</u> Eddy current losses are resistive heating losses in the core of the transformer. They are proportional to the square of the voltage applied to the transformer. 3. <u>Hysteresis losses:</u> Hysteresis losses are associated with the rearrangement of the magnetic domains in the core during each half-cycle, as explained before. These losses are proportional to the applied voltage. 4. <u>Leakage flux:</u> These fluxes escape the core and pass through only one of the windings. Leakage fluxes produce a self-inductance in the primary and secondary coils, and the effects of this inductance must be considered.









# The Equivalent Circuit of a Transformer

 The ideal transformer symbol <u>can be removed</u> from the equivalent circuit by refereeing one side into another as shown below:



Equivalent circuit of single-phase transformer referrred to <u>**PRIMARY</u>** side</u>



Equivalent circuit of single-phase transformer referrred to <u>SECONDARY</u> side





## **Approximate Equivalent Circuits**

**Example:** A **50-kVA 2400:240-V 60-Hz** distribution transformer has a leakage impedance of **0.72 + j0.92 ohm** in the high-voltage winding and **0.0070 + j0.0090 ohm** in the low-voltage winding. At rated voltage and frequency, the impedance of the shunt branch (*equal to the impedance of Rc and jXm in parallel*) accounting for the exciting current is **6.32 + j43.7 ohm** when viewed from the low-voltage side.

Draw the equivalent circuit referred to

- (a) the high-voltage side
- (b) the low-voltage side, and label the impedances numerically.

# Self-study

The equivalent circuit shows an ideal transformer with an impedance of (R2+jX2) equals to 1 + j4 ohm connected in series with the secondary. The turns ratio N1/N2 = 5:1. (a) Draw an equivalent circuit with the series impedance referred to the primary side. (b) For a primary voltage of 120 V rms and a short connected across the terminals A-B, calculate the primary current and the current flowing in the short.



# Self Study

The **50-kVA 2400:240-V 60-Hz** single-phase distribution transformer has a leakage impedance of **0.72 + j0.92 ohm** in the high-voltage winding and **0.0070 + j0.0090** ohm in the low-voltage winding. This transformer is used to step down the voltage at the load end of a feeder whose impedance is **0.30 + j 1.60 ohm**. The voltage Vs at the sending end of the feeder is **2400 V**. Find the voltage at the secondary terminals of the transformer when the load connected to its secondary draws rated current from the transformer and the power factor of the load is **0.80 lagging**. *Neglect excitation branch*.



## **Determining Equivalent Circuit Parameters**

- It is possible to experimentally determine the values of the inductances and resistances in the transformer approximate model (*slide no:46*).
- An adequate approximation of these values can be obtained by <u>two tests</u>:
  - Open-circuit test
  - Short-circuit test
- In the open-circuit test, the secondary side is open-circuited and excitation branch parameters are approximayely found.
- In the short-circuit test, the secondary side is short-circuited and series equivalent impedance is approximayely found.



## **Determining Equivalent Circuit Parameters**

### **Steps of Open Circuit Test:**

- The **full** (*rated*) line voltage is applied to the primary of the transformer.
- The input voltage, input current, and input real power to the transformer are measured by the voltmeter, ammeter, and wattmeter, respectively as shown in the figure.
- From this information, it is possible to determine the excitation impedance using the equations below:
- The magnitude of the **excitation admittance** (*referred to the primary side*) can be found as

 $|Y_E| = \frac{I_{\rm OC}}{V_{\rm OC}} \longrightarrow$  Ammeter reading Voltmeter reading







### **Determining Equivalent Circuit Parameters**

### **Steps of Short Circuit Test:**

- The secondary terminals of the transformer are short circuited.
- The primary terminals are connected to a fairly low-voltage source.
- The input voltage is adjusted until the current in the shortcircuited windings is equal to its rated value. (*Be sure to keep the primary voltage at a safe level. It would not be a good idea to burn out the transformer's windings while trying to test it.*)
- The input voltage, input current, and input real power are again measured by the voltmeter, ammeter, and wattmeter, respectively.
- From this information, it is possible to determine the series impedance using the following equations:



 $\geq_{R_c}$ 

aV.

### **Determining Equivalent Circuit Parameters**

### **Steps of Short Circuit Test:**



$$|Z_{SE}| = \frac{V_{SC}}{I_{SC}} \longrightarrow$$
 Voltmeter reading

• The power factor angle of the series impedance is calculated as

$$PF = \cos \theta = \frac{P_{SC}}{V_{SC}I_{SC}} \quad \text{Wattmeter reading}$$
  

$$\theta = \cos^{-1} \frac{P_{SC}}{V_{SC}I_{SC}} \quad (Power factor angle)$$
  

$$Voltmeter reading \quad \text{Ammeter reading}$$
  

$$\cdot \text{ From the information of } |Z_E| \text{ and } \theta, \text{ it is possible to} \\ \text{calculate } R_{eq} \text{ and } X_{eq}, \text{ as follows:} \quad P_{SC} Z_{SE} = (V_{SC}) + (I_{SC}) + (I_{SC})$$

# Self-study

The equivalent circuit impedances of a **20-kVA**, **8000/240-V**, **60-Hz** transformer are to be determined. The opencircuit test and the short-circuit test were performed on the primary side of the transformer, and the following data were taken:

Open-circuit test (on primary)	Short-circuit test (on primary)	
$V_{\rm OC} = 8000  \mathrm{V}$	$V_{\rm SC} = 489  \rm V$	
$I_{\rm OC}=0.214{\rm A}$	$I_{\rm SC} = 2.5  {\rm A}$	
$V_{\rm OC} = 400 \ {\rm W}$	$P_{\rm SC} = 240 \ { m W}$	

Find the impedances of the approximate equivalent circuit (*slide no:46, figure b*) referred to the primary side, and sketch that circuit.

# Voltage Regulation of Transformers

- A practical transformer has always a series impedance.
- As a result, the secondary (output) voltage of a transformer <u>varies</u> with the load even if the primary (input) voltage remains <u>constant</u>.
- Voltage regulation is the percentage of voltage difference between no load and full load (*rated*) voltages of a transformer with respect to its full load voltage.
- Voltage regulation is a performance parameter of the transformers which is used for comparison of transformers.

$$VR = \frac{V_{\mathcal{S},nl} - V_{\mathcal{S},nl}}{V_{\mathcal{S},nl}} \times 100\%$$

where VR is the voltage regulation in % percentage  $V_{s,nl}$  is the **no-load** voltage of secondary side  $V_{s,fl}$  is the **full-load** (*rated load*) voltage of secondary side

A well-designed transformer will normally has **low** voltage regulation which is mostly less than **10%**.

An **ideal** transformer will have zero voltage regulation











# Voltage Regulation of Transformers

- So far, we have seen that voltage regulation can be either **positive** or **negative** depending on the **load power factor type**.
- Also, voltage regulation changes as load changes as seen below:



## **Transformer Efficiency**

- The **efficiency** of a transformer is defined as the ratio of its output real (*active*) power (*P*<sub>out</sub>) to its input real (*active*) power (*P*<sub>in</sub>), usually expressed in % percentage.
- The efficiency of an ideal transformer is 100%.
- For practical transformers, the efficiency is close but less than 100%.
- The efficiency is a performance parameter like "voltage regulation", used to compare transformers.
- The efficiency of a transformer can be calculated by the following equation:

$$\boxed{\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\%} \qquad P_{out} = \text{Vs. Is. } \cos(\theta_s)$$
$$P_{in} = \text{Vp. Ip. } \cos(\theta_p)$$

Vs is the rms voltage of secondary side Is is the rms current of secondary side  $\theta_s$  is the phase angle between Vs and Is Vp is the rms voltage of primary side Ip is the rms current of primary side  $\theta_p$  is the phase angle between Vp and Ip

### **Transformer Efficiency**

### Typical efficiencies for some power transformers

Single Phase		Three Phase	
kVA	Efficiency	kVA	Efficiency
15	97.7	15	97.0
25	98.0	30	97.5
37.5	98.2	45	97.7
50	98.3	75	98.0
75	98.5	112.5	98.2
100	98.6	150	98.3
167	98.7	225	98.5
250	98.8	300	98.6
333	98.9	500	98.7
-		750	98.8
Source: MEMA TP-1-2002		1000	98.9

Source: https://library.automationdirect.com

66





# **Transformer Loss Calculation**

There are also reactive losses of the transformers, besides their real losses.

- Reactive losses are due to the
  - Leakage reactance of the primary winding
  - Leakage reactance of the secondary winding
  - The reactance of the core

Rated power (kVA)	Reactive power (kvar) to be compensated			
	No load	Full load		
100	2.5	6.1		
160	3.7	9.6		
250	5.3	14.7		
315	6.3	18.4		
400	7.6	22.9		
500	9.5	28.7		
630	11.3	35.7		
800	20	54.5		
1000	23.9	72.4		
1250	27.4	94.5		
1600	31.9	126		
2000	37.8	176		
Reactive power consumption of some distribution transformers with 20 kV primary windings				

 $Q_{losses} = Q_{windings} + Q_{core}$ 



# Self-study

• Solve the Example 2.5 at page 103 from Chapman

# Self-Study

An open circuit and short-circuit tests are performed on a 50-kVA 2400:240-V single-phase transformer and the following data are obtained. Find at first, the equivalent circuit parameters of the transformer and determine the efficiency and the voltage regulation at full load for a power factor of

a) 0.95 lagging

b) 0.75 leading

c) Unity

Open circuit test (on the HV side)	Short circuit test (on the HV side)
Voltmeter reading = 240 V	Voltmeter reading = 48 V
Ammeter reading = 5.41 A	Ammeter reading = 20.8 A
Wattmeter reading = 186 W	Wattmeter reading = 617 W



### Autotransformers

Example: The 50-kVA, 2400:240-V transformer is connected as an autotransformer, as shown in the figure. The winding *ab* is the 240-V winding, while the winding *dc* is the 2400-V winding.

(It is assumed that the 240-V winding has enough insulation to withstand a voltage of 2640 V to ground.)

- a) Compute the voltage and current ratings of high-voltage and low-voltage sides, respectively.
- b) Compute the kVA rating of the autotransformer.







77

## Self-study

- Solve Example 2.7 at page 113 from Chapman
- Solve Example 2.8 at page 116 from Chapman

# Three-phase Transformers

- Almost all the major power generation and distribution systems in the world today are three-phase AC systems.
- Three-phase transformers are used to interconnect these systems having different voltage levels.









### **Three-phase Transformers** The primaries and secondaries of any three-phase transformer can be independently connected in either Wye ٠ (Y) or Delta (D). This gives a total of **four possible connections** for **three-phase transformers**: ٠ 1) Wye-Wye (Y-Y) or Star-Star aI/√3 √3 aI visa V/c V/√3 a 1/√3 2) Wye-Delta (Y-D) or Star-Delta a 3) Delta-Wye (D-Y) or Delta-Star (a) Y- $\Delta$ connection (b) $\Delta$ -Y connection 4) Delta-Delta (D-D) 1/√3 aI/√3 (c) $\Delta$ - $\Delta$ connection (d) Y-Y connection Common three-phase transformer connections. The transformer windings are indicated by the heavy lines 82

# **Three-phase Transformers**

- 1) Wye-Wye (Y-Y) Connection:
- In this connection type, both the primary and secondary side are connected in Wye (Y) as shown below.



# Three-phase Transformers

- 1) Wye-Wye (Y-Y) Connection:
- In this connection type, both the primary and secondary side are connected in Wye (Y) as shown below.







# **Three-phase Transformers**

The Attributes of Wye-Wye (Y-Y) Connection:

- The Y-Y connection is seldom used because:
  - If loads connected to the transformer are <u>unbalanced</u>, then the LL voltages of the transformer <u>can become</u> <u>severely unbalanced</u> due to <u>unequal voltage drops on phase impedances</u> of the transformer.
  - > <u>Third-harmonic voltages</u> can be large because of the **nonlinearity** of the **transformer core**.
- Both problems **negatively affect** the **power quality** of the power system in which this type of transformer is connected.
- The <u>unbalance problem</u> and the <u>third-harmonic problem</u> can be solved using one of two techniques:

88

# Three-phase Transformers

The Attributes of Wye-Wye (Y-Y) Connection:

Both the <u>unbalance problem</u> and the <u>third-harmonic problem</u> can be solved using one of two techniques:

**1)** <u>Solidly ground</u> the neutral points (*N* and *n*) of the Y-Y transformer: By this way, the neutral provides a return path for any current imbalances in the load. Moreover, by this way, the third-harmonic currents flow in the neutral instead of building up unwanted large third-harmonic voltages.



**2)** <u>Add a third (tertiary) winding</u> to the transformer as shown below. By this way, the third-harmonic voltages cause a circulating current flow within this winding and harmonics will not be reflected outside of the windings.



89

# **Three-phase Transformers**

### 2) Wye-Delta (Y-D) Connection:

• In this connection type, the primary is connected as Wye (Y) and secondary is connected as Delta (D) as shown below.



## **Three-phase Transformers**

### 2) Wye-Delta (Y-D) Connection:

• In this connection type, the primary is connected as Wye (Y) and secondary is connected as Delta (D) as shown below.



### **Three-phase Transformers** 2) Wye-Delta (Y-D) Connection: • In this connection type, the primary is connected as Wye (Y) and secondary is connected as Delta (D) as shown below. $V_{AB} = V_{AN} - V_{BN}$ LL voltages at $V_{BC} = V_{BN} - V_{CN}$ **PRIMARY SIDE** $V_{CA} = V_{CN} - V_{AN}$ Α $V_{AB}$ а $V_{BN}$ $V_{CA}$ $V_{ab}$ V<sub>BC</sub> V $V_{ca}$ b Primary Side Secondary Side $V_{bc}$ Phasor diagrams of Y-D connection **PRIMARY SIDE SECONDARY SIDE** Source: https://electricalnotes.wordpress.com 91 Y-D connection diagram



# **Three-phase Transformers**

The Attributes of Wye-Delta (Y-D) Connection:

- This connection has <u>no problem</u> with third-harmonic components in its voltages, since they are consumed in a circulating current on the delta side.
- This connection is also more stable with respect to unbalanced loads, since the delta side partially redistributes any imbalance that occurs.
- This arrangement has a property that the **primary side LL voltages** are leading the **secondary side LL voltages** by **30° degrees**.
- This **natural phase shift** can cause problems during **paralleling different types of transformers**. For example when paralleling a **Y-Y** transformer and a **Y-D** transformer.
- Since, the **phase angles of the secondary voltages must be** <u>same</u> if two transformers are **connected in parallel** for **load sharing**.

### **Three-phase Transformers** The Attributes of Wye-Delta (Y-D) Connection: The Y-D connection is commonly used in stepping down from a high voltage to a medium or low voltage. One reason is that a neutral is provided for grounding on the high-voltage side that is used to protect the transmission line from very high fault currents and to reduce insulation costs of the transmission side. **Basic Structure of the Electric System** Color Key: Blue: Transmission Transmission Lines 500, 345, 230, and 138 kV Green: Distribution 2644 Black Generation Y-D Primary Cus 13kV and 4 Generator Step Up Transfor **Generating Station** 138kV or 230kV ndary Cus 94

95

# **Three-phase Transformers**

### 3) Delta-Wye (D-Y) Connection:

• In this connection type, the primary is connected as Delta (D) and secondary is connected as Wye (Y) as shown below.



## **Three-phase Transformers**

### 3) Delta-Wye (D-Y) Connection:

• In this connection type, the primary is connected as Delta (D) and secondary is connected as Wye (Y) as shown below.







## **Three-phase Transformers**

The Attributes of Delta-Wye (D-Y) Connection:

- The D-Y connection has the same advantages and the same phase shift as the Y-D transformer.
- The D-Y connection is commonly used in stepping up from medium or low voltage to a high voltage.
- One reason is that a neutral is provided for grounding on the high-voltage side that is used to protect the transmission line from very high fault currents and to reduce insulation costs of the transmission side.





### 4) Delta-Delta (D-D) Connection:

• In this connection type, the primary and secondary side are connected as Delta (D) as shown below.









### Derating of a Transformer

- If a 60-Hz transformer is to be operated on 50-Hz power system, its applied voltage (*primary*) must also be <u>reduced</u> by a factor of 1/6.
- If this is not done, the transformer core can go to the saturation region and the peak flux in the core will be too high.
- This reduction in applied voltage together with the frequency is called «*derating*».

$$v(t) = V_M \sin \omega t \quad (primary applied voltage)$$

$$\phi(t) = \frac{1}{N_P} \int v(t) dt \quad (flux in the core is calculated by Faraday's Law)$$

$$= \frac{1}{N_P} \int V_M \sin \omega t dt$$

• By considering the same equation, a 50-Hz transformer may be operated at a 20 % higher voltage on 60-Hz power system if this action does <u>not cause</u> insulation problems.

### Inrush Current Problem

• We know that the flux in the core is determined by the primary voltage of the transformers.

 $\phi_{\max} = \frac{V_{\max}}{\omega N_P}$ 

 $\phi_{\max} = \frac{2V_{\max}}{\omega N_P}$ 

$$\phi(t) = \frac{1}{N_P} \int v(t) \, dt$$

• The phase angle of primary voltage will effect the result of this integral, for example if

$$v(t) = V_M \sin(\omega t + 90^\circ)$$

• Or;

$$v(t) = V_M \sin \omega t$$



• We know that the magnetization current and the maximum flux are related with each other.





## Self-study

• Solve all problems of Chapter 2 from Chapman

### **Review Questions**

- 1) Is the turns ratio of a transformer the same as the ratio of voltages across the transformer? Why or why not?
- 2) Why does the magnetization current impose an upper limit on the voltage applied to a transformer core?
- 3) What components compose the excitation current of a transformer? How are they modeled in the transformer 's equivalent circuit?
- 4) What is the leakage flux in a transformer? Why is it modeled in a transformer equivalent circuit as an inductor?
- 5) List and describe the types of losses that occur in a transformer.
- 6) Why does the power factor of a load affect the voltage regulation of a transformer?
- 7) Why does the short-circuit test essentially show only I<sup>2</sup>R losses and not excitation losses in a transformer?
- 8) Why does the open-circuit test essentially show only excitation losses and not I<sup>2</sup>R losses?
- 9) Why can autotransformers handle more power than conventional transformers of the same size?
- 10) What are the problems associated with the Y Y three-phase transformer connection?
- 11) What types of connections can be used? What are their advantages and disadvantages?
- 12) Can a 60-Hz transformer be operated on a 50-Hz system? What actions are necessary to enable this operation?
- 13) What happens to a transformer when it is first connected to a power line? Can anything be done to mitigate this problem?
- 14) A distribution transformer is rated at 18 kVA, 20,000/480 V, and 60 Hz. Can this transformer safely supply 15 kVA to a 415-V load at 50 Hz? Why or why not?
- 15) Why does one hear a hum when standing near a large power transformer?

### **END OF CHAPTER 2**

### TRANSFORMERS