1

2



Electromechanical Energy Conversion – I

Ву

Prof. Dr. A. Mete VURAL mvural@gantep.edu.tr

CHAPTER 4

DC MOTORS AND GENERATORS

3

Introduction

- DC generators are DC machines that convert mechanical energy to DC electric energy.
- DC motors are DC machines that convert DC electric energy to mechanical energy.
- The difference between a DC motor and a DC generator is the direction of power flow.



Speed Regulation

- DC motors are often compared by their speed regulations.
- Speed regulation is a measure of a DC motor that shows how the speed of the motor <u>drops</u> as the load is increased.
- Speed regulation (SR) of a motor is defined by



 w_{nl} is the no-load speed of the motor in **rad/s** w_{fl} is the full-load (*rated load*) speed of the motor in **rad/s** n_{nl} is the no-load speed of the motor in **rev/min** n_{fl} is the full-load (*rated load*) speed of the motor in **rev/min**

Types of DC Motors

- DC motors are driven from a DC power supply.
- Unless otherwise specified, the input voltage to a DC motor is assumed to be <u>constant</u>, because that
 assumption simplifies the analysis of motors and makes the comparison easy between different types of DC
 motors.
- There are five major types of DC motors in general use:
 - Separately excited DC motor
 - Shunt DC motor
 - Permanent-magnet DC motor
 - Series DC motor
 - Compounded DC motor
 - Cumulatively compounded DC motor
 - Differentially compounded DC motor
- Each of these types will be analyzed in detail in this Chapter.

6



The Equivalent Circuit of a DC Motor

• The internal generated voltage (armature voltage) of a DC machine is given by the equation

$$E_A = K\phi\omega$$

• The induced torque developed by the DC machine is given by

$$\tau_{\rm ind} = K\phi I_A$$

where;

K is the machine constant \emptyset is the flux generated in the stator by either field circuit or permanent magnets in Wb **w** is the speed of the rotor (or *shaft*) in rad/s I_A is the armature current in Amperes (A)

The Magnetization Curve of a DC Machine

• How is the internal generated voltage (armature voltage) related to the field current I_F in the machine?



To get the **maximum possible power** per pound of weight out of a machine, most motors and generators are designed to operate **near the saturation point** on the magnetization curve (*at the knee of the curve*).

This implies that a fairly large increase in field current is often necessary to get a small increase in E_A when operation is near full load.

9

The magnetization curve of a dc machine expressed as a plot of E_A versus I_F for a fixed speed of w_0 or n_0



Shunt DC Motor A shunt DC motor is a motor whose field circuit gets its power directly across the armature terminals. ٠ The analysis principles of a separately excited DC motor and shunt DC motor is same. ٠ Lumped $V_T = E_A + I_A R_A$ together and called RF $I_I = I_A + I_F$ V_{T} L Single DC power supply Field circuit Armature terminals 11

Terminal Characteristic of a Shunt DC Motor

- A terminal characteristic of a machine is a plot of the machine's output quantities versus each other.
- For a motor, the output quantities are output (shaft) torque and speed.
- So, the terminal characteristic of a motor is a plot of its output torque versus speed.

• How does a shunt DC motor respond to a load?

- Suppose that the **load** on the shaft of a shunt DC motor is **increased**.
- Then the load torque "*Tload*" will exceed the induced torque "*Tind*" in the machine, and the motor will start to slow down.
- > When the motor slows down, its internal generated voltage drops ($E_A = K \emptyset w$).
- > So the **armature current** in the motor $I_A = (V_T E_A)/R_A$ increases.
- > As the armature current rises, the induced torque in the motor increases (Tind = $K \phi I_A$)
- > Finally the induced torque will be equal the load torque at a lower mechanical speed of rotation.

13

Terminal Characteristic of a Shunt DC Motor

- The output characteristic of a shunt DC motor can be derived from the induced voltage and torque equations of the motor and Kirchhoff's Voltage Law (KVL).
- KVL equation for a shunt DC motor is

$$V_T = E_A + I_A R_A$$

- Since,
 - $E_A = K\phi\omega$

 $V_T = K\phi\omega + I_A R_A$

• Since,

τ.



Terminal Characteristic of a Shunt DC Motor under Armature Reaction

- If a motor has armature reaction, then when the load increases, the flux-weakening effects reduce its flux.
- When the flux reduces, the speed of the motor increases. (See the speed equation given below)
- The terminal characteristic of a shunt DC motor with armature reaction is shown in the figure.

$$\emptyset / \qquad \longrightarrow \qquad \int \omega = \frac{V_T}{K\phi} - \frac{R_A}{(K\phi)^2} \tau_{\text{ind}}$$

 If a motor has <u>compensating windings</u>, there will be no fluxweakening problems in the machine, and the flux in the machine will be <u>constant</u> (*independent of load*). So the terminal characteristic becomes <u>linear</u> (See the figure)



Example:

A **50-hp**, **250-V**, **1200 r/min** dc shunt motor **with compensating windings (armature reaction is ignored)** has an armature resistance (*including the brushes, compensating windings, and interpoles*) of **0.06** Ω . Its field circuit has a total resistance Radj + RF of **50** Ω , which produces a **no-load speed** of **1200 r/min**. There are **1200 turns per pole** on the shunt field winding (*See the figure*).

(a) Find the speed of this motor when its input current is 100 A.(b) Find the speed of this motor when its input current is 200 A.(c) Find the speed of this motor when its input current is 300 A.

(d) Plot the **torque-speed characteristic** of this motor.



Example:

(a) If $I_L = 100$ A, then the armature current in the motor is

$$I_A = I_L - I_F = I_L - \frac{v_T}{R_F}$$

= 100 A - $\frac{250 \text{ V}}{50 \Omega}$ = 95 A

..

Therefore, E_A at this load will be

$$E_A = V_T - I_A R_A$$

= 250 V - (95 A)(0.06 \Omega) = 244.3 V

The resulting speed of the motor is

$$n_2 = \frac{E_{A2}}{E_{A1}} n_1 = \frac{244.3 \text{ V}}{250 \text{ V}} 1200 \text{ r/min} = 1173 \text{ r/min}$$



17

Example:

(b) If $I_L = 200$ A, then the armature current in the motor is

$$I_{\rm A} = 200 \, {\rm A} - \frac{250 \, {\rm V}}{50 \, \Omega} = 195 \, {\rm A}$$

Therefore, E_A at this load will be

$$E_A = V_T - I_A R_A$$

= 250 V - (195 A)(0.06 \Omega) = 238.3 V

The resulting speed of the motor is

$$n_2 = \frac{E_{A2}}{E_{A1}} n_1 = \frac{238.3 \text{ V}}{250 \text{ V}} 1200 \text{ r/min} = 1144 \text{ r/min}$$



Example:

(c) If $I_L = 300$ A, then the armature current in the motor is

$$I_A = I_L - I_F = I_L - \frac{v_T}{R_F} = 300 \text{ A} - \frac{250 \text{ V}}{50 \Omega} = 295 \text{ A}$$

.,

Therefore, E_A at this load will be

$$E_A = V_T - I_A R_A$$

= 250 V - (295 A)(0.06 \OM2) = 232.3 V

The resulting speed of the motor is

$$n_2 = \frac{E_{A2}}{E_{A1}} n_1 = \frac{232.3 \text{ V}}{250 \text{ V}} 1200 \text{ r/min} = 1115 \text{ r/min}$$



19

Example:

(d) To plot the output characteristic of this motor, it is necessary to find the torque corresponding to each value of speed. At no load, the induced torque τ_{ind} is clearly zero. The induced torque for any other load can be found from the fact that power converted in a dc motor is

$$\begin{split} & \left[\frac{P_{conv} = E_A I_A}{P_{out}} \right] \\ \text{From this equation, the induced torque in a motor is} \\ & \pi_{ind} = \frac{E_A I_A}{\omega} \\ \text{Therefore, the induced torque when } I_L = 100 \text{ A is} \\ & \pi_{ind} = \frac{(244.3 \text{ V})(95 \text{ A})}{(1173 \text{ r}/min)(1 \text{ min}/60s)(2\pi \text{ rad}/r)} = 190 \text{ N} \cdot \text{m} \\ \text{The induced torque when } I_L = 200 \text{ A is} \\ & \pi_{ind} = \frac{(238.3 \text{ V})(95 \text{ A})}{(1144 \text{ r}/min)(1 \text{ min}/60s)(2\pi \text{ rad}/r)} = 388 \text{ N} \cdot \text{m} \\ \text{The induced torque when } I_L = 300 \text{ A is} \\ & \pi_{ind} = \frac{(232.3 \text{ V})(295 \text{ A})}{(1115 \text{ r}/min)(1 \text{ min}/60s)(2\pi \text{ rad}/r)} = 587 \text{ N} \cdot \text{m} \\ \end{split}$$



Nonlinear Analysis of a Shunt DC Motor

- The relationship between field current (or flux) and internal generated voltage of a DC machine is nonlinear as shown in the figure.
- So the nonlinear magnetization curve should be used in the analysis of DC machines if accurate solution is expected.



The magnetization curve of a dc machine expressed as a plot of E_A versus I_F for a fixed speed of w_0 or n_0



Example:

A **50-hp**, **250-V**, **1200** r/min dc shunt motor without compensating windings has an armature resistance (including the brushes and interpoles) of **0.06** Ω . Its field circuit has a total resistance RF + Radj of **50** Ω , which produces a **no-load speed of 1200** r/min. There are **1200** turns per pole on the shunt field winding, and the armature reaction produces a demagnetizing magnetomotive force of 840 A.turns at a load current of 200 A. The magnetization curve of this machine is shown in the figure.

(a) Find the speed of this motor when its input current is **200 A**.

(b) This motor is essentially identical to the one in previous example except for the absence of compensating windings. How does its speed compare to that of the previous motor at a load current of **200 A**?

(c) Calculate and plot the **torque-speed characteristic** for this motor.



Solution

(a) If $I_L = 200$ A, then the armature current of the motor is

$$I_A = I_L - I_F = I_L - \frac{V_T}{R_F}$$

= 200 A - $\frac{250 \text{ V}}{50 \Omega}$ = 195 A

Therefore, the internal generated voltage of the machine is

$$E_A = V_T - I_A R_A$$

= 250 V - (195 A)(0.06 \OMeta) = 238.3 V

At $I_L = 200$ A, the demagnetizing magnetomotive force due to armature reaction is 840 A • turns, so the effective shunt field current of the motor is

$$I_F^* = I_F - \frac{\mathcal{Y}_{AR}}{N_F}$$
(9-12)
= 5.0 A - $\frac{840 \text{ A} \cdot \text{turns}}{1200 \text{ turns}} = 4.3 \text{ A}$

From the magnetization curve, this effective field current would produce an internal generated voltage E_{A0} of 233 V at a speed n_0 of 1200 r/min.

We know that the internal generated voltage E_{A0} would be 233 V at a speed of 1200 r/min. Since the actual internal generated voltage E_A is 238.3 V, the actual operating speed of the motor must be

$$\frac{E_A}{E_{A0}} = \frac{n}{n_0}$$
(9-13)

$$n = \frac{E_A}{E_{A0}} n_0 = \frac{238.3 \text{ V}}{233 \text{ V}} (1200 \text{ r/min}) = 1227 \text{ r/min}$$



Example:

(b) At 200 A of load in Example 9-1, the motor's speed was n = 1144 r/min. In this example, the motor's speed is 1227 r/min. Notice that the speed of the motor with armature reaction is higher than the speed of the motor with no armature reaction. This relative increase in speed is due to the flux weakening in the machine with armature reaction.



<section-header><text><list-item><list-item><list-item><list-item><text>

Adjusting Field Resistance:

- If the field resistance is <u>increased</u>, then the field current <u>decreases</u>
- When the field current <u>decreases</u>, the flux of the machine also <u>decreases</u>
- A <u>decrease</u> in flux causes an <u>instantaneous decrease</u> in the internal generated voltage (E_A=KØw), which causes an <u>increase</u> in the machine's armature current:

$$I_A \uparrow = \frac{V_T - E_A \downarrow}{R_A}$$



Speed Control Of Shunt DC Motor

Adjusting Field Resistance:

• However, the induced torque is given as:

$$\tau_{\rm ind} = K \phi I_A$$

• So does induced torque increase or decrease ?

?
$$\int \tau_{ind} = K\phi I_A \int$$
 Armature current increases
Flux decreases







Adjusting Field Resistance:

- When the induced torque begins to increase, it becomes greater than the load torque (Tind > Tload) and the motor speeds up.
- However, as the motor speeds up, the internal generated voltage EA rises, causing armature current to fall.

$$\int I_A = \frac{V_T - E_A}{R_A}$$

- As armature current <u>falls</u>, the induced torque <u>falls</u> too, and finally induced torque again <u>equals</u> load torque but at a <u>higher</u> steady-state speed than the case <u>before</u> increasing field resistance.
- Naturally, decreasing field resistance would reverse the whole process, and the speed of the motor would drop

$R_F \uparrow speed \uparrow$	$R_F / speed /$	
		33



Adjusting Armature Voltage:

- In this method, the armature voltage is changed.
- But, field voltage is constant (not changed). •



Speed Control Of Shunt DC Motor

Adjusting Armature Voltage:

If armature voltage is increased, then the armature current increases:

$$[I_A = (V_A \uparrow - E_A)/R_A]$$

As armature current increases, then induced torque increases:

$$au_{\mathrm{ind}} = K \phi I_A \uparrow$$

- When induced torque becomes greater than load torque, then motor speed increases: •
- But, as the motor speed (w) increases, the internal generated voltage increases:

$$\int E_A(=K\phi\omega\uparrow).$$

When the internal generated voltage increases, then armature current decreases:

$$I_A [= (V_A - E_A)/R_A]$$

When the armature current decreases, then the induced torque decreases until (Tind=Tload) at a higher speed: $/\tau_{\rm ind} = K \phi I_A /$

Adjusting Armature Voltage:



The effect of armature voltage speed control on torque-speed characteristic of a separately excited DC motor.

Speed Control Of Shunt DC Motor

Inserting A Resistor In Series With The Armature Circuit:

If a resistor (R_{extra}) is inserted <u>in series</u> with the armature circuit, armature current <u>decreases</u>:

$$\oint I_A = \frac{V_A - E_A}{R_A + R_{extra}}$$

• When the armature current decreases, then the induced torque decreases:

$$/\tau_{\rm ind} = K \phi I_A /$$

- When the induced torque decreases, then the speed of the motor decreases.
- But when the speed <u>decreases</u>, then the internal generated voltage <u>decreases</u>:

 $\int E_A (= K\phi\omega)$

When the internal generated voltage <u>decreases</u>, the armature current <u>increases</u>:

$$\int I_A = \frac{V_A - E_A}{R_A + R_{extra}}$$

38

Inserting A Resistor In Series With The Armature Circuit:

- Now, the armature current is both decreasing and increasing; so which one is dominant over the other one?
- The decreasing effect is more stronger than the other and hence the motor slows down after adding resistance.
- However, this speed control method is not very effective.
- Because, the loss in the inserted resistor is very large.
- For this reason, <u>this method is rarely used</u>.



Speed Control Of Shunt DC Motor ٠ Can we use two methods together? Adjusting field resistance is very effective for the speeds which are higher than base speed of the motor. Adjusting armature voltage is very effective for the speeds which are lower than base speed of the motor. **Adjusting Field Resistance:** $R_{adj(min)} \leq R_{adj} \leq R_{adj(max)}$ We cannot increase • If $R_{adj} = R_{adj(min)} \implies I_F = I_{F(max)} \implies \emptyset = \emptyset_{(max)} \implies w = w_{(min)}$ field current so much because field windings can be **damaged** There is **no problem** • If $R_{adj} = R_{adj(max)} \implies I_F = I_{F(min)} \implies \emptyset = \emptyset_{(min)} \implies w = w_{(max)}$ here because, field current can be **CONCLUSION** Adjusting field resistance is very effective to decreased safely. increase motor speed (higher than rated speed) ! 40



- By combining these two speed-control techniques, it is possible to get a very wide range of speed variations for a motor.
- These two speed-control techniques can be successfully applied to both shunt and separately excited DC motors.







Series DC Motor

- A series DC motor is a DC motor whose field windings is connected in series with the armature circuit.
- The series field winding generally consists of a relatively <u>few turns</u>.
- The important feature of the series DC motor is that the flux is directly proportional to the armature current.
- The equivalent circuit of a series DC motor is shown in the figure.



Series DC Motor

• The Kirchhoff's Voltage Law equation for a series DC motor is given as:

$$V_T = E_A + I_A(R_A + R_S)$$

• The induced torque in a series DC motor is given as:

$$\tau_{\rm ind} = K\phi I_A$$

• The flux in this machine is directly proportional to its armature current until saturation;

$$\phi = cI_A$$

• So the induced torque can be written as:

$$\tau_{\rm ind} = K\phi I_A = KcI_A^2$$

• The result is that the torque in the motor is proportional to the square of its armature current

47

Series DC Motor

$\tau_{\rm ind} = K\phi I_A = KcI_A^2$

- As a result of the above relationship, we understand that a **series DC motor** gives **more torque per ampere** than any other DC motor.
- Therefore series DC motors are used in applications requiring very high torques.
- Examples of such applications are the **starter motors** in cars, elevator motors, tractor motors in locomotives, cranes, and forklifts.



Source: https://www.quora.com/



4KW 48V Series Wound DC Traction Electric Motor

Series DC Motor	Place of Origin: Motor: Size & Diameter:	Shandong, China Brush 170mm-242mm	a (Mainland)) Br Vo Ex	and Name: oltage: scited Type:	SU ver	PER ious ries or separately	N C	Model Number: Certification: nsulation Class:	ZC4-48 CE F
	Duty System: Use:	S2-60min Electric Car)	Pr	otection Class:	IP2	20	I	Гуре:	DC Mo
	Mode	Rated Power (Kw	Rated Volt (V)	Rated Am (A)	p Rated Speed (r/min)	Duty	Protection Class			
	ZC2.2-4	8 2.2	48	57	2000			IP First number - Protection aga		ainst
	ZC2.2-4	8 2.2	48	57	2500			sonu objects		
	ZC2.2-4	8 2.2	48	57	2800			 0 - No specia 1 - Protected 	against solid objects up	to 50 mm,
	ZC2.2-6	0 2.2	60	46	3300			e.g. accidenta	al touch by persons hand	ds.
	ZC3-48	3	48	78	1500			 z - Protected e.g. persons f 	against solid objects up Ingers,	to 12 mm,
	ZC3-48	3	48	78	2000		/	 3 – Protected 	against solid objects ov	er 2.5 mm
supernotor enalibaba com	ZC3-48	3	48	78	2500			(tools and wir • 4 - Protected	res). against solid objects ow	er 1 mm
	ZC3-48	3	48	78	2800			(tools, wires,	and small wires).	
	ZC3-48	3	48	78	3200			 5 – Protected 	against dust limited ing	ress (no
	ZC3-48	3	48	78	3500			6 – Totally pro	otected against dust.	
	ZC3-60	3	60	63	2000	S2	₩			
	ZC3-60	3	60	63	2800	60min	IP20	IP Second r	number – Protectio	n agains
	ZC3-60	3	60	63	3500		× .	liquids		
	ZC3-72	3	72	52	3500			 U - No protection 1 - Protection 	ection. on against vertically fall	ing drops o
	ZC3.5-4	8 3.5	48	91	2800			water e.g. o	ondensation.	
	ZC3.5-6	0 3.5	60	73	2800			 2 - Protectle to 15a from 	on against direct sprays the vertical	of water u
	ZC3.5-	2 3.5	72	61	2800			 3 - Protecte 	ed against direct sprays	of water u
	ZC4-48	4	48	104	1500			to 60o from	the vertical.	
	ZC4-48	4	48	104	2000			 4 - Protections - 	on against water spraye limited ingress permitt	ed from all red.
	ZC4-48	4	48	104	2500			 5 - Protecte 	ed against low pressure	ets of wat
	ZC4-48	4	48	104	2800			from all dire	ections - limited ingress	à.
	ZC4-48	4	48	104	3200					
	ZC4-48	4	48	104	3500				4	8

<section-header><text><list-item><list-item><equation-block><equation-block><text><equation-block><text>

Terminal Characteristic of a Series DC Motor

• Also, we remember that the armature voltage equation is

$$E_A = K\phi\omega.$$

• Substituting the last two equations into the KVL equation yields:

$$V_T = E_A + I_A(R_A + R_S)$$
$$E_A = K\phi\omega \quad I_A = \sqrt{\frac{\tau_{\text{ind}}}{Kc}}$$

$$V_T = K\phi\omega + \sqrt{\frac{\tau_{\rm ind}}{Kc}}(R_A + R_S)$$

• If the flux is eliminated from the above equation then the terminal characteristic equation can be derived.

Terminal Characteristic of a Series DC Motor

Notice that

$$I_A = \frac{\phi}{c}$$

• And the induced torque equation can be rewritten as

 $\tau_{\text{ind}} = K\phi I_A \longrightarrow \tau_{\text{ind}} = \frac{K}{c}\phi^2$

• Therefore, the **flux** in the motor can be rewritten as

$$\phi = \sqrt{\frac{c}{K}} \sqrt{\tau_{\text{ind}}}$$

• Substituting this **flux equation** into the following equation:

Terminal Characteristic of a Series DC Motor

$$V_T = K \sqrt{\frac{c}{K}} \sqrt{\tau_{\text{ind}}} \omega + \sqrt{\frac{\tau_{\text{ind}}}{Kc}} (R_A + R_S)$$

• If the above equation is solved for **speed (w)**:

$$\begin{split} \sqrt{Kc} \ \sqrt{\tau_{\text{ind}}} \omega \ &= \ V_T \ - \ \frac{R_A \ + \ R_S}{\sqrt{Kc}} \ \sqrt{\tau_{\text{ind}}} \\ \omega \ &= \ \frac{V_T}{\sqrt{Kc} \ \sqrt{\tau_{\text{ind}}}} \ - \ \frac{R_A \ + \ R_S}{Kc} \end{split}$$

 The resulting torque-speed relationship of a series DC motor is given as:

$$\omega = \frac{V_T}{\sqrt{Kc}} \frac{1}{\sqrt{\tau_{ind}}} - \frac{R_A + R_S}{Kc}$$



52

Example:

Example: The figure shows a **250-V series dc motor** with compensating windings and a total series resistance **RA** + **Rs of 0.08** Ω . The series field consists of **25 turns per pole**, with the magnetization curve also shown.

(a) Find the speed and induced torque of this motor for when its armature current is **50 A**.

(b) Calculate and plot the torque-speed characteristic for this motor.



The equivalent circuit of a series dc motor







Compounded DC Motor

- A compounded DC motor is a DC motor with both a shunt and a series field windings as shown in figure.
- We can say that a **compounded DC motor** is the <u>combination</u> of both a shunt DC motor and a series DC motor.
- The **dots** that appear on the two field coils have the <u>same meaning</u> as the dots on a **transformer**:
- Current flowing into a dot produces a positive MMF.
- If current flows into the dots on both field coils, the two MMFs are <u>added</u> to produce a larger total MMF.
- This situation is known as "cumulative compounding".
- This type of motors are called as "Cumulatively Compounded DC Motors".



Compounded DC Motor

- Current leaving a dot produces a negative MMF.
- If one current flows into the dot on one field coil and the other current leaves a dot on the other field coil, the resulting MMF is obtained by subtracting one MMF from the other.
- This situation is known as "differential compounding".
- This type of motors are called as "Differentially Compounded DC Motors".



Compounded DC Motor

• The Kirchhoff's Voltage Law equation for a compounded DC motor is given as:

$$V_T = E_A + I_A(R_A + R_S)$$

• The currents in the **compounded DC motor** are shown to be:

$$I_A = I_L - I_F$$
$$I_F = \frac{V_T}{R_F}$$

• The net MMF and the effective shunt field current in the compounded DC motor are given by

$$\mathcal{F}_{net} = \mathcal{F}_F \pm \mathcal{F}_{SE} - \mathcal{F}_{AR}$$
• Positive sign is associated with a
cumulatively compounded DC motor
• Negative sign is associated with a
differentially compounded DC motor

Torque-Speed Characteristic of a <u>Cumulatively</u> Compounded DC Motor

- The cumulatively compounded DC motor has a higher starting torque than a shunt DC motor:
- Because, there is more flux in a compounded DC motor during starting.
- Since both shunt and series field windings generate MMF with the same polarity and they are added
- This is an advantage of the compounded DC motor over shunt DC motor during starting.



Torque-Speed Characteristic of a <u>Cumulatively</u> Compounded DC Motor

- The cumulatively compounded DC motor combines the advantages of shunt and series DC motors.
- At **light loads**, the series field has a very small effect, so the motor behaves <u>approximately</u> as a shunt DC motor.
- As the load gets very large, the series flux becomes quite important and the torque-speed curve begins to look like a series DC motor's characteristic.
- Cumulatively compounded DC motor has generally <u>higher</u> torque than a shunt DC motor.
- The shunt filed winding in the cumulatively compounded DC motor allows to make the speed control possible.



The torque-speed characteristic of a cumulatively compounded DC motor compared to series and shunt motors with the same full-load rating

Torque-Speed Characteristic of a <u>Differentially</u> Compounded DC Motor

- In a differentially compounded DC motor, the shunt MMF and series MMF force <u>subtract</u> from each other.
- This means that as the load on the motor <u>increases</u>, armature current <u>increases</u> and the flux in the motor <u>decreases</u>.
- But as the flux <u>decreases</u>, the speed of the motor <u>increases</u>.
- This speed <u>increase</u> causes another increase in load, which further <u>increases</u> armature current, further <u>decreasing</u> the flux, and <u>increasing</u> the speed again.
- The result is that differentially compounded DC motor becomes <u>unstable</u> and tends to run away
- Because of this situation, differentially compounded DC motor is <u>unsuitable</u> for any application.



Self-study

• Solve Example 9.6 at page 571 from Chapman

Speed Control in the <u>Cumulative</u> Motor	ely Compounded DC	
 The techniques available for the control of speed in a cumu same as those available for a shunt DC motor. There are three speed control methods (two common method) 	latively compounded DC motor are the Is and one less common method):	
 Adjusting the field resistance R_F (and thus the field flux) Adjusting the armature voltage V_T 	common methods	
3) Inserting a resistor in series with the armature circuit	Less common method	
		63

DC Motor Starters

- In order for a **DC motor** to function properly on the job, it must have **some special control and protection equipment** associated with it. The purposes of this equipment are:
 - > To **protect** the motor against damage due to **<u>short circuits</u>** in the equipment.
 - > To protect the motor against damage from long-term overloads.
 - > To protect the motor against damage from excessive starting currents.
 - > To provide a convenient manner in which to control the operating speed of the motor.

DC Motor Starters

- At starting conditions, the DC motor is not turning, and so armature voltage (EA) is ZERO.
- Since the internal resistance of a DC motor is generally very low, a very high current flows during starting.
- DC motor starters are used to limit the very high starting current of DC motors.

For example, for a **50-hp** motor if **RA=0.06** Ω and **VT=250V**:

I_{starting} = (VT-EA) / RA = (250V-0V) / 0.06 = 4167 A

I_{rated} = (50*746)/250 = <u>149.2</u>

Then; $\frac{I_{starting}}{I_{rated}} \approx 28$

65

DC Motor Starters

 A solution to the problem of excess current during starting is to insert a starting resistor in series with the armature to limit the current flow until the motor reaches rated operating conditions.



Self-study

• Solve Example 9.7 at page 575 from Chapman

Introduction to DC Generators

- DC generators are DC machines used as generators.
- There is no real difference between a generator and a motor except for the direction of power flow.
- There are <u>five major</u> types of DC generators, classified according to the manner in which their field flux is produced:

Separately excited DC generator:

The field flux is derived from a separate power source independent of the generator itself.

> Shunt DC generator:

The field flux is derived by connecting the field circuit directly across the terminals of the generator.

Series DC generator:

The field flux is produced by connecting the field circuit in series with the armature of the generator.

Cumulatively compounded DC generator:

Both a shunt and a series field are present, and their effects are additive.

Differentially compounded DC generator:

Both a shunt and a series fie ld are present, but their effects are subtractive.

68

Introduction to DC Generators

- DC generators are quite rare in modern power systems.
- Even for DC power systems such as those in automobiles now use AC generators plus rectifiers to produce DC power.



Introduction to DC Generators

- The terminal characteristics of DC generators is the plot of output voltage versus output current.
- So, DC generators are compared by their terminal characteristics, power ratings, efficiencies and voltage regulations.
- Voltage regulation (VR) of a DC generator is defined as:

$$VR = \frac{V_{\rm nl} - V_{\rm fl}}{V_{\rm fl}} \times 100\%$$

 V_{nl} is the **no-load** terminal voltage of the DC generator V_{fl} is the **full-load** (*rated-load*) terminal voltage of the DC generator

- A positive voltage regulation means a drooping terminal characteristic
- A Negative voltage regulation means a <u>rising</u> terminal characteristic







Control of Terminal Voltage of a Separately Excited DC Generator

 Since armature resistance (RA) is <u>constant</u> and the armature current (IA) is dependent on the magnitude of the load on the generator, we need to control armature voltage (EA) in order to control the terminal voltage (VT) of a separately excited DC generator:



75

Nonlinear Analysis of a Separately Excited DC Generator

- Nonlinear analysis covers (as in case of DC motors)
 - > The magnetization curve (non-linear relationship between armature voltage (EA) and field current (IF))
 - In addition, if a machine has armature reaction, its flux will be reduced with each increase in load, causing armature voltage (EA) to decrease.
- The only way to accurately <u>determine the output voltage</u> in a DC generator <u>with armature reaction</u> is to make graphical analysis.
- The total MMF in a separately excited DC generator with armature reaction is given as:

$$\mathcal{F}_{net} = N_F I_F - \mathcal{F}_{AR}$$

• If the above equation is divided to **NF** for both sides:

$$I_F^* = I_F - \frac{\mathscr{F}_{AR}}{N_F}$$

Nonlinear Analysis of a Separately Excited DC Generator

Example:



Nonlinear Analysis of a Separately Excited DC Generator

Example:

- (a) If the variable resistor R_{adj} in this generator's field circuit is adjusted to 63 Ω and the generator's prime mover is driving it at 1600 r/min, what is this generator's no-load terminal voltage?
- (b) What would its voltage be if a 360-A load were connected to its terminals? Assume that the generator has compensating windings.
- (c) What would its voltage be if a 360-A load were connected to its terminals but the generator does not have compensating windings? Assume that its armature reaction at this load is 450 A • turns.
- (d) What adjustment could be made to the generator to restore its terminal voltage to the value found in part a?
- (e) How much field current would be needed to restore the terminal voltage to its no-load value? (Assume that the machine has compensating windings.) What is the required value for the resistor $R_{\rm adj}$ to accomplish this?

Nonlinear Analysis of a Separately Excited DC Generator

Example:

Solution

(a) If the generator's total field circuit resistance is

$$R_F + R_{adj} = 83 \Omega$$

then the field current in the machine is

$$I_F = \frac{V_F}{R_F} = \frac{430 \text{ V}}{83 \Omega} = 5.2 \text{ A}$$

From the machine's magnetization curve, this much current would produce a voltage $E_{A0} = 430$ V at a speed of 1800 r/min. Since this generator is actually turning at $n_m = 1600$ r/min, its internal generated voltage E_A will be

$$\frac{E_A}{E_{A0}} = \frac{n}{n_0}$$
(9-13)

The magnetization curve for the generator in Example 9-9.

$$E_A = \frac{1600 \text{ r/min}}{1800 \text{ r/min}} 430 \text{ V} = 382 \text{ V}$$

Since $V_T = E_A$ at no-load conditions, the output voltage of the generator is $V_T = 382$ V.

78

Nonlinear Analysis of a Separately Excited DC Generator

Example:

(b) If a 360-A load were connected to this generator's terminals, the terminal voltage of the generator would be

 $V_T = E_A - I_A R_A = 382 \text{ V} - (360 \text{ A})(0.05 \Omega) = 364 \text{ V}$

(c) If a 360-A load were connected to this generator's terminals and the generator had 450 A • turns of armature reaction, the effective field current would be

$$I_F^* = I_F - \frac{\mathscr{P}_{AR}}{N_F} = 5.2 \text{ A} - \frac{450 \text{ A} \cdot \text{turns}}{1000 \text{ turns}} = 4.75 \text{ A}$$

From the magnetization curve, $E_{A0} = 410$ V, so the internal generated voltage at 1600 r/min would be

$$\frac{E_A}{E_{A0}} = \frac{n}{n_0}$$
(9-13)
$$E_A = \frac{1600 \text{ s/min}}{1800 \text{ s/min}} 410 \text{ V} = 364 \text{ V}$$

Therefore, the terminal voltage of the generator would be

$$V_T = E_A - I_A R_A = 364 \text{ V} - (360 \text{ A})(0.05 \Omega) = 346 \text{ V}$$

It is lower than before due to the armature reaction.

Nonlinear Analysis of a Separately Excited DC Generator

Example:

- (d) The voltage at the terminals of the generator has fallen, so to restore it to its original value, the voltage of the generator must be increased. This requires an increase in E_A , which implies that $R_{\rm adj}$ must be decreased to increase the field current of the generator.
- (e) For the terminal voltage to go back up to 382 V, the required value of E_A is

$$E_A = V_T + I_A R_A = 382 \text{ V} + (360 \text{ A})(0.05 \Omega) = 400 \text{ V}$$

To get a voltage E_A of 400 V at $n_a = 1600$ r/min, the equivalent voltage at 1800 r/min would be

$$\frac{E_A}{E_{A0}} = \frac{n}{n_0}$$
(9-13)
$$E_{A0} = \frac{1800 \text{ r/min}}{1600 \text{ r/min}} 400 \text{ V} = 450 \text{ V}$$

From the magnetization curve, this voltage would require a field current of $I_F = 6.15$ A. The field circuit resistance would have to be

$$R_{F} + R_{adj} = \frac{V_{F}}{I_{F}}$$

20 \Omega + R_{adj} = \frac{430 V}{6.15 A} = 69.9 \Omega
R_{adj} = 49.9 \Omega \approx 50 \Omega

80

Shunt DC Generator

- A shunt DC generator is a DC generator that supplies its own field current by having its field connected <u>directly across the terminals</u> of the machine.
- Shunt DC generator has an advantage over the separately excited DC generator in that no external power supply is required for the field circuit.
- But there is a question: If the generator supplies its own field current, how does it get the initial field flux to start when it is <u>first</u> turned on?



The simplified equivalent circuit of a shunt DC generator

Voltage Buildup Mechanism in a Shunt DC Generator

- The voltage buildup in a DC generator depends on the presence of a residual flux (Ø_{res}) in the poles of the generator.
- When a generator <u>first</u> starts to turn, an internal voltage will be generated by means of residual flux:

 $E_A = K\phi_{\rm res}\omega$

(This voltage is normally very small 1-2 Volt)

- If residual flux <u>does not exist</u> in the DC generator than we have to disconnect the field from the armature circuit and connect it directly to an external DC power source such as a <u>battery</u>.
- This method is known as "flashing the field".



Terminal Characteristic of a Shunt DC Generator ٠ The terminal characteristic of a shunt DC generator differs from that of a separately excited DC generator, because the amount of field current in the machine depends on its terminal voltage. V_T Assume that we start the DC machine without any load. ٠ Now as the load on the generator is increased, line The simplified equivalent circuit of a shunt DC generator current and armature current increases: $V_T = E_A - R_A I_A$ LOAD $R_A I_A$ I_A As VT decreases, field current and hence flux also decreases The decrease in flux decreases armature voltage EA 83 and hence VT is again decreased by flux reduction.



Voltage Control for a Shunt DC Generator

 The voltage control technique of a shunt DC generator is <u>same</u> as that of a separately excited DC generator in principle.



The Series DC Generator

- A series DC generator is a DC generator whose field is connected in series with its armature.
- Since the armature has much higher current than that of shunt field, the series field circuit will have <u>only a very</u> few turns of wire to generate a sufficient amount of MMF = Ns*Is.
- The wire in series field circuit will be much thicker than the wire in a shunt field circuit because of high current.



The simplified equivalent circuit of a series DC generator

The Terminal Characteristic of a Series DC Generator

- At No-load, there is no line current and hence no field current; as a result armature voltage will be very small (Because of any residual flux)
- As the load is <u>increased</u>, line current and hence field current <u>rises</u>, so armature voltage <u>rises rapidly</u>.
- Armature voltage is always greater than terminal voltage because of the voltage drop → (RA + Rs).IA.
- After a while, the machine approaches saturation, and armature voltage becomes <u>approximately constant</u>.
- After the saturation point, voltage drop effect becomes <u>very strong</u> and the terminal voltage <u>drops</u> <u>very fast</u>.



Terminal characteristic for a series DC generator



87

The Terminal Characteristic of a Series DC Generator

- If armature reaction is <u>active</u> in the series DC generator, a too much increase in load will greatly <u>reduce</u> the terminal voltage, even approaching to <u>zero very fast</u>.
- Series DC generators are used <u>only</u> in a few specialized applications, such as arc welding.
- In arc welding, a <u>large</u> armature reaction is required as the one shown in the figure.
- Notice that when the welding electrodes <u>make contact</u> with each other before welding begins, a very large current flows.
- As the operator <u>separates</u> the welding electrodes, there is a very steep rise in the generator 's voltage, while the current remains high. This voltage ensures that <u>a welding arc is</u> <u>maintained</u> through the air between the electrodes.



A series DC generator terminal characteristic with large armature reaction effects



The Cumulatively Compounded DC Generator

• A cumulatively compounded DC generator is a DC generator with both series and shunt fields, connected so that the MMF from the two fields are <u>added</u> with each other.



The equivalent circuit of a cumulatively compounded DC generator with a **long-shunt connection**

The **dots** that appear on the two field coils have the same meaning as the dots on a transformer: Current flowing into a dot produces a **positive magnetomotive force**.

Long-shunt connection means that the shunt field winding is connected in parallel to the series combination of armature and the series field winding.



The Terminal Characteristic of a Cumulatively Compounded DC Generator

- Suppose that the load on the cumulatively compounded DC generator is increased.
- Then as the load <u>increases</u>, the load (line) current and armature current increases too.
- As armature current increases the voltage drop also increases and hence terminal voltage decreases:

 $V_{T} = E_{A} - I_{A}(R_{A} + R_{S})$ (long-shunt connection)

or $V_T = E_A - R_S I_A - R_S I_L$

 $R_{S}I_{A} - R_{S}I_{L}$ (short-shunt connection)

Also as the armature current and load current increases, the MMF of the series winding also increases:



The equivalent circuit of a cumulatively compounded DC generator with a long-shunt connection



The equivalent circuit of a cumulatively compounded DC generator with a short-shunt connection

- The <u>increase</u> in MMF of series winding <u>increases</u> the total MMF in the machine and hence EA <u>increases</u>.
- As EA increases, terminal voltage tends to increase as well.

The Terminal Characteristic of a Cumulatively Compounded DC Generator

So which effect is more stronger than another ?



- The answer depends on how much is the MMF of the series field winding strong or the number of turns (N_{se}) in the series field winding !
- <u>Three cases</u> will be considered:
 - UNDER-COMPOUNDED CASE: N_{SE} is small (There are a few number of turns in series field winding)
 - FLAT-COMPOUNDED CASE: N_{SE} is larger (There are more number of turns in series field winding)
 - OVER-COMPOUNDED CASE: N_{SE} is much larger (There are much more number of turns in series field winding)









The Differentially Compounded DC Generator

- A differentially compounded DC generator is a DC generator with both shunt and series fields, but this time their MMFs <u>subtract</u> from each other.
- Like the cumulatively compounded DC generator, the differentially compounded DC generator can be connected in either long-shunt or short-shunt fashion.



The Terminal Characteristic of a Differentially Compounded DC Generator

- In the differentially compounded DC generator, the voltage drop and flux-strengthening effect were both present in the machine as in case of cumulatively compounded DC generator.
- But these two effects act in the same direction.
 - As armature current (or LOAD) increases, voltage drop increases as well. This will tend to decrease terminal voltage.



As armature current increases, the series MMF reduces the total MMF in the generator.

$$(\tilde{\mathscr{F}}_{tot} = N_F I_F - N_{SE} I_A \uparrow),$$

> A <u>decrease</u> in total MMF and hence total flux, <u>decreases</u> also terminal voltage. F_{TOT} V_T



Self-study

• Solve all problems of Chapter 4 from Chapman

Review Questions

- 1) What is the speed regulation of a dc motor?
- 2) How can the speed of a shunt dc motor be controlled? Explain in detail.
- 3) What is the practical difference between a separately excited and a shunt dc motor?
- 4) What effect does armature reaction have on the torque-speed characteristic of a shunt dc motor? Can the effects of armature reaction be serious? What can be done to remedy this problem?
- 5) What are the desirable characteristics of the permanent magnets in PMDC machines?
- 6) What are the principal characteristics of a series dc motor? What are its uses?
- 7) What are the characteristics of a cumulatively compounded dc motor?
- 8) What are the problems associated with a differentially compounded dc motor?
- 9) What happens in a shunt dc motor if its field circuit opens while it is running?
- 10) Why is a starting resistor used in dc motor circuits?
- 11) How can a dc starting resistor be cut out of a motor's armature circuit at just the right time during starting?
- 12) What is the purpose of a field loss relay?
- 13) What types of protective features are included in typical solid-state dc motor drives? How do they work?
- 14) How can the direction of rotation of a separately excited dc motor be reversed?
- 15) How can the direction of rotation of a shunt dc motor be reversed?
- 16) How can the direction of rotation of a series dc motor be re versed?
- 17) Name and describe the features of the five types of generators covered in this chapter.
- 18) How does the voltage buildup occur in a shunt dc generator during starting?
- 19) What could cause voltage buildup on starting to fail to occur? How can this problem be remedied?
- 20) How does armature react ion affect the output voltage in a separate ly excited dc generator?
- 21) What causes the extraordinarily fast voltage drop with increasing load in a differentially compounded dc generator?

