



EEE 322

Electromechanical Energy Conversion – II

Prepared By

Dr. A.Mete VURAL

Given By

Dr. Ali Osman ARSLAN

aoarslan@gantep.edu.tr

CHAPTER 2

SYNCHRONOUS GENERATORS

Synchronous Generators

Synchronous generators (*alternators*) are synchronous machines used to convert mechanical power to AC electric power.



The rotor is being replaced inside the stator of a large synchronous generator in a hydro power plant

Synchronous Generators



The rotor is being replaced inside the stator of a large synchronous generator in a hydro power plant



Operation principle of synchronous generator


- A **DC current** is applied to the **rotor winding** which produces a **rotor magnetic field**.
- The rotor of the generator is then **turned** by a **prime mover**, producing a **rotating magnetic field** within the machine.
- This **rotating magnetic field** induces a **three-phase set of voltages** at the stator windings of the generator.



Reference: <https://www.youtube.com/watch?v=tiKH48EMgKE>

Field winding vs armature winding

- *Two terms* commonly used to describe the windings on a synchronous machine: **field windings** and **armature windings**
- The "**field windings**" is the winding that produces the **main magnetic field** in the synchronous machine
- For **synchronous machines**, the **field windings** are on the **rotor**
- The "**armature windings**" is the winding where **the three-phase set of voltages** are induced
- For **synchronous machines**, the **armature windings** are on the **stator**

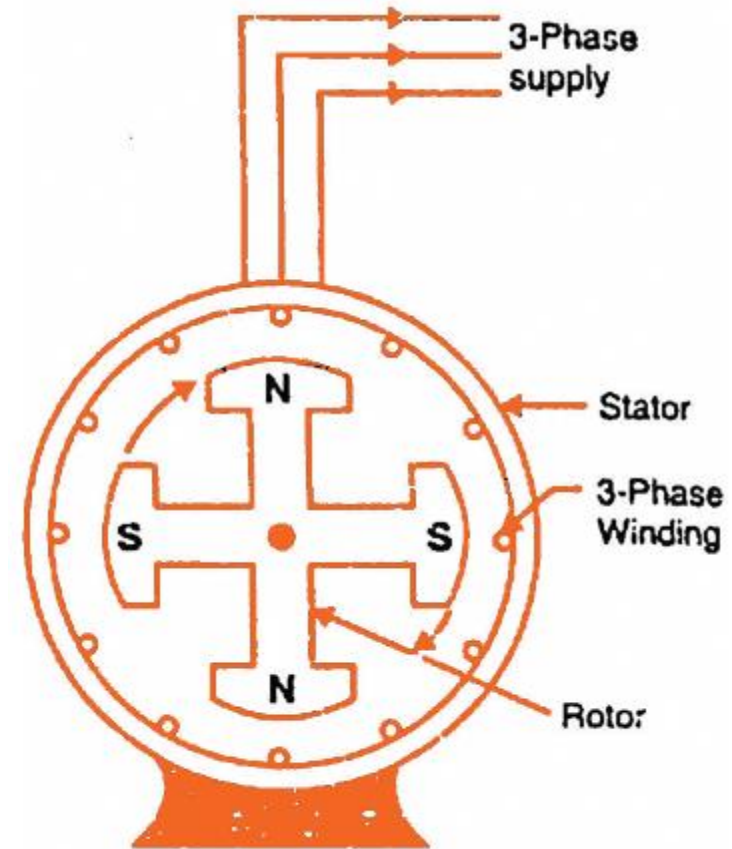

Reference: <http://www.studyelectrical.com>

Rotor types of synchronous generator

- There **two types of rotors** in synchronous generators and motors
 - ✓ Cylindrical rotor (*non-salient rotor*)
 - ✓ Salient-pole rotor



Cylindrical rotor

- **Cylindrical rotors** are generally designed for **high speed rotation**, such as in steam turbines
- Because of high rotor speed, the pole number can be kept small
- Pole number is generally **2 or 4**

$$n_m = \frac{120f_e}{P}$$

If $f_e = 50$ Hz;

$$120 \times 50 = 6000 = n_m P$$

↑ higher

↓ lower

Rotor types of synchronous generator

- There **two types of rotors** in synchronous generators and motors
 - ✓ Cylindrical rotor (*non-salient rotor*)
 - ✓ Salient-pole rotor



Salient-pole rotor

- **Salient-pole** rotors are generally designed for **low speed rotation**, such as in hydro turbines
- Because of low rotor speed, the pole number should be increased
- Pole number is generally **4 or more**

$$n_m = \frac{120f_e}{P}$$

If $f_e = 50$ Hz;

$$120 \times 50 = 6000 = n_m P$$



↑ higher

↓ lower

How DC current is supplied to rotor ?

- There are **two common approaches** to supplying DC current to the rotor (*field winding*)

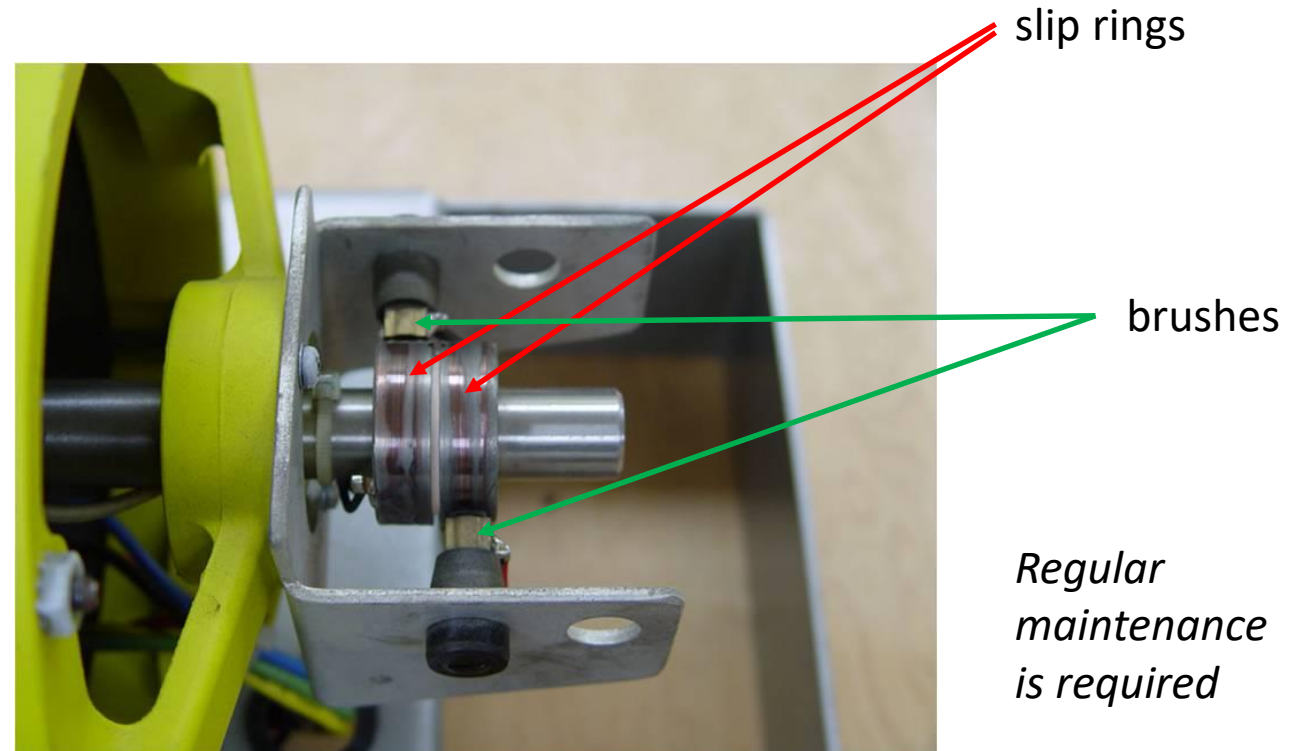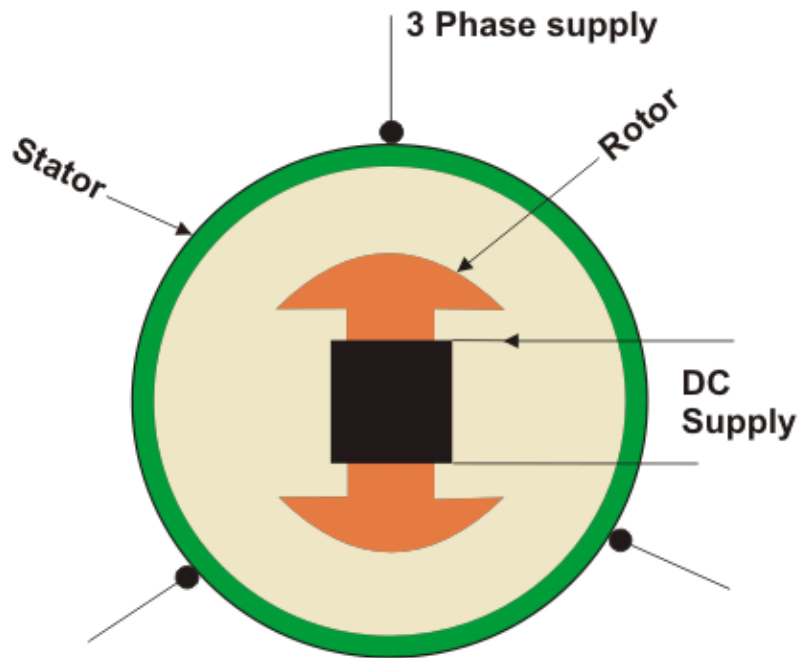
First method: Supply the DC current from an **external DC source** to the rotor by means of *slip rings* and *brushes* (*suitable for smaller generators*)



How DC current is supplied to rotor ?


- There are **two common approaches** to supplying DC current to the rotor (*field winding*)

Second method: Supply the DC current from a **special DC power source** mounted directly on the shaft of the synchronous generator (**Brushless exciter for larger generators**)

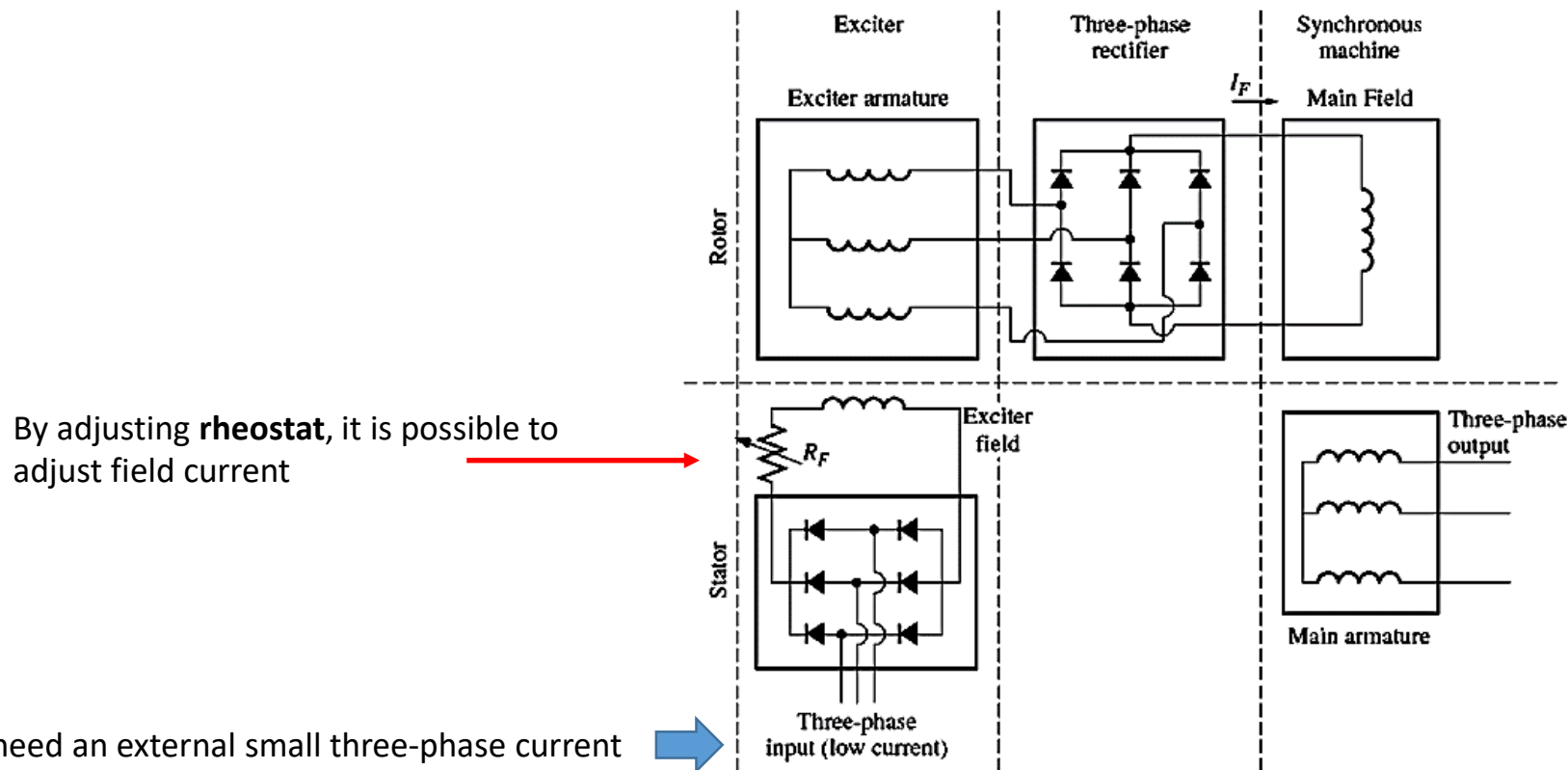

Option 1

How DC current is supplied to rotor ?

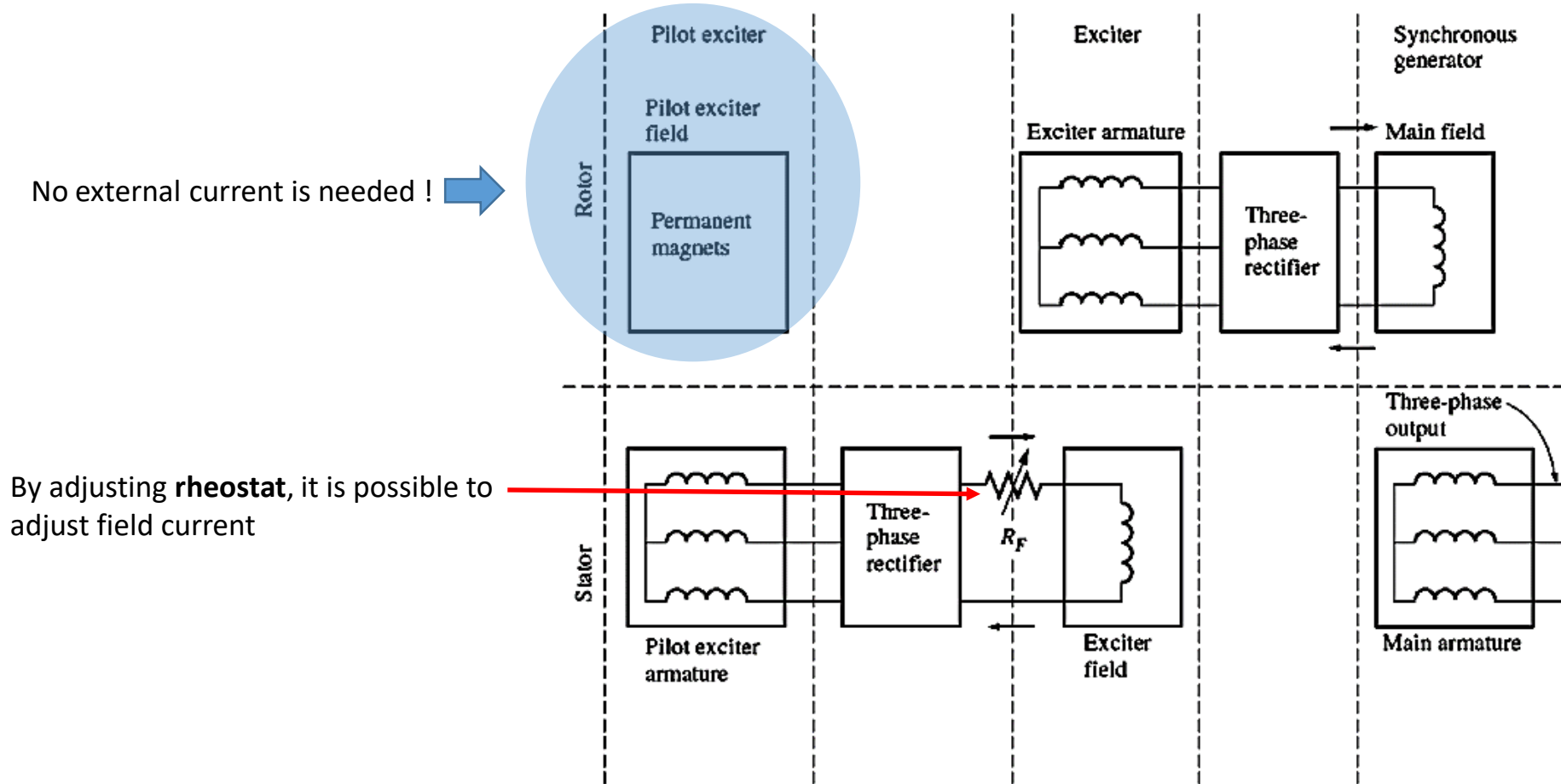

Option 2

Speed of rotation of a synchronous generator

- **Synchronous generators** are by definition *synchronous*, meaning that the electrical frequency produced in the stator is *locked* or *synchronized* with the mechanical rate of rotation of the generator.
- In another words, the speed of rotating magnetic field and mechanical rate of rotation are **equal**
- However, **asynchronous generators** are by definition *asynchronous*, meaning that there is **always a difference** between the speed of rotating magnetic field and mechanical rate of rotation of the generator.

$$f_e = \frac{n_m P}{120}$$

f_e is the electrical frequency in the stator (Hz)

n_m is the mechanical speed of magnetic field rotation (rev/min or rpm)

n_m is also equals to the rotor speed of synchronous machines (also called “*synchronous speed*”)

P is number of poles (always even number)

Internal generated voltage of a syn. generator

- In Chapter 1, we have seen that the magnitude of the induced voltage in a given stator phase is equal to:

$$E_A = \sqrt{2}\pi N_C \Phi f$$

- Let's write this equation in more simpler form:

$$E_A = K\Phi\omega$$



$$K = \frac{\sqrt{2}}{2} N_C \quad (\text{a constant related with the machine})$$

N_C is the number of conductors per phase

- The induced voltage E_A depends on;
 - Flux in the machine
 - Angular speed of rotor
 - A constant related with the machine

Internal generated voltage of a syn. generator

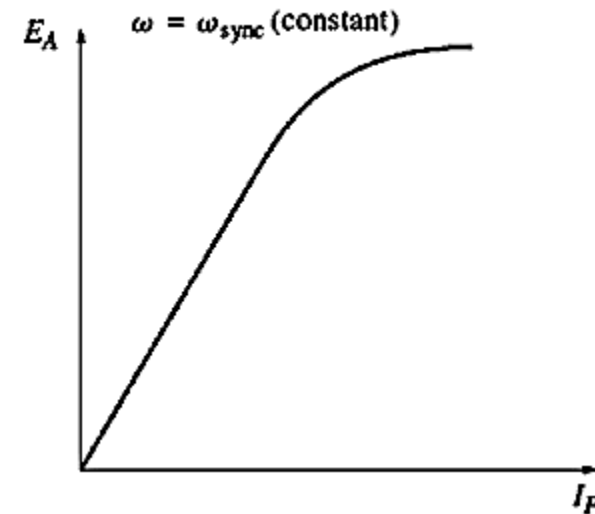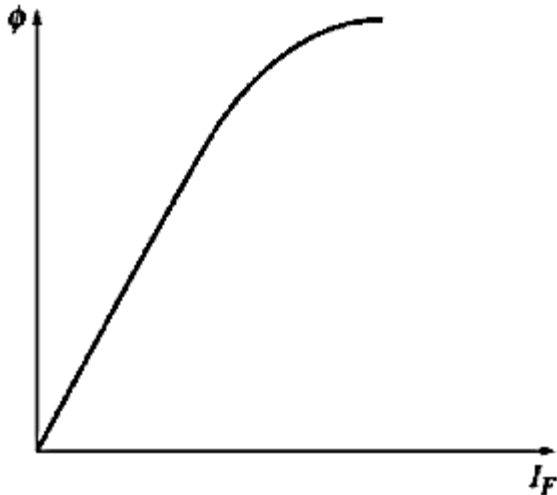
- The field circuit current I_F is related to the flux Φ
- E_A is directly proportional to the flux Φ (if ω is constant)
- So E_A **must be related** to the field current I_F



Magnetization curve (*open-circuit characteristic*) of the synchronous machine


Derivation of equivalent circuit of sync. gen.

- The figure shows a **two-pole rotor** rotating inside a **three-phase stator**
- Now assume that there is **no load** connected to the stator
- The rotor magnetic field B_R produces an **internal generated voltage (E_A)**
- The peak value of E_A (E_{Amax}) coincides with the direction of B_R .
- With **no load** on the generator, there is **no armature current flow**
- E_A will be taken directly from the terminals of the generator
- In this case, phase voltage (V_ϕ) is equal to E_A

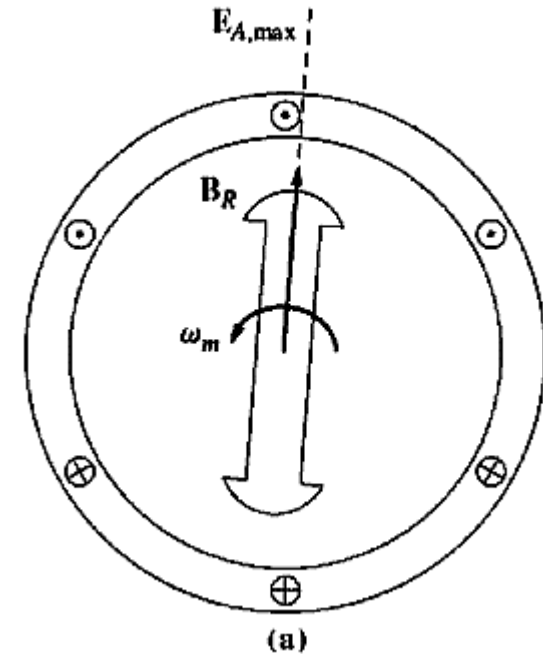


Derivation of equivalent circuit of sync. gen.

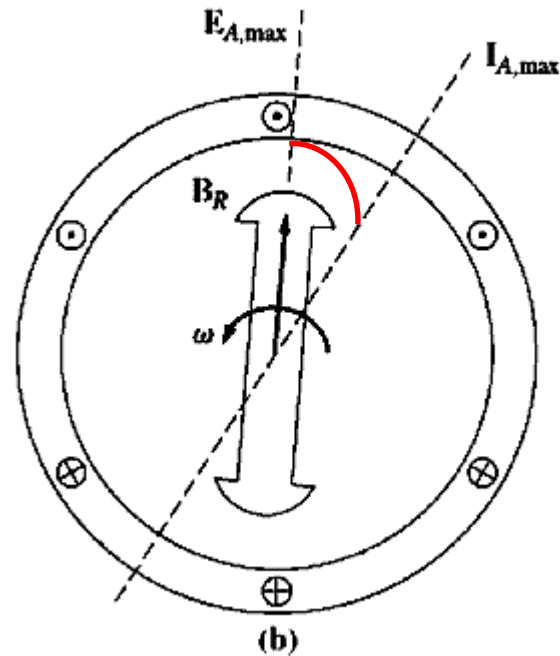- Now suppose that the generator is connected to a **lagging load**
- Since the **load is lagging**, the peak current will occur at an angle **behind** the peak voltage



Derivation of equivalent circuit of sync. gen.

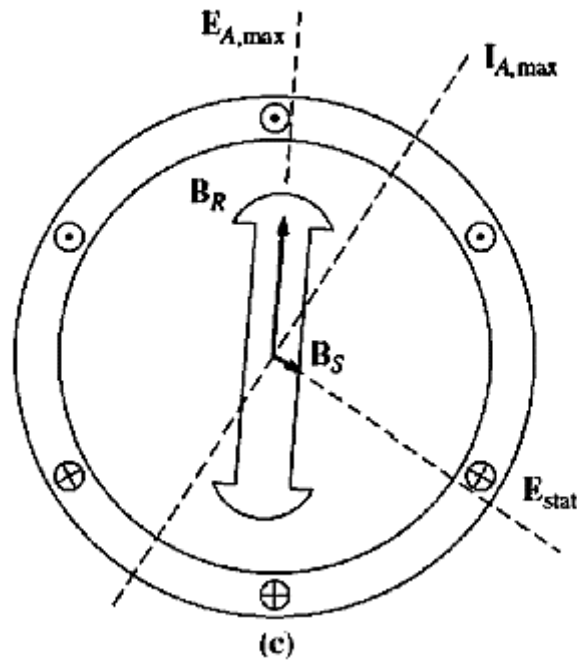- The current flowing in the stator windings produces a magnetic field of its own
- This stator magnetic field is called (B_s)
- The direction of B_s is found by the right hand rule
- The stator magnetic field (B_s) induces a voltage on the stator, called “*armature reaction voltage*” (E_{STAT})



Derivation of equivalent circuit of sync. gen.


- With two voltages present in the stator windings, the phase voltage of the generator becomes the sum of the **internal generated voltage** (E_A) and the **armature reaction voltage** (E_{STAT})

$$V_\phi = E_A + E_{STAT}$$

- On the other hand, the **net magnetic field** in the generator becomes the sum of the rotor and stator magnetic fields


$$B_{net} = B_R + B_S$$

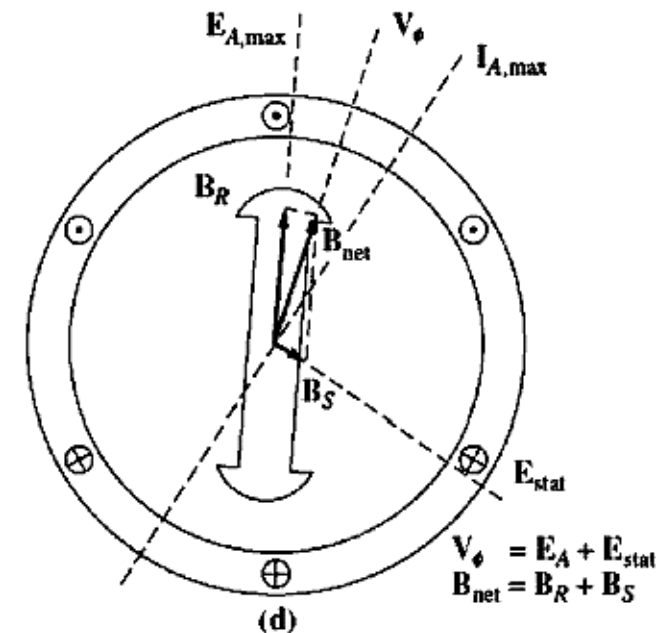- Since the angles of B_R and E_A are the same
- and the angles of B_S and E_{STAT} are the same
- The angles of V_ϕ and B_{net} will be the same



Definition of armature reaction

- When a synchronous generator's rotor is spun (*rotated*), a voltage E_A is induced in stator windings
- If a load (*three phase*) is attached to the terminals of the generator, a three-phase current flows in stator windings
- This three-phase stator current produce a magnetic field (B_S) of its own in the machine.
- The stator magnetic field (B_S) distorts the original rotor magnetic field (B_R)
- This distortion effect is called “**armature reaction**”

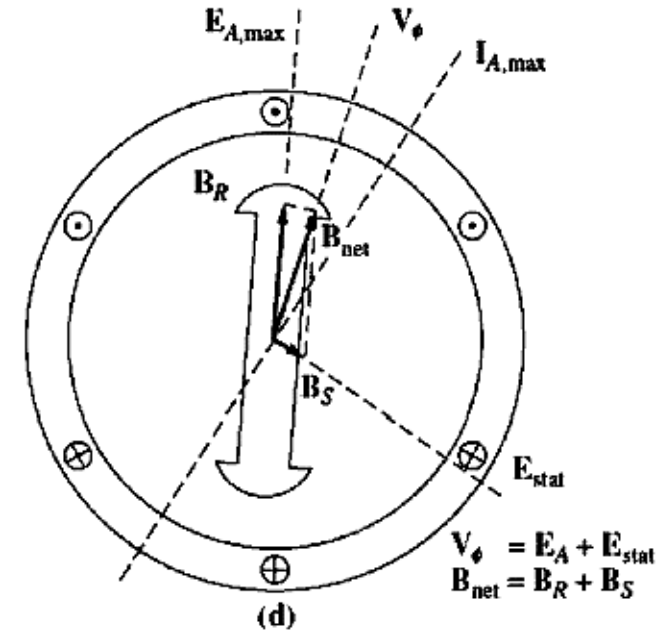


$$\left. \begin{aligned} B_S &= 0 \\ B_{net} &= B_R \\ B_{net} &= B_R + B_S \end{aligned} \right\} \text{(without load)}$$

$$\left. \begin{aligned} B_{net} &\neq B_R \\ B_{net} &= B_R + B_S \end{aligned} \right\} \text{(with load) (armature reaction)}$$

Modeling of armature reaction

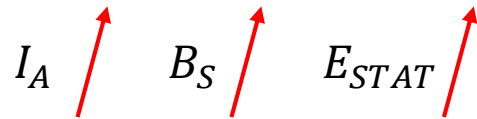- How can the effects of **armature reaction** on the phase voltage be **modeled** ?
- First; the voltage E_{STAT} lies at an **angle of 90° behind** the armature current I_A
- Second; the voltage E_{STAT} is directly proportional to the armature current I_A




- If X is a constant of proportionality (**reactor**), then the **armature reaction voltage** E_{STAT} can be expressed as:

$$E_{STAT} = -jXI_A \quad \rightarrow \quad (-j \text{ means that } E_{STAT} \text{ lags } I_A \text{ by } 90^\circ)$$


- Since;

$$V_\phi = E_A + E_{STAT}$$

$$V_\phi = E_A - jXI_A$$

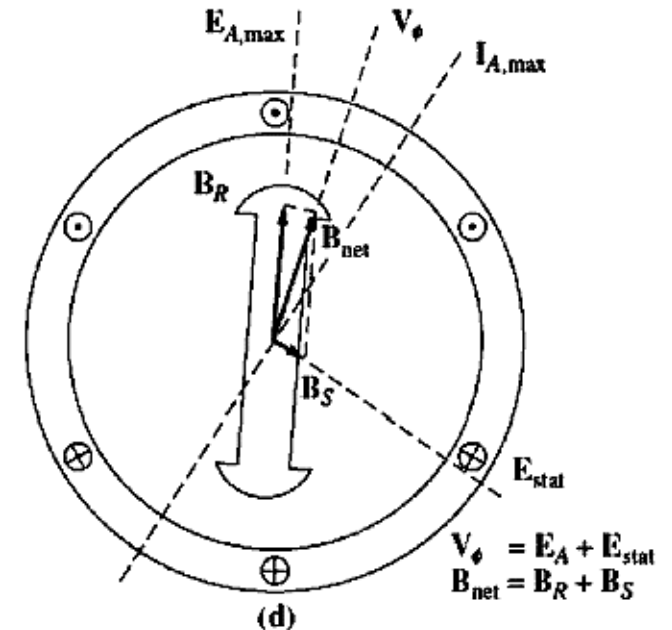

Modeling of armature reaction

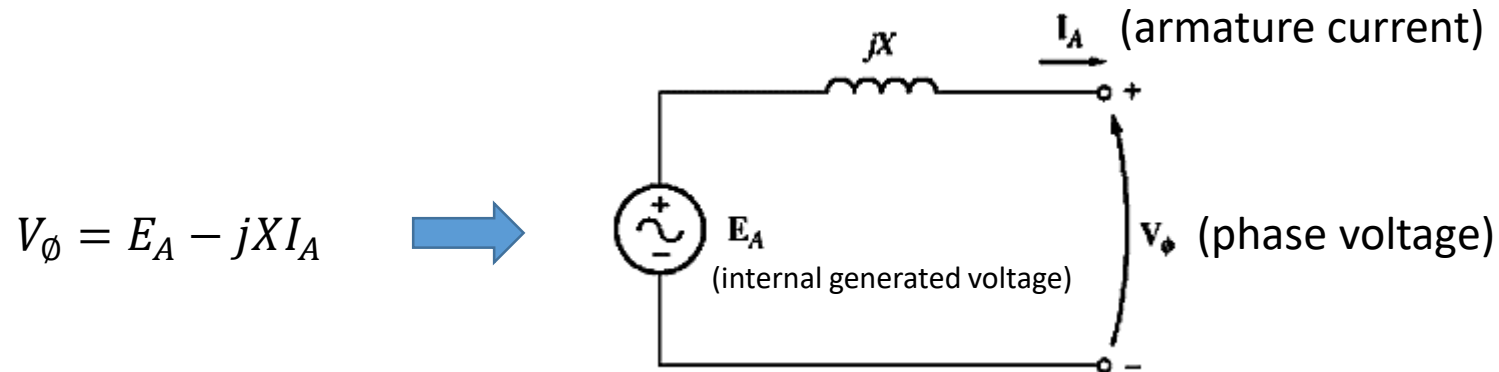

- In addition to armature reaction, the **stator coils** have a **self-inductance (L_A)** and a **resistance (R_A)**
- These parameters can also be used in the mathematical model for more accurate calculations:
- If;

$$X_A = 2\pi f L_A \text{ (armature self-reactance)}$$
$$R_A \text{ (armature resistance)}$$

$$V_{\phi} = E_A - jXI_A - jX_A I_A - R_A I_A$$

Modeling of armature reaction


$$V_\phi = E_A - jXI_A - jX_A I_A - R_A I_A$$

- If we join these two reactances in the last equation:

$$X_S = X + X_A \quad \text{(synchronous reactance)}$$


- The final form of the voltage equation for the stator is obtained as:

$$V_\phi = E_A - jX_S I_A - R_A I_A$$

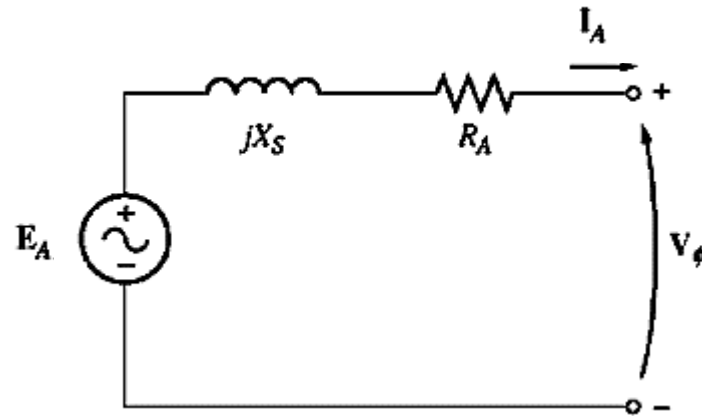

Per-phase equivalent circuit of stator

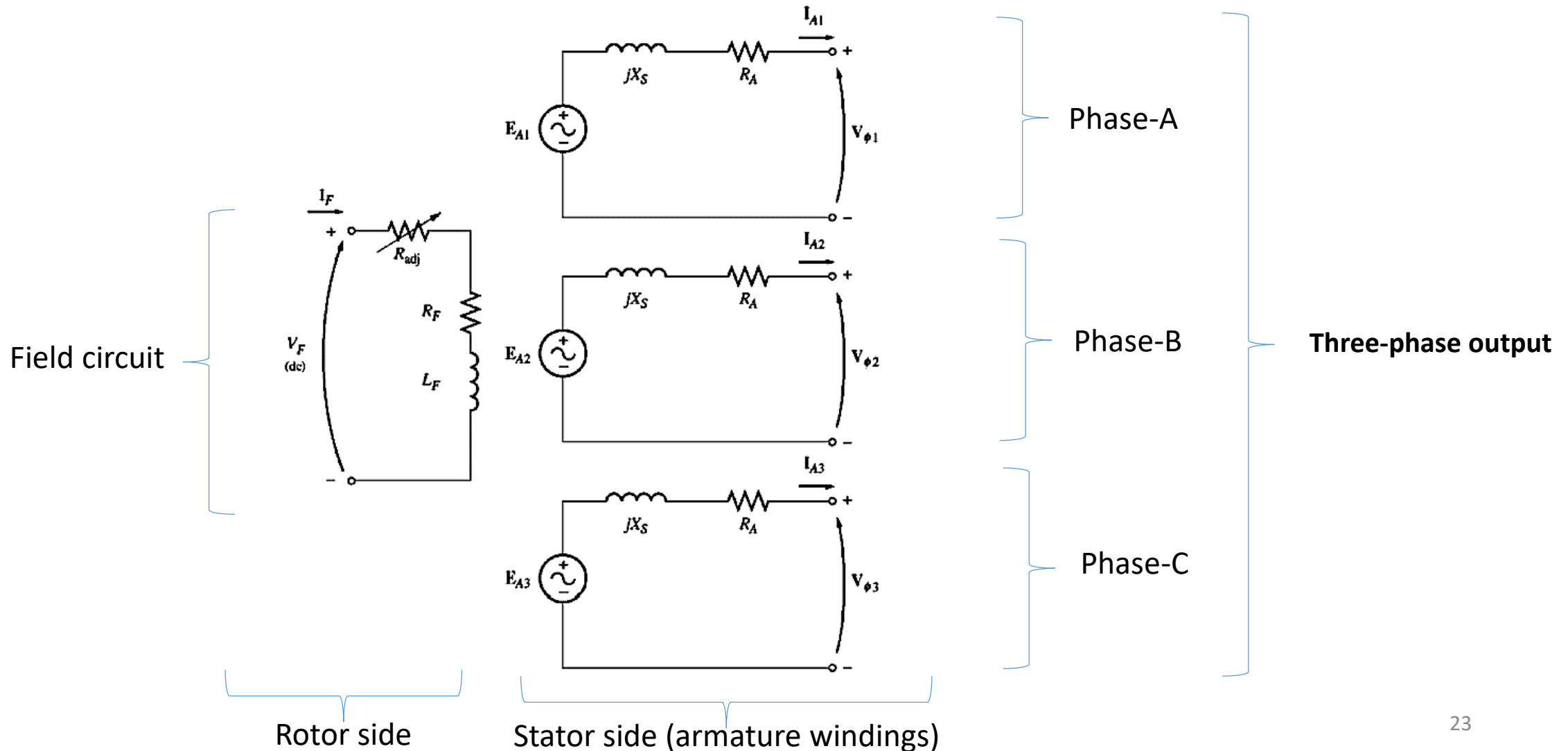Full equivalent circuit of synchronous generator



Full equivalent circuit of synchronous generator

- The stator windings of the generator can be connected as **wye (Y)**:

$$|E_{A1}| = |E_{A2}| = |E_{A3}| = E_A$$

$$|V_{\phi 1}| = |V_{\phi 2}| = |V_{\phi 3}| = V_{\phi}$$

$$|V_{AB}| = |V_{BC}| = |V_{CA}| = V_{LL}$$


$$|I_{A1}| = |I_{A2}| = |I_{A3}| = I_A$$

$$|I_{L1}| = |I_{L2}| = |I_{L3}| = I_L$$

$$V_{LL} = \sqrt{3} \cdot V_{\phi}$$

$$I_L = I_A$$

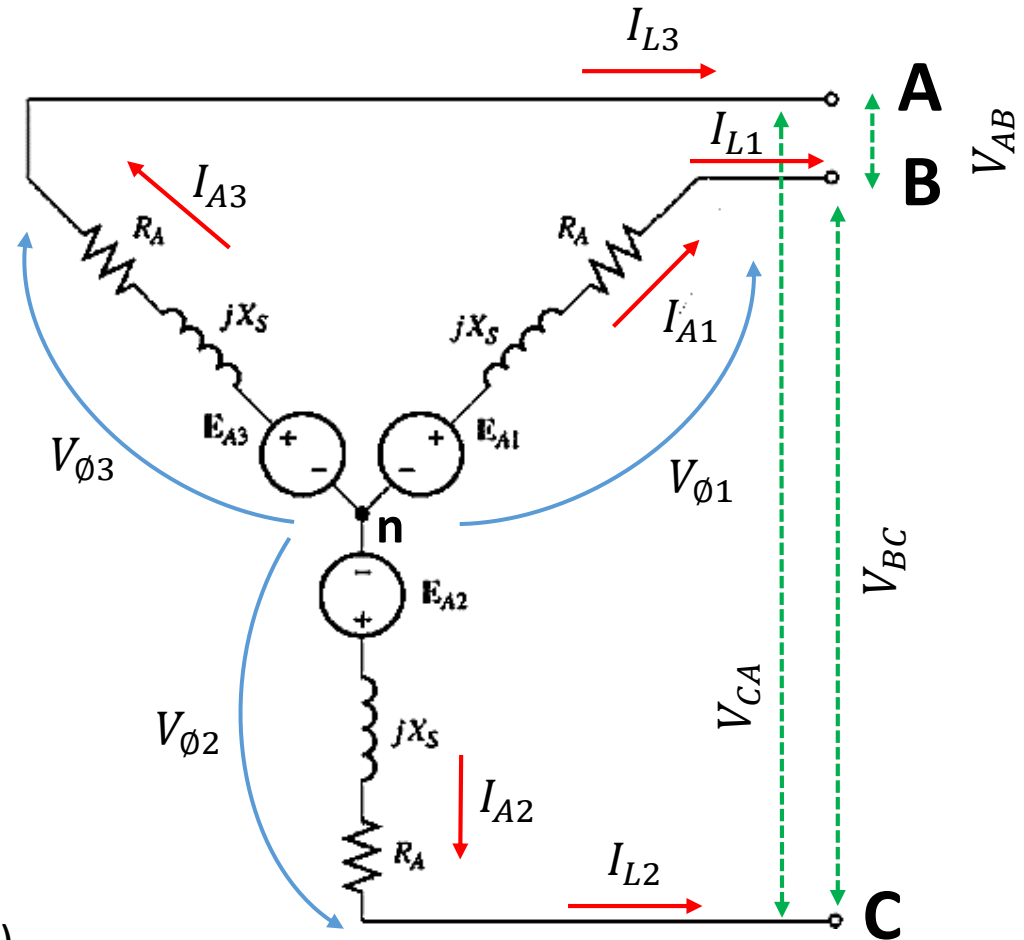Line-to-line voltage (V_{LL}) = line voltage = terminal voltage (V_T)



Equivalent circuit of stator connected in Y

Full equivalent circuit of synchronous generator

- The stator windings of the synchronous generator can be connected as **delta (Δ)**:

$$|E_{A1}| = |E_{A2}| = |E_{A3}| = E_A$$

$$|V_{\phi 1}| = |V_{\phi 2}| = |V_{\phi 3}| = V_{\phi}$$


$$|V_{AB}| = |V_{BC}| = |V_{CA}| = V_{LL}$$

$$|I_{A1}| = |I_{A2}| = |I_{A3}| = I_A$$

$$|I_{L1}| = |I_{L2}| = |I_{L3}| = I_L$$

$$V_{LL} = V_{\phi}$$


$$I_L = \sqrt{3} \cdot I_A$$

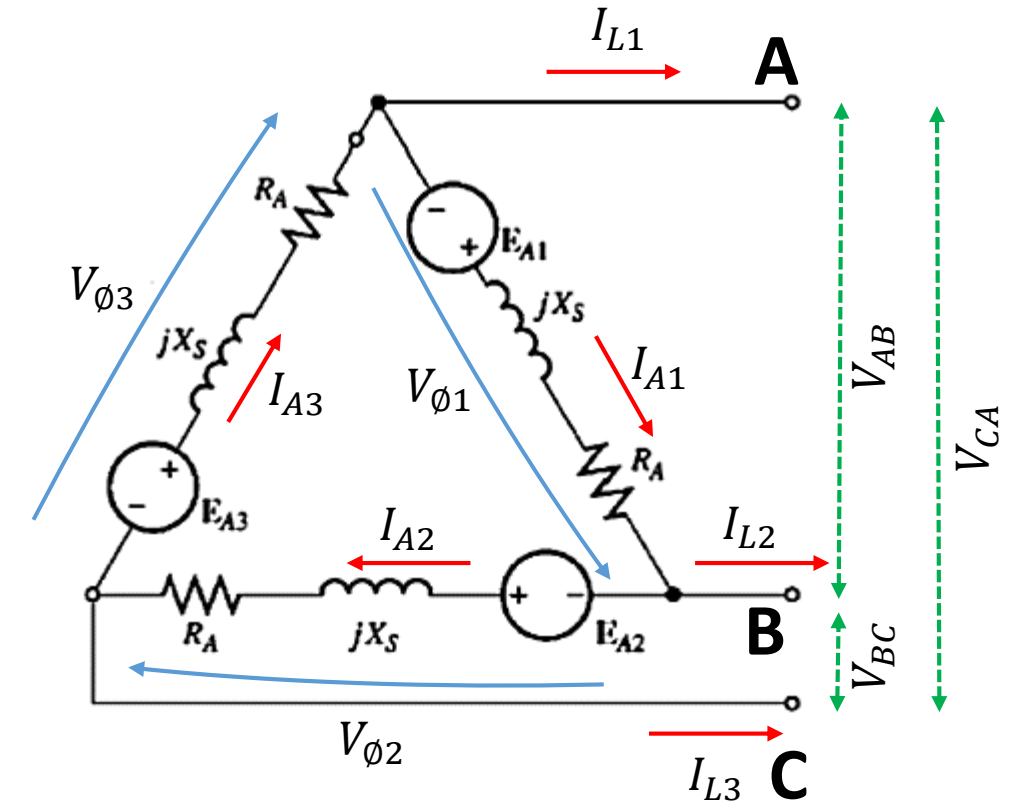

Equivalent circuit of stator connected in Δ

Line-to-line voltage (V_{LL}) = line voltage = terminal voltage (V_T)

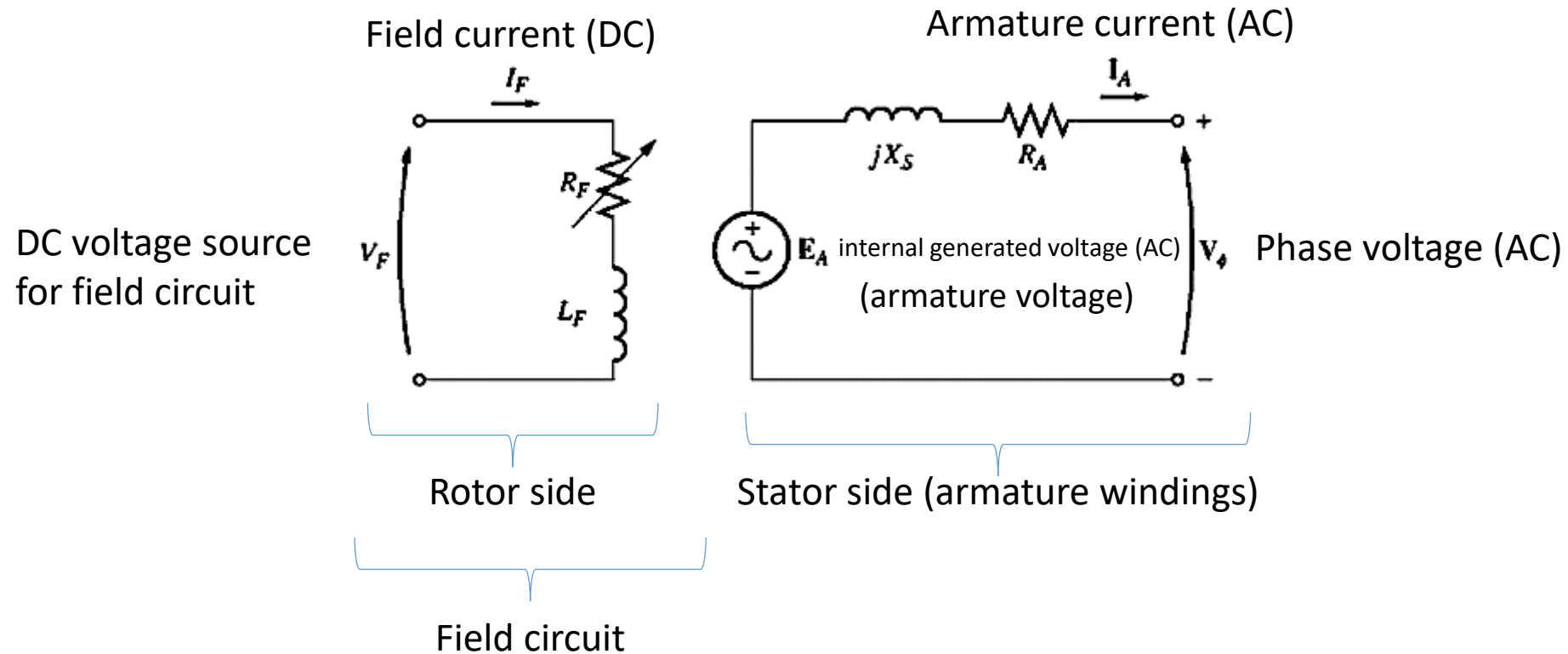
Per-phase equivalent circuit of sync. gen.



NOTE: By changing R_F , we can control the magnitude of E_A




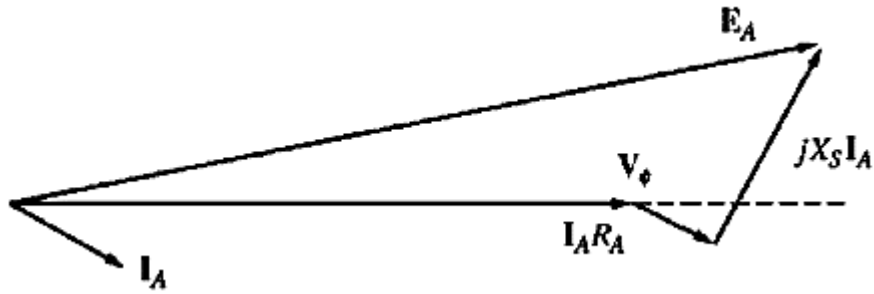Phasor diagram of a synchronous generator




Syn. generator is supplying a **lagging power factor load**
(*inductive load*)

(the most common case)

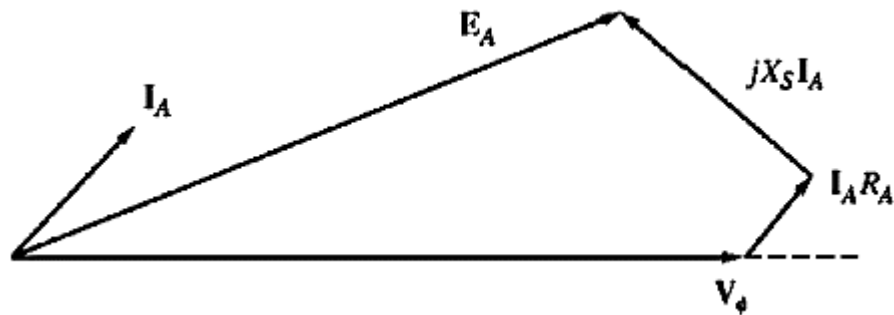

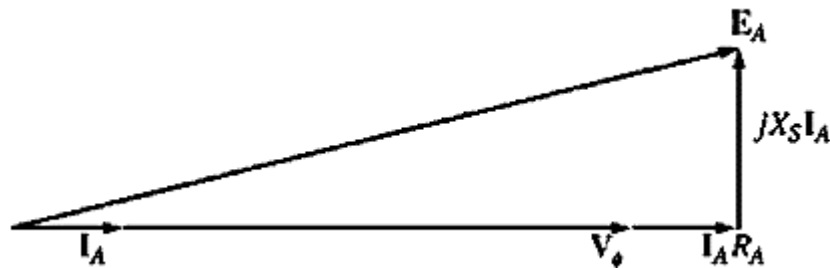Syn. generator is supplying a **leading power factor load**
(*capacitive load*)



Syn. generator is supplying a **unity power factor load**
(*purely resistive load*)

Power and torque in synchronous generators


- A **synchronous generator** is a **synchronous machine** used as a **generator**
- **Synchronous generator** converts **mechanical power** into **three-phase electrical power**
- The **prime mover** is the source of **mechanical power**
- The prime mover can be a “**diesel engine**”, “**steam turbine**”, “**water turbine**”, or any suitable system
- **The rule is that:** The prime mover **speed must be kept constant** in order to generate a **constant frequency of electrical power**

$$f_e = \frac{n_m P}{120}$$



Different types of prime mover

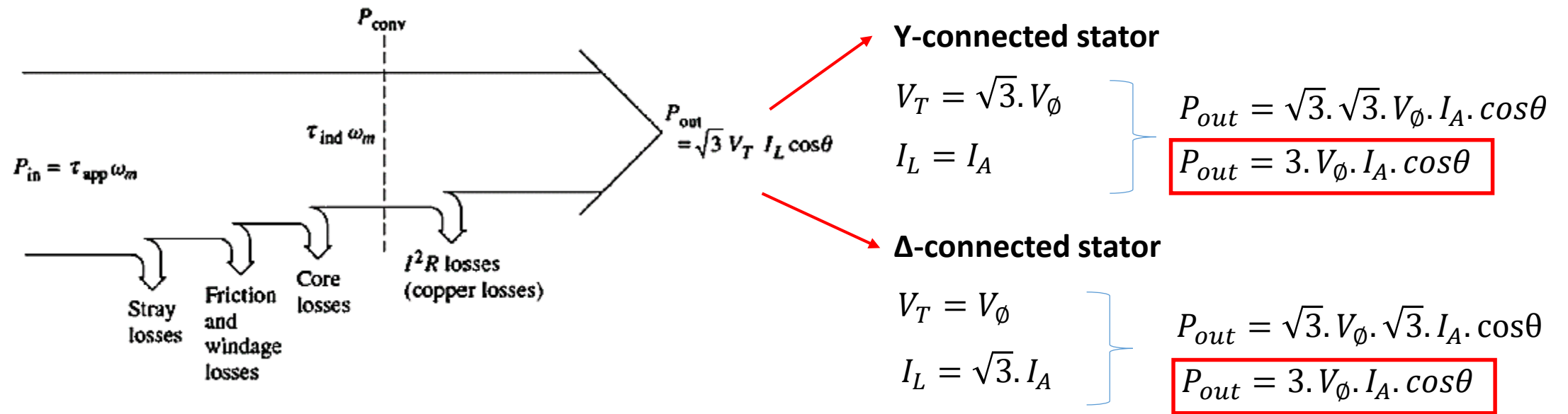Power-flow diagram of a synchronous generator



Power-flow diagram of a synchronous generator

$$P_{out} = \sqrt{3} \cdot V_{\phi} \cdot \sqrt{3} \cdot I_A$$

$$P_{out} = 3 \cdot V_{\phi} \cdot I_A \cdot \cos\theta$$

Three-phase output **active (real)** power of the synchronous generator

The unit is: **W or kW or MW**

$$Q_{out} = \sqrt{3} V_T \cdot I_L \cdot \sin\theta$$

$$Q_{out} = 3 \cdot V_{\phi} \cdot I_A \cdot \sin\theta$$

Three-phase output **reactive** power of the synchronous generator

The unit is: **VAR or kVAR or MVAR**

$$S_{out} = P_{out} + jQ_{out}$$

Three-phase output **complex power** of the synchronous generator

$$|S_{out}| = \sqrt{P_{out}^2 + Q_{out}^2}$$


Three-phase output **apparent power** of the synchronous generator

The unit is: **VA or kVA or MVA**

Y or Δ
connected
stator

Power-flow diagram of a synchronous generator

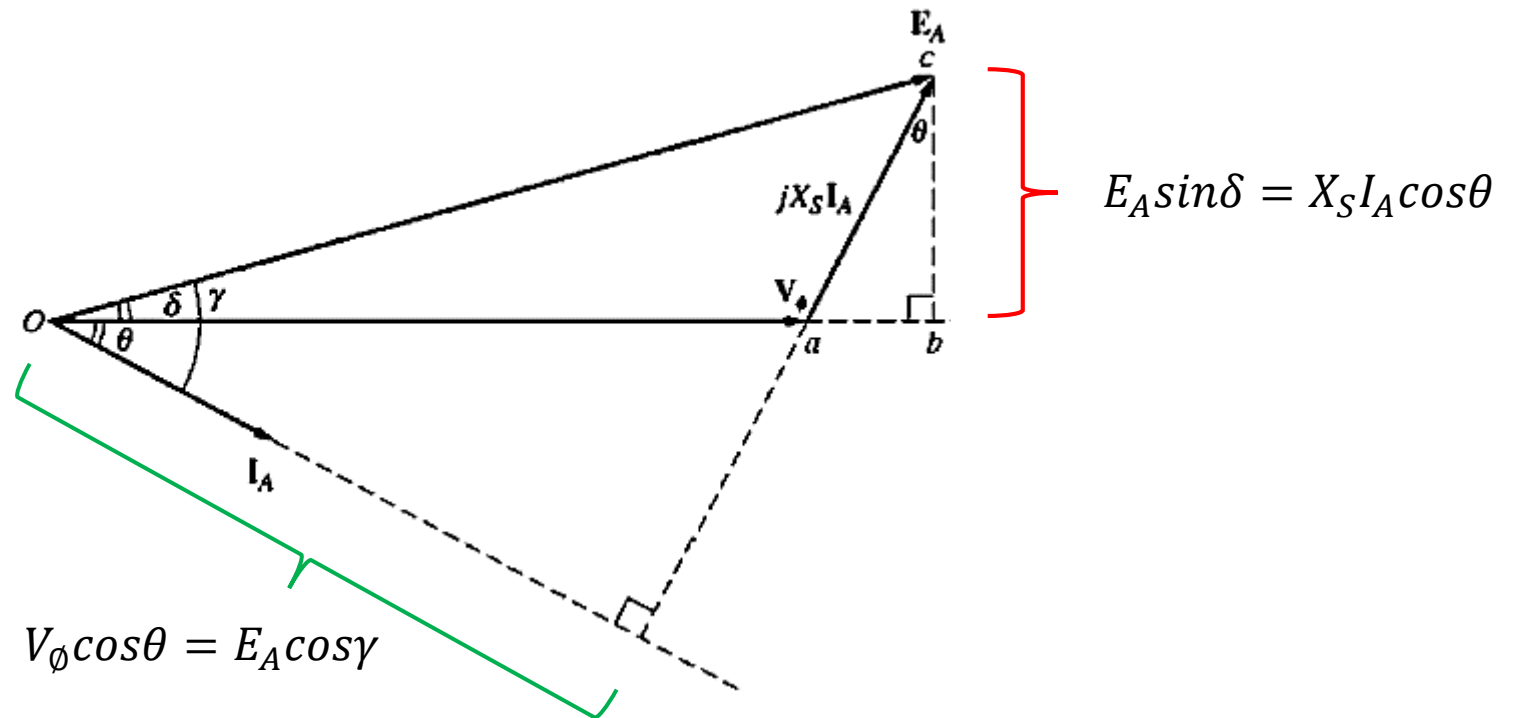- Generally **synchronous reactance** is much greater than **armature resistance** ($X_S \gg R_A$)
- Hence R_A can be ignored in most of the calculations (*but this is not always a rule !*)
- By geometric properties the following two equations can be written if R_A is ignored:



Phasor diagram of sync. gen if R_A is ignored

Power-flow diagram of a synchronous generator

- Three practical equations for the synchronous generator can be obtained by the following derivations:
- At first;

$$E_A \sin \delta = X_S I_A \cos \theta$$

$$I_A \cos \theta = \frac{E_A \sin \delta}{X_S}$$

- And since;

$$P_{out} = 3 \cdot V_\phi \cdot I_A \cdot \cos \theta$$


$$P_{out} = 3V_\phi \frac{E_A \sin \delta}{X_S} \quad (\text{if } \mathbf{R}_A \text{ is ignored})$$

Power-flow diagram of a synchronous generator

- **Torque (power) angle δ** is increased by increasing driving torque
- **Maximum real power output** from a synchronous generator is attained **when $\delta = 90^\circ$**
- **If $\delta > 90^\circ$** , real power output suddenly drops to zero and **the machine loses synchronism**
- $P_{out(max)}$ is called “**steady-state stability limit**” of the synchronous generator
- Generally, synchronous generators are operated with a **small torque angle δ ($15^\circ \leq \delta \leq 20^\circ$)**

$$P_{out} = 3V_\phi \frac{E_A \sin \delta}{X_S} \quad (\text{if } R_A \text{ is ignored})$$
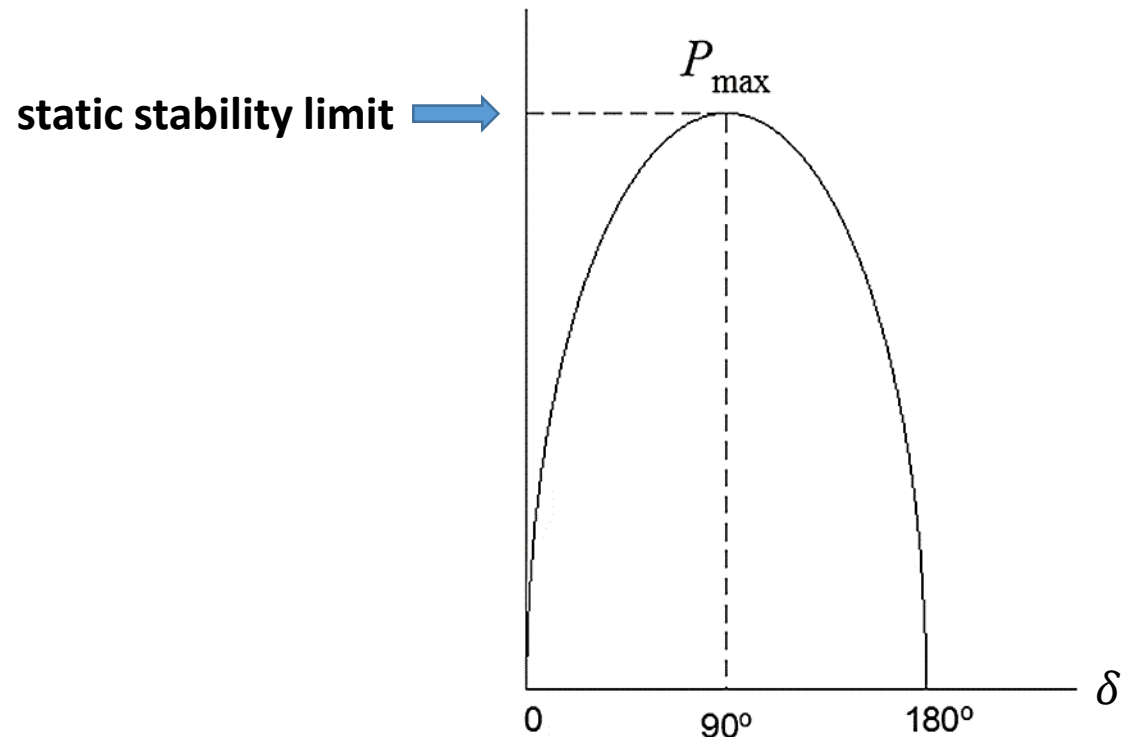
$$P_{out(max)} = \frac{3V_\phi E_A}{X_S} \quad (\text{when } \delta = 90^\circ)$$



Real power output and output electrical frequency are controlled by **generator governor** that controls input mechanical power

Power-flow diagram of a synchronous generator

- Secondly;
- When R_A is ignored, this means that **converted power** becomes equal to **output real power**


$$P_{conv} \cong P_{out}$$

- Since;

$$\left. \begin{aligned} P_{out} &= 3 \cdot V_{\phi} \cdot I_A \cdot \cos\theta \\ V_{\phi} \cos\theta &= E_A \cos\gamma \end{aligned} \right\} P_{out} = 3 \cdot I_A \cdot E_A \cos\gamma$$

$$\tau_{ind} \omega_m \cong 3 \cdot I_A \cdot E_A \cos\gamma$$
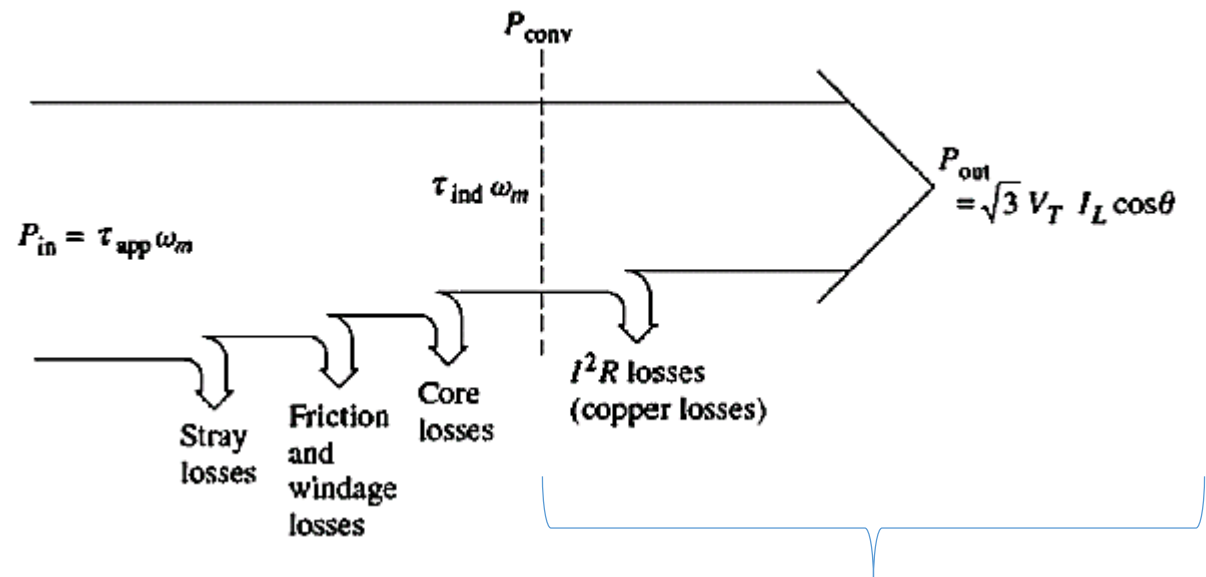
$$\tau_{ind} \cong 3 \cdot I_A \cdot \frac{E_A \cos\gamma}{\omega_m}$$



$$P_{conv} \cong P_{out}$$

(If R_A is ignored)

Power-flow diagram of a synchronous generator

- Thirdly;
- Since;

$$P_{conv} \cong P_{out}$$

$$P_{out} = 3V_{\phi} \frac{E_A \sin \delta}{X_S}$$

$$\tau_{ind} \omega_m \cong 3V_{\phi} \frac{E_A \sin \delta}{X_S}$$


$$\tau_{ind} = 3V_{\phi} \frac{E_A \sin \delta}{\omega_m X_S} \quad (\text{if } R_A \text{ is ignored})$$

Measuring sync. gen. model parameters

- The equivalent circuit of a synchronous generator that has been derived contains **three quantities** that must be determined in order to completely describe the behavior of a real synchronous generator:

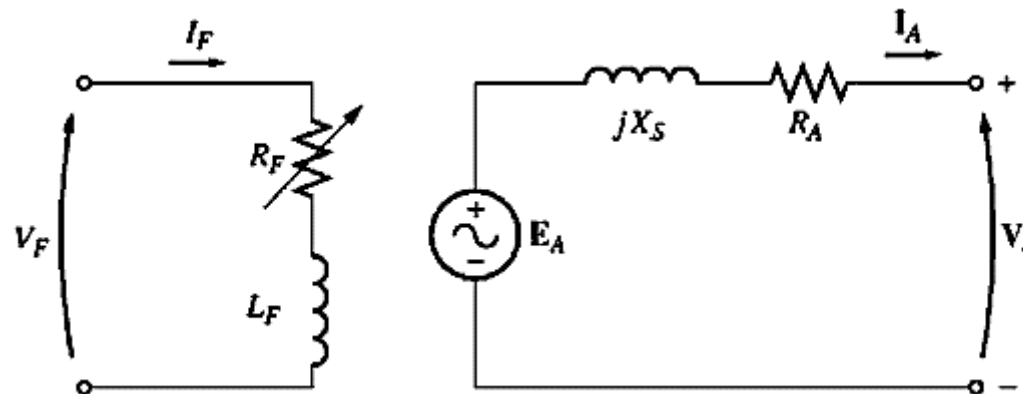- 1) The relationship between field current I_F and flux Φ (or between I_F and armature voltage E_A)
- 2) Synchronous reactance, X_S
- 3) Armature resistance, R_A

- Different tests are applied to determine these quantities



Measuring sync. gen. model parameters

- The **first** test is «**open-circuit test**» on the synchronous generator
- The steps of this test can be listed as:
 - The **terminals of the stator** are **open circuited**
 - A voltmeter is connected through the terminals of the stator
 - The **field current** is set to **zero**
 - The generator is turned at the **rated speed** with the prime mover (for example an AC/DC motor)
 - The field current is **gradually increased in steps** and the **terminal voltage** is **measured** at each step
 - Since the stator is *open-circuited*, **armature voltage** E_A can be measured from stator terminals:


□ If stator is **Y-connected**:

$$V_{T(OC)} = \sqrt{3} \cdot E_A \rightarrow E_A = \frac{V_{T(OC)}}{\sqrt{3}}$$


□ If stator is **Δ -connected**:

$$V_{T(OC)} = E_A$$

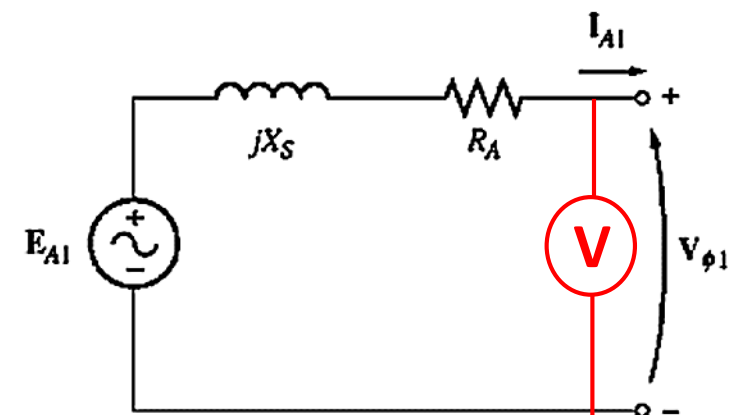- The measured points are plotted to obtain **open-circuit characteristics**



Measuring sync. gen. model parameters

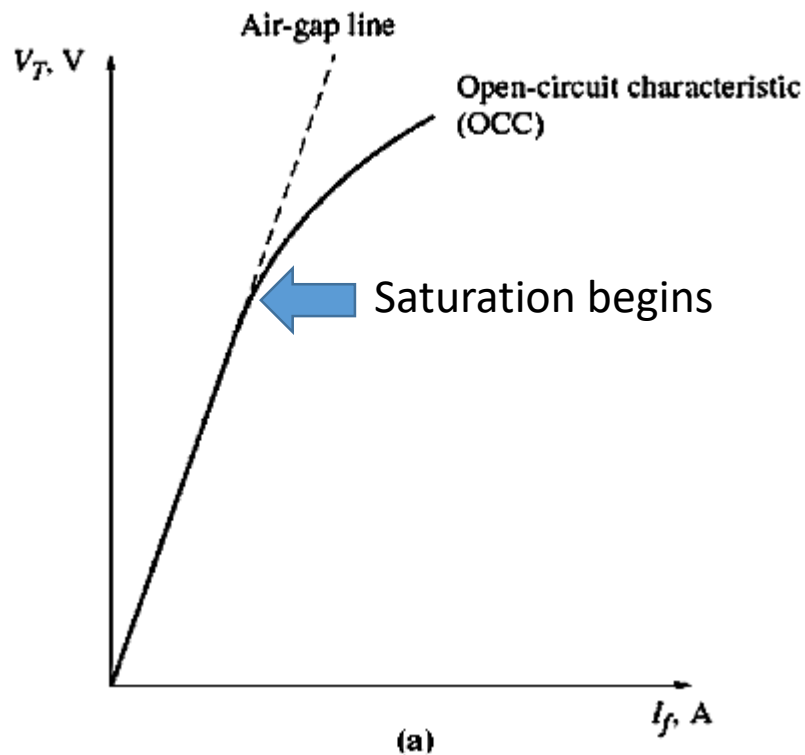


The **open-circuit characteristic (OCC)** of a three-phase synchronous generator


- With OCC, we can find the magnitude of E_A for any given field current I_F
- Initially, the curve is almost perfectly **linear**, until some **saturation** is observed at high field currents
- When the iron finally saturates, the reluctance of the iron increases dramatically, and the flux increases much more slowly with an increase in magnetomotive force
- The linear portion of OCC is called «**air-gap line**»

Measuring sync. gen. model parameters

- The **second** test is «**short-circuit test**» on the synchronous generator
- The steps of this test can be listed as:
 - The **terminals of the stator** are **short-circuited using an ammeter**
 - **The field current** is set to **zero**
 - The generator is turned at the **rated speed** with the prime mover (for example an AC/DC motor)
 - The field current is **gradually increased in steps** and the **short-circuit armature current (or line current)** (*ammeter reading*) is measured
 - The measured points are plotted to obtain **short-circuit characteristics**

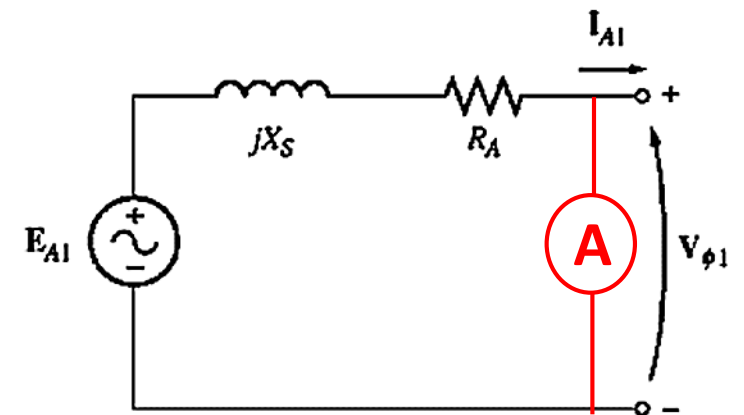

Measuring sync. gen. model parameters

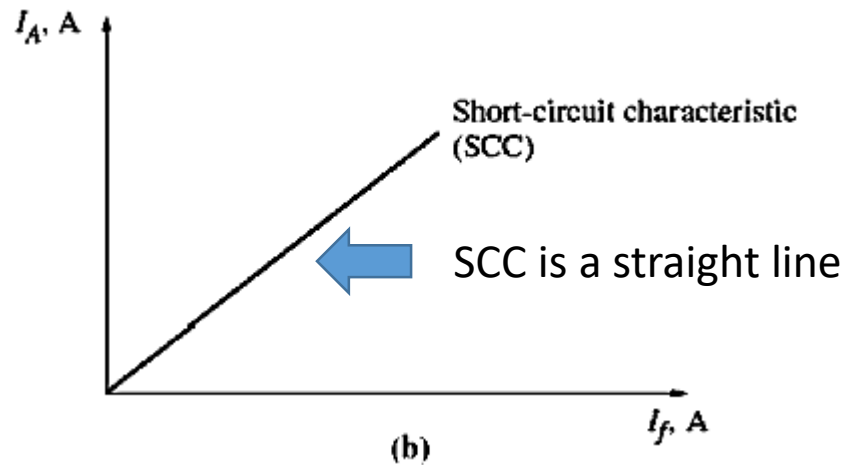

The **short-circuit characteristic (SCC)** of a three-phase synchronous generator

Measuring sync. gen. model parameters

- An important question: *Why is SCC a straight line?*
- Since;


$$V_{\phi} = E_A + E_{STAT} = 0 \quad (\text{Short-circuit})$$

$$E_A = -E_{STAT}$$

- Since B_R is related with E_A and,
- B_S is related with E_{STAT}
- B_R and B_S will **cancel** each other
- So there will be **no magnetic field** in the machine and hence **no saturation is observed**
- Because of this reason, **SCC of a synchronous generator is a straight line**

Measuring sync. gen. model parameters

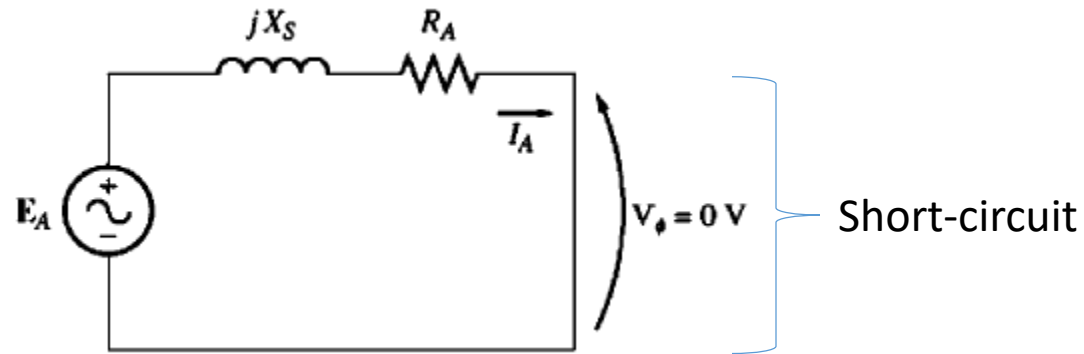- Let's join the results of these two tests (*open-circuit and short-circuit tests*) to find X_S :



$$I_A = \frac{E_A}{R_A + jX_S} \quad \rightarrow \quad |I_A| = \frac{|E_A|}{\underbrace{\sqrt{R_A^2 + X_S^2}}_{|Z_S| \text{ (synchronous impedance)}}} \quad \text{(The magnitude of armature current)}$$

Measuring sync. gen. model parameters

- Since;

$$|Z_S| = \sqrt{R_A^2 + X_S^2}$$

- And generally;

$$X_S \gg R_A$$

$$|Z_S| \cong X_S$$


$$X_S \cong \frac{|E_A|}{|I_A|} = \frac{|V_{\phi(OC)}|}{|I_A|}$$

- Therefore, an approximate method for determining the synchronous reactance X_S at a given field current is

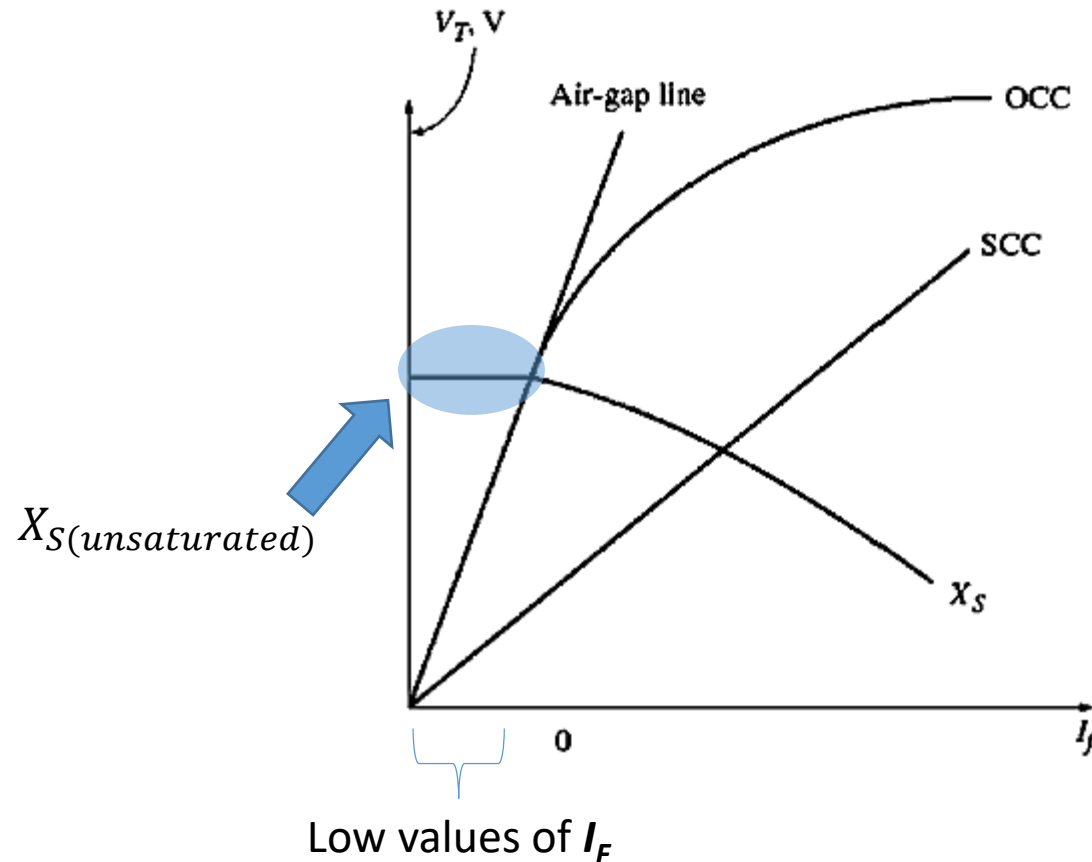- 1) Get the internal generated voltage E_A from **OCC** at that field current
- 2) Get the short-circuit current $I_{A,SC}$ from **SCC** at that field current
- 3) Find X_S by applying the below equation.

Measuring sync. gen. model parameters


- But with this method we can only find the **approximated value** of X_s in **unsaturated region**
- We have to use **low field current values** to find the value of X_s in **unsaturated region**



Measuring sync. gen. model parameters

- The **third** test is «*armature resistance measurement test*» on the synchronous generator
- The steps of this test can be listed as:
 - Stop the rotation of the rotor of the synchronous generator
 - Set the **field current** to **zero**
 - Measure the armature resistance by an ohmmeter (ohmmeter uses DC voltage)
 - or apply a DC voltage to the armature windings and measure the armature current
 - The reason of using DC voltage is to set all reactances to be zero (frequency will be zero)
 - This technique is **not perfectly accurate**, since the **AC resistance** will be larger than **DC resistance** because of the **skin effect**

Measuring sync. gen. model parameters

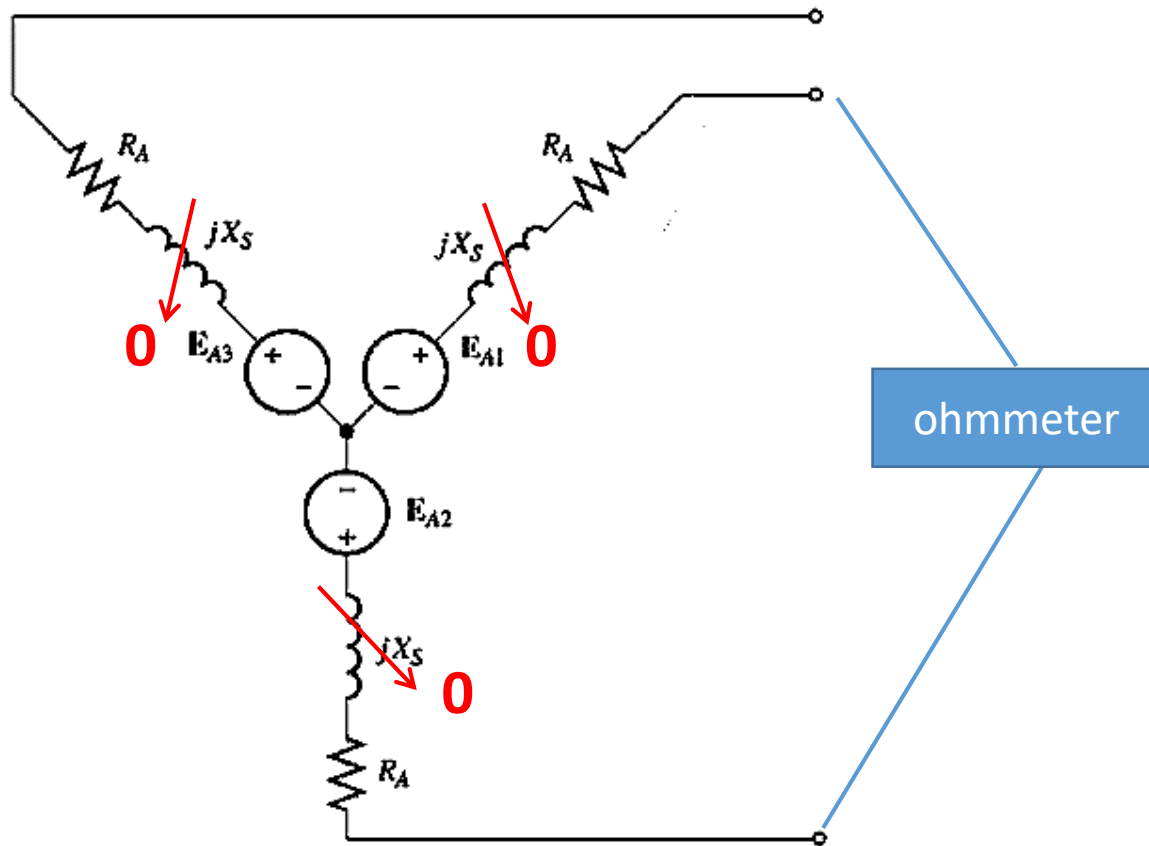


$$\text{ohmmeter reading} = 2R_A$$

$$R_A = \frac{\text{ohmmeter reading}}{2}$$

Applying armature resistance measurement test to **Y-connected** stator

Measuring sync. gen. model parameters

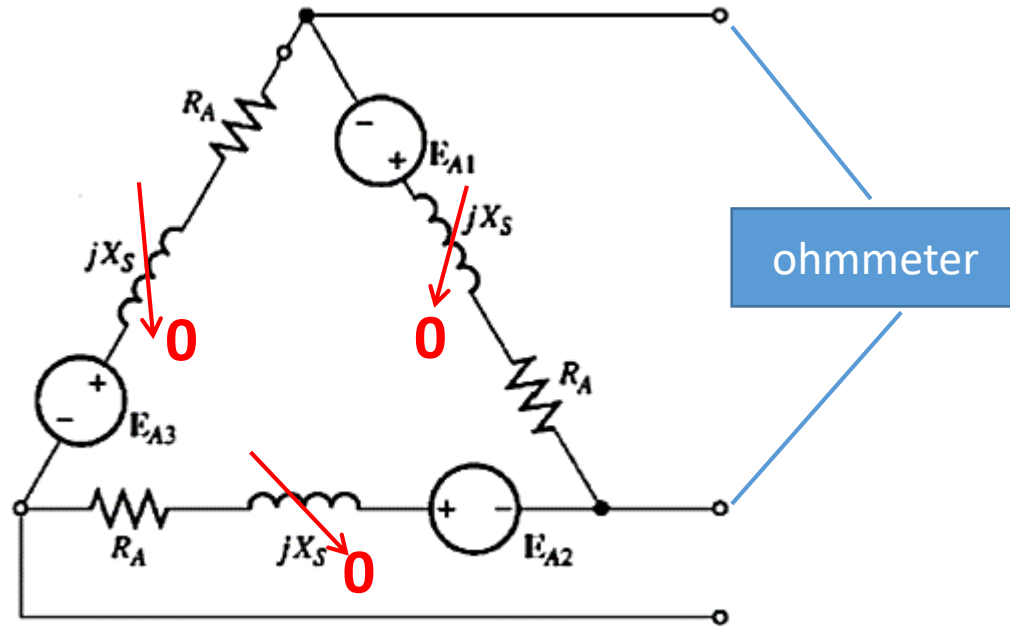

ohmmeter reading = $(R_A + R_A)$ parallel with R_A


$$\text{ohmmeter reading} = \frac{2}{3} R_A$$

$$R_A = \frac{\text{ohmmeter reading}}{2/3}$$

Applying armature resistance measurement test to **Δ -connected** stator

Short-circuit ratio

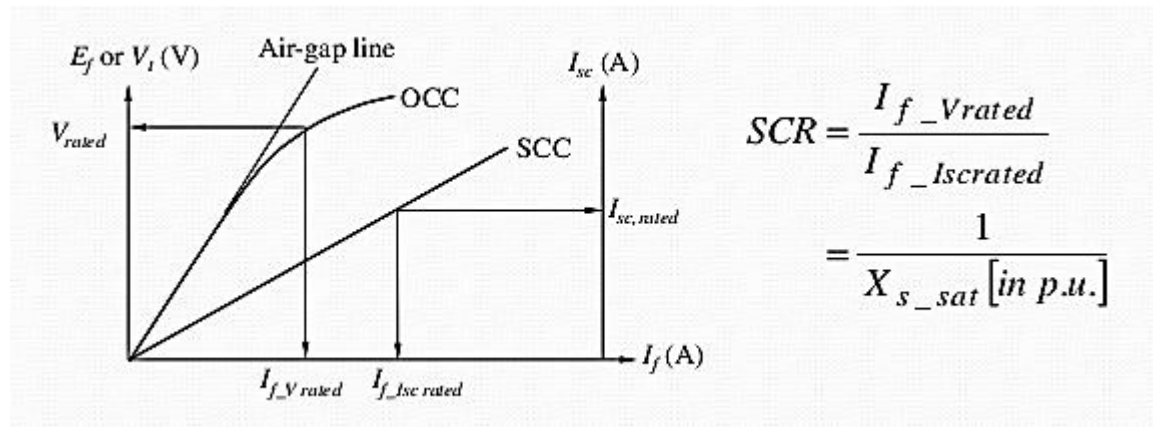- The **short-circuit ratio (SCR)** of a **synchronous generator** is defined as the ratio of the **field current** required for the **rated voltage at open circuit** to the **field current** required for the **rated armature current at short circuit**
- **SCR** is also the reciprocal of the per-unit value of the approximate saturated synchronous reactance



Short-circuit ratio

Example: A 200-kVA, 480-V, 50-Hz, Y-connected synchronous generator with a rated field current of 5 A was tested, and the following data were taken:

1. $V_{T,OC}$ at the rated field current was measured to be **540 V**
2. $I_{L,SC}$ at the rated field current was measured to be **300 A**
3. When a DC voltage of **10 V** was applied to the two of the terminals of the stator, a current of **25 A** was measured.

Find the values of the **armature resistance** and the **approximate synchronous reactance** in ohms that would be used in the generator model at the rated conditions.

Short-circuit ratio

Solution:

From armature resistance measurement test :

Since stator is Y-connected:

$$R_A = \frac{\text{ohmmeter reading}}{2}$$

$$R_A = \frac{10V/25A}{2} = 0.2 \text{ ohm}$$

Short-circuit ratio

Solution:

- The internal generated voltage at the rated field current is equal to:

$$E_A = V_{\phi(OC)} = \frac{V_T}{\sqrt{3}} = \frac{540V}{\sqrt{3}} = 311.8 V$$

- The short-circuit current is equal to the line current, since the generator is Y-connected:

$$I_{A(SC)} = I_{L(SC)} = 300 A$$

$$|Z_S| = \sqrt{R_A^2 + X_S^2} = \frac{E_A}{I_A} = \frac{311.8}{300} = 1.039 \text{ ohm}$$

Alternative way:

$$X_S \cong \frac{|E_A|}{|I_A|} = \frac{|V_{\phi(OC)}|}{|I_A|} = \frac{311.8}{300} = 1.039$$


- Since;

$$R_A = 0.2 \text{ ohm} \Rightarrow \sqrt{(0.2)^2 + X_S^2} = 1.039 \Rightarrow X_S = 1.02 \text{ ohm}$$

Short-circuit ratio


Solution:

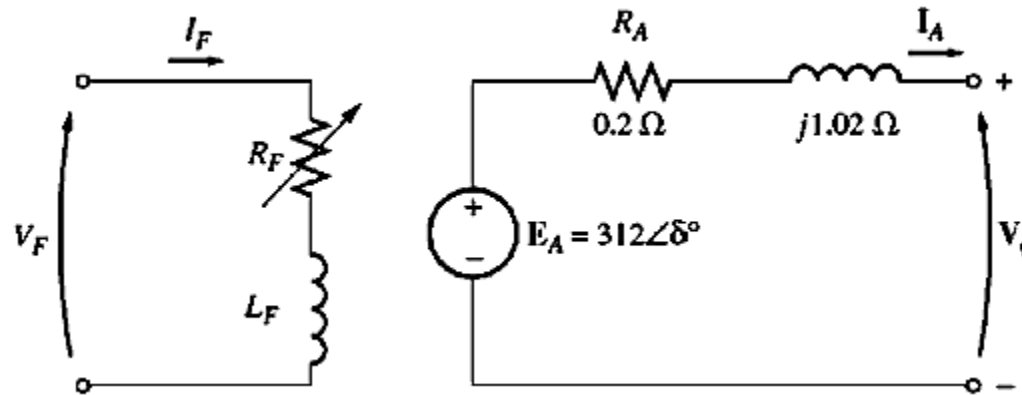- The resulting per-phase equivalent circuit of the synchronous generator is shown below:



Synchronous generator operating alone


- A sync. generator is **rarely operated alone** for *emergency purposes* or a *few specialized applications*
- We assume that R_A (armature resistance) is generally **ignored** in our analysis
- We assume that **shaft speed** is **constant** (generator output frequency is **constant**, 50 or 60 Hz)
- If otherwise not stated we can assume that I_F and hence the flux (Φ) is constant in the machine
- The field current on the rotor (I_F) can be controlled if desired

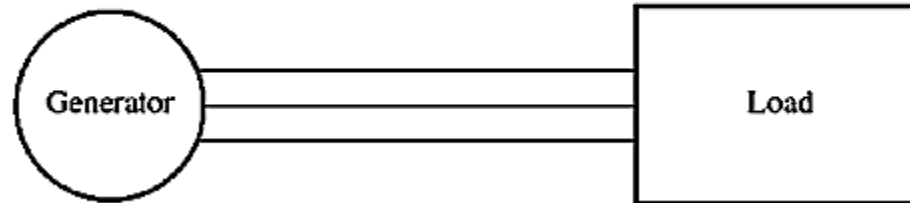

Synchronous generator operating alone (*connected to load*)

Synchronous generator operating alone

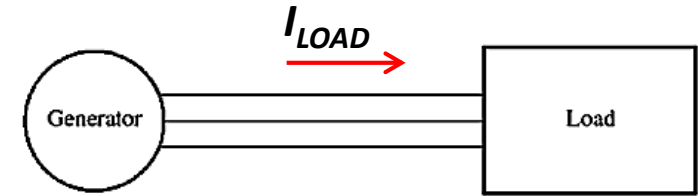- Now assume that the **load of the generator is increased !**
- *What happens now ?*



- An increase in the load means that the load's **real** and/or **reactive power** taken from the generator is **increased**
- Such a **load increase** increases the **load current** drawn from the generator





- The magnitude of the internal generated voltage E_A **does not change** *when the load increases*, because;
 - ✓ we do not change field current I_F , hence the flux in the machine (Φ) is constant
 - ✓ the speed of the prime mover is constant (ω)

$$\underbrace{|E_A|}_{\text{constant}} = K \underbrace{\Phi}_{\text{constant}} \omega$$

Synchronous generator operating alone

Lagging power factor case:

$$|E_A| = K\phi\omega = \text{constant}$$

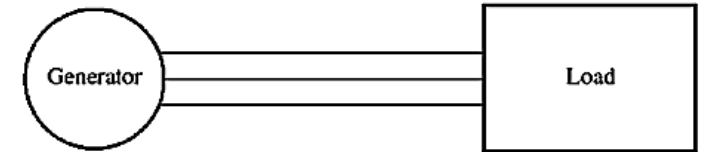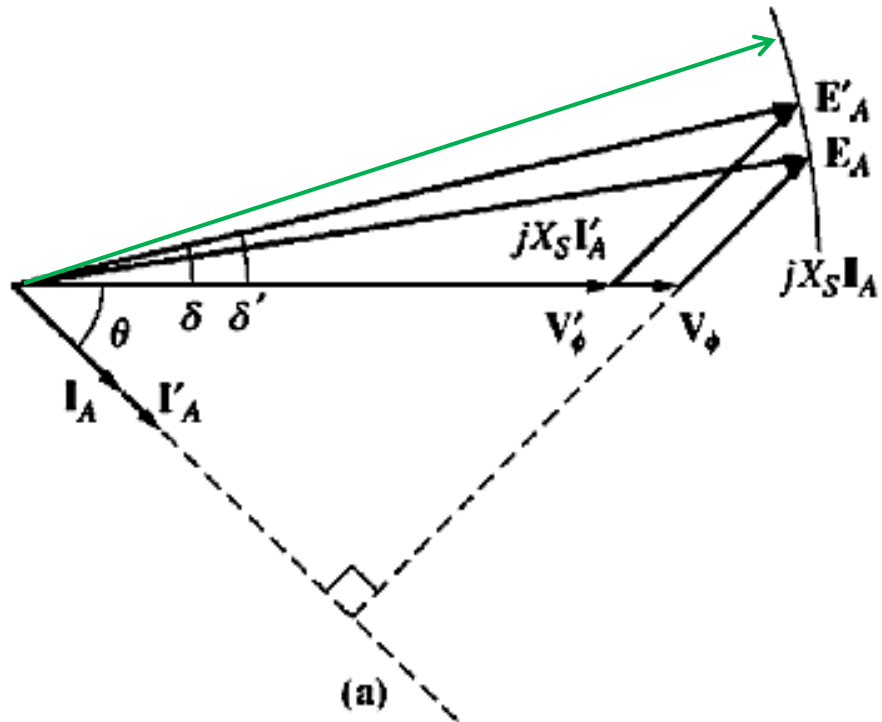

Green distance is constant

The results:



- 1) Phase voltage of the generator **decreases**
- 2) Torque angle **increases**

The effect of an increase in the load at **lagging power factor**

Synchronous generator operating alone

Unity power factor case:

$$|E_A| = K\phi\omega = \text{constant}$$

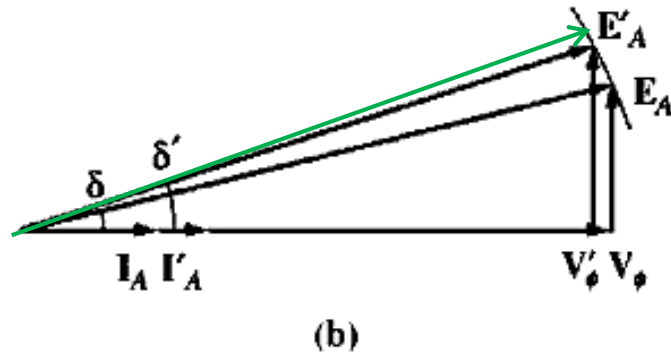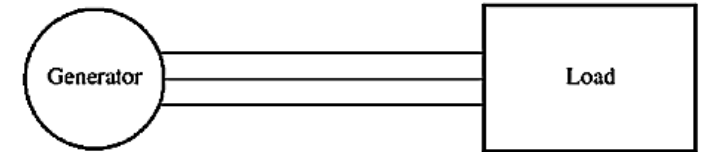

Green distance is constant

The results:



- 1) Phase voltage of the generator **decreases**
- 2) Torque angle **increases**

The effect of an increase in the load at **unity power factor**

Synchronous generator operating alone

Leading power factor case:

$$|E_A| = K\phi\omega = \text{constant}$$

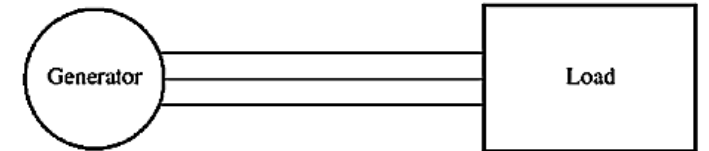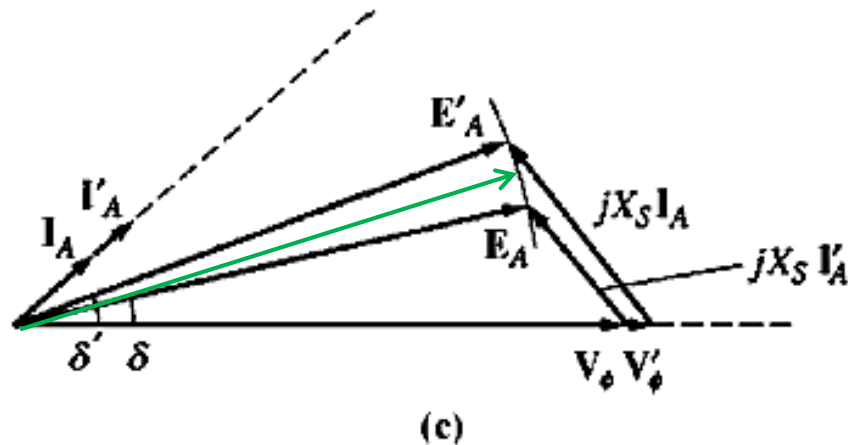

Green distance is constant

The results:

- 1) Phase voltage of the generator **increases**
- 2) Torque angle **increases**

The effect of an increase in the load at **leading power factor**

Synchronous generator operating alone

- In summary:

If we increase the load connected to the synchronous generator;

- Phase voltage (and also terminal voltage) **decreases** if the load has a **lagging power factor**
- Phase voltage (and also terminal voltage) **decreases** if the load has a **unity power factor**
- Phase voltage (and also terminal voltage) **increases** if the load has a **leading power factor**

- And **torque angle increases** for all cases

Synchronous generator operating alone

Voltage Regulation and Load type:

$$VR = \frac{V_{nl} - V_{fl}}{V_{fl}} \times 100\%$$

1) If load is **lagging power factor load**:

$$V_{fl} < V_{nl} \rightarrow VR > 0$$

2) If load is **unity power factor load**:


$$V_{fl} < V_{nl} \rightarrow VR > 0$$

3) If load is **leading power factor load**:

$$V_{fl} > V_{nl} \rightarrow VR < 0$$

Synchronous generator operating alone

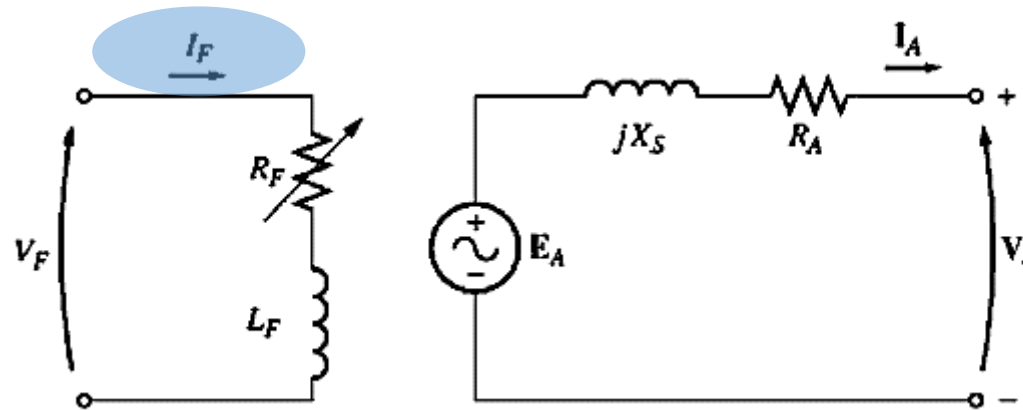- We see that in previous section, **terminal voltage of generator changes when load changes.**
- So what can we do to restore the voltage to its previous value ?
- **The solution: Adjust field current**
- **Our purpose: $V_R \approx 0$**



$$R_F \swarrow \quad I_F \nearrow \quad \Phi \nearrow \quad \nearrow |E_A| = K\Phi\omega \quad \nearrow |V_\Phi| \quad \nearrow |V_T|$$

Synchronous generator operating alone

Example 1: A 480-V, 60-Hz, delta-connected, four-pole synchronous generator has the OCC shown in the figure. This generator has a synchronous reactance of $j0.1$ ohm and armature resistance of 0.0125 ohm. At full-load, the machine supplies 1200A at 0.8 PF lagging. Under full-load conditions, the friction and windage losses are 40 kW and the core losses are 30 kW. Ignore any field circuit losses.

(a) What is the speed of rotation of this generator?

(b) How much field current must be supplied to the generator to make the terminal voltage 480 V at no load?


(c) If the generator is now connected to a load and the load draws 1200 A at 0.8 PF lagging, how much field current will be required to keep the terminal voltage equal to 480 V?

(d) How much power is the generator now supplying? How much power is supplied to the generator by the prime mover? What is this machine's overall efficiency?

(e) If the generator's load were suddenly disconnected from the line, what would happen to its terminal voltage?

(j) Finally, suppose that the generator is connected to a load drawing 1200 A at 0.8 PF *leading*. How much field current would be required to keep V_T at 480 V?

Synchronous generator operating alone

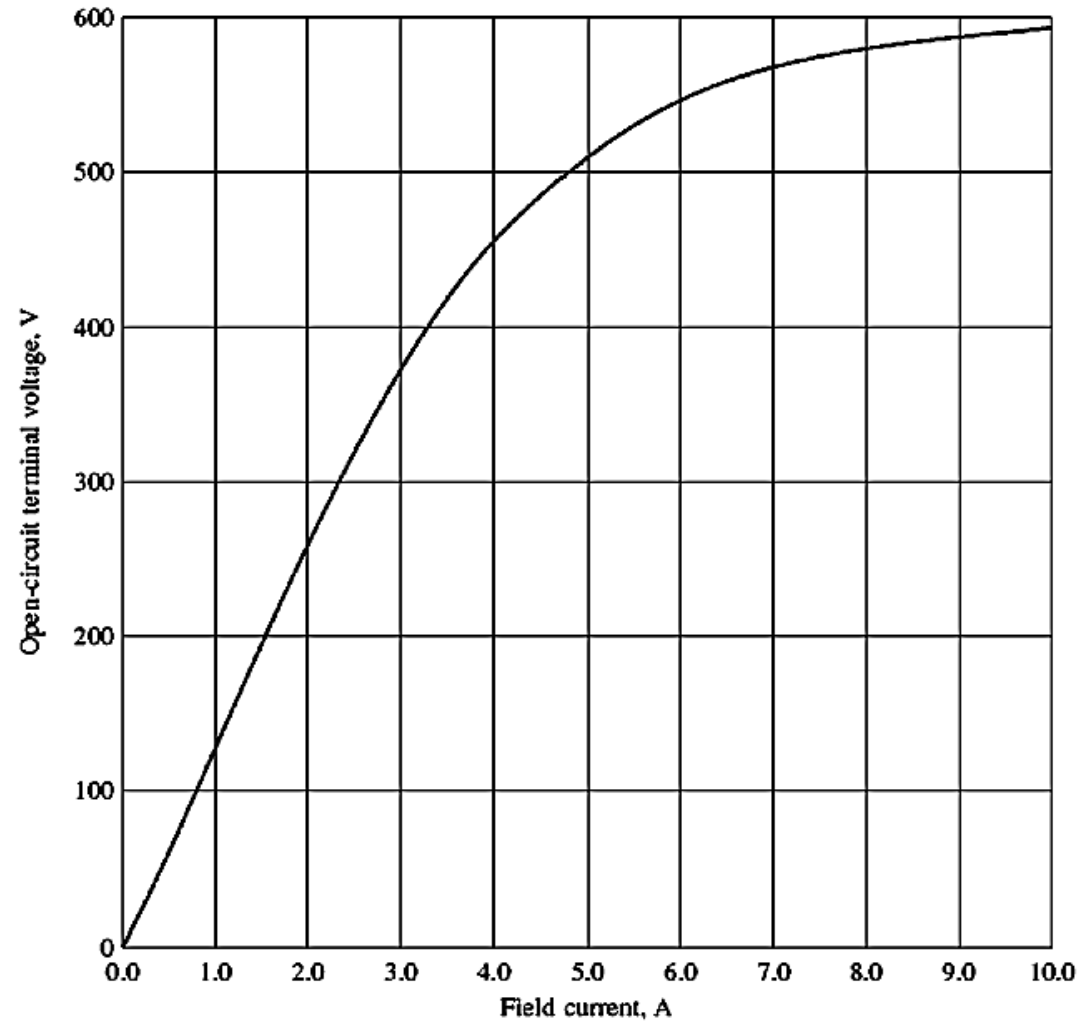

OCC characteristics of the synchronous generator

Synchronous generator operating alone

Example 2: A 480-V, 50-Hz, Y-connected, six-pole synchronous generator has a per-phase synchronous reactance of 1.0 ohm. Its full-load armature current is 60 A at 0.8 PF lagging. This generator has friction and windage losses of 1.5 kW and core losses of 1.0 kW at 60 Hz at full load. Since the armature resistance is being ignored, assume that the copper losses are negligible. The field current has been adjusted so that the terminal voltage (VT) is 480 V at no load.

(a) What is the speed of rotation of this generator?

(b) What is the terminal voltage of this generator if the following are true?

1. *It is loaded with the rated current at 0.8 PF lagging.*
2. *It is loaded with the rated current at 1.0 PF.*
3. *It is loaded with the rated current at 0.8 PF leading.*

(c) What is the efficiency of this generator (*ignoring electrical losses*) when it is operating at the rated current and 0.8 PF lagging?


(d) How much shaft torque must be applied by the prime mover at full load? How large is the induced torque ?

(e) What is the voltage regulation of this generator at 0.8 PF lagging? At 1.0 PF? At 0.8 PF leading?

Parallel operation of AC generators

Why do we need parallel operation of AC generators?

- Several generators can supply a bigger load than one machine by itself.
- Having many generators increases the reliability of the power system, since the failure of anyone of them does not cause a total power loss to the load.
- Having many generators operating in parallel allows one or more of them to be removed for shutdown and preventive maintenance.
- If only one generator is used and it is not operating at near full load, then it will be relatively inefficient. With several smaller machines in parallel, it is possible to operate only a fraction of them. The ones that do operate are operating near full load and thus more efficiently.

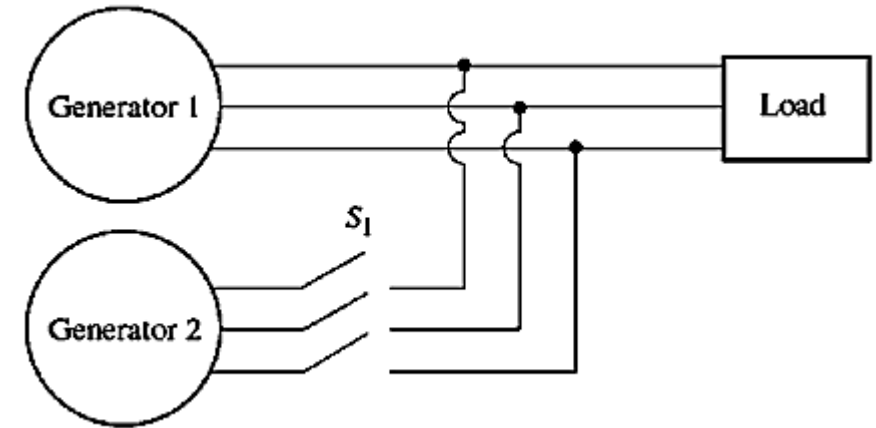

Conditions required for paralleling

- Before paralleling (*closing switch S1*) some conditions should be satisfied:


1) The **rms line voltages** of the two generators must be **equal**

$$|V_{AB}| \text{ for } G1 = |V_{AB}| \text{ for } G2$$

$$|V_{BC}| \text{ for } G1 = |V_{BC}| \text{ for } G2$$



$$|V_{CA}| \text{ for } G1 = |V_{CA}| \text{ for } G2$$

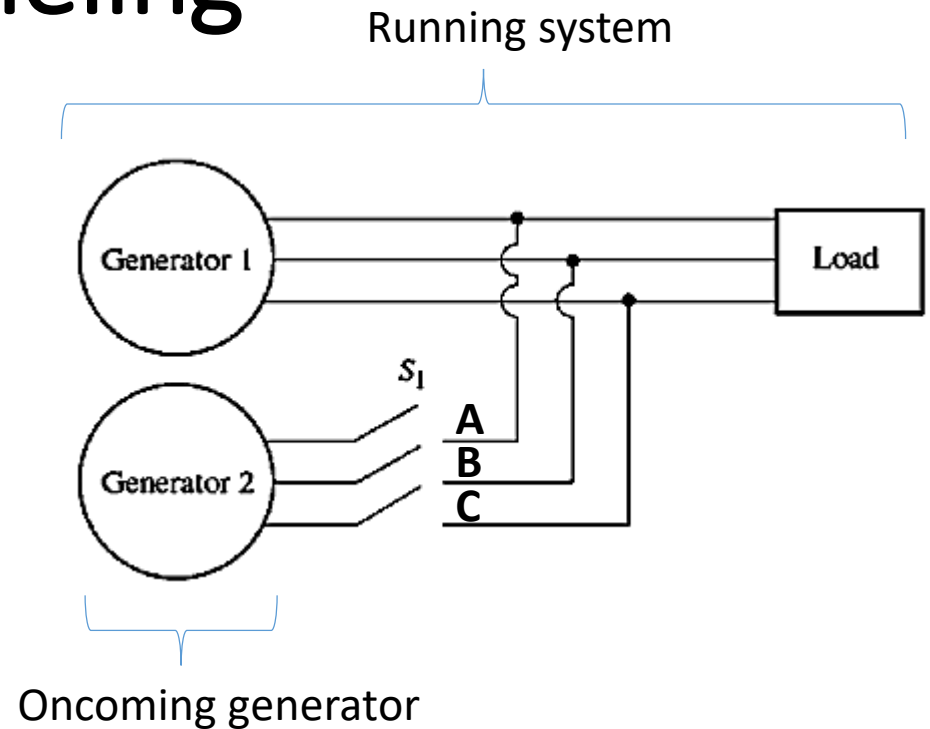- Adjusting the line voltage of the *oncoming generator* is done by adjusting its **field current**.
- By using **voltmeter**, the field current of the oncoming generator should be adjusted until its terminal voltage becomes equal to the line voltage of the running system.




Conditions required for paralleling

2) The two generators must have the **same phase sequence**

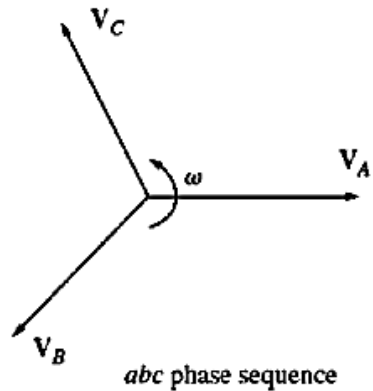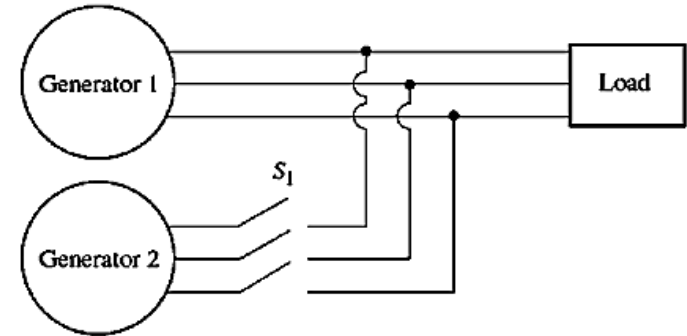


Gen1

Positive phase sequence

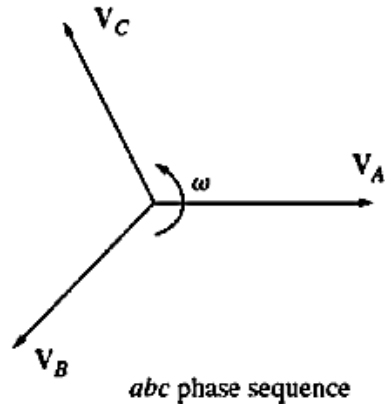


Gen2

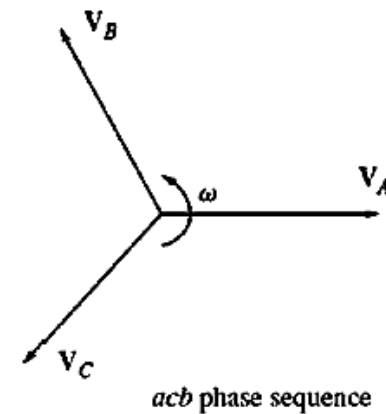

Gen1


Negative phase sequence

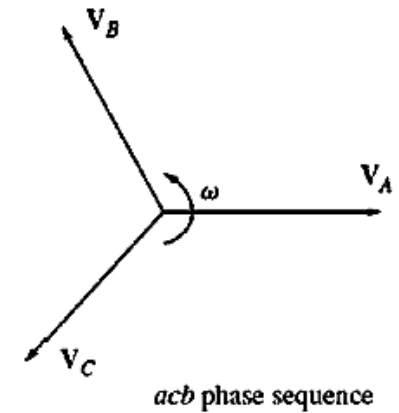

Gen2

Conditions required for paralleling

- To check phase sequences we have three options:

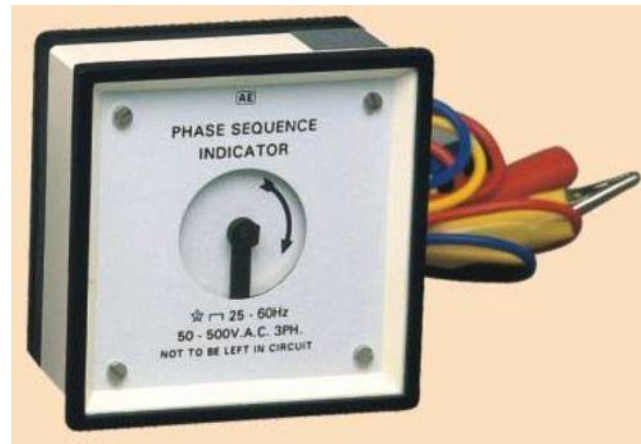


Option 1: use phase sequence indicator



Option 2: use a small three-phase induction motor and observe its rotation direction

Conditions required for paralleling

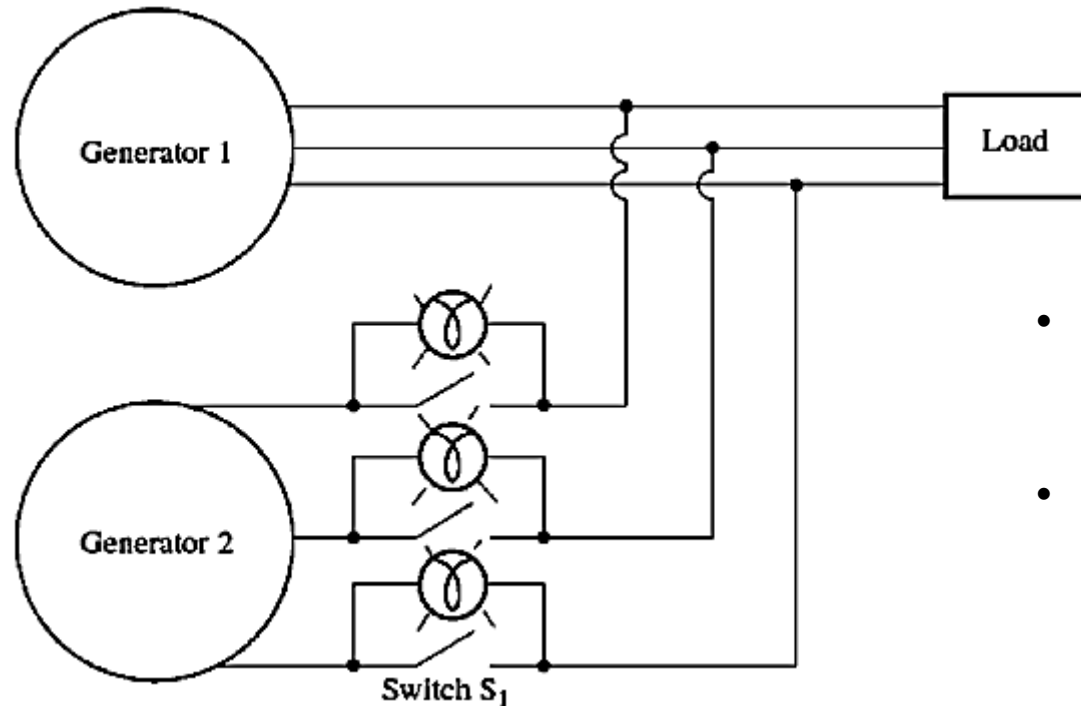- To check phase sequences we have three options:




- If all three bulbs **get bright and dark together**, this means that both generators have the same phase sequence
- If the bulbs **brighten in succession**, this means that the generators have the opposite phase sequence, and two phases of the Gen 2 **must be exchanged**

Option 3: Use three-bulbs connected as shown

Conditions required for paralleling

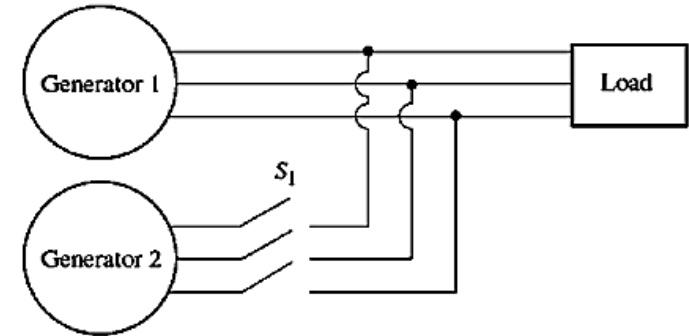3) The **frequency of the oncoming generator** must be adjusted to be **slightly higher** than the frequency of the running system. So that when it is connected, it will come on the line supplying power as a **generator**, instead of consuming the power as a **motor**



This check can be done by **two options**:

1) Use a frequency meter



2) Use a tachometer to measure the shaft speed of Gen 2




$$n_m = \frac{120f_e}{P}$$

Conditions required for paralleling

4) The **phase angles** of the same phases must be **equal**.

- To check phase angles we have **two options**:

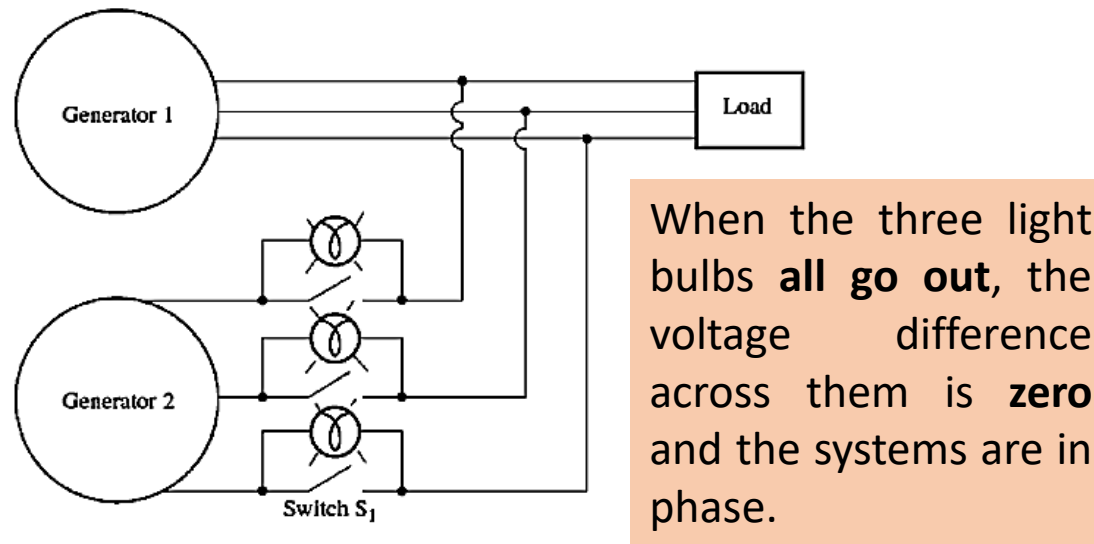

Option 1: Use three-bulbs method

Conditions required for paralleling

Option 2: Use a synchroscope




A ***synchroscope*** is a meter that measures the phase angle difference between the ***a-phases*** of the two systems.

How can we use synchroscope ?

- The needle should **rotate slowly**.
- ***If it rotates to the right:*** This means that the oncoming generator is **faster** than the running system (***the desired situation***)
- ***If it rotates to the left:*** This means that the oncoming generator is **slower** than the running system
- When the synchroscope needle is **in the vertical position**, we can close switch **S1**

Frequency-Power characteristics

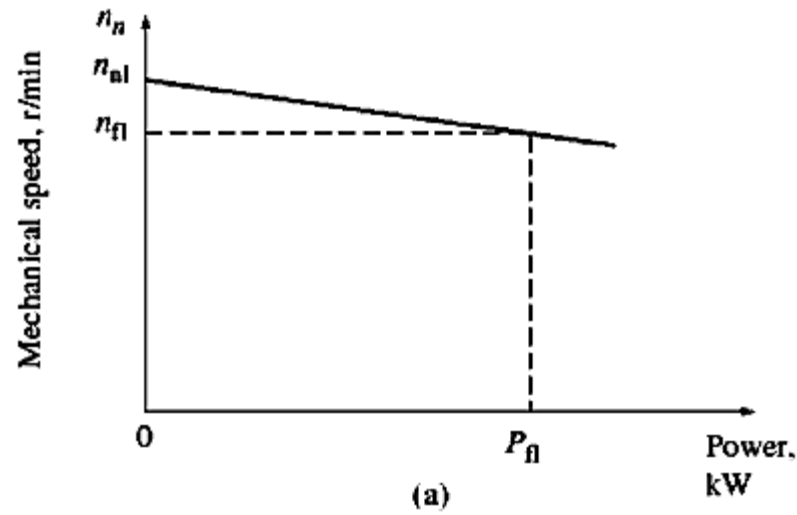- All generators are driven by a *prime mover*, which is the generator's source of mechanical power. Examples are steam turbine, diesel engines, gas turbines, water turbines, wind turbines, etc...
- All prime movers tend to behave in a similar fashion: **The power drawn from them increases, the speed at which they turn decreases.**



The speed vs power characteristics for a typical prime mover

Frequency-Power characteristics


- The speed droop (**SD**) of a prime mover is defined by the following equation:

$$SD = \frac{n_{nl} - n_{fl}}{n_{fl}} \times 100\%$$

n_{nl} → No-load speed of the prime mover

n_{fl} → Full-load speed of the prime mover

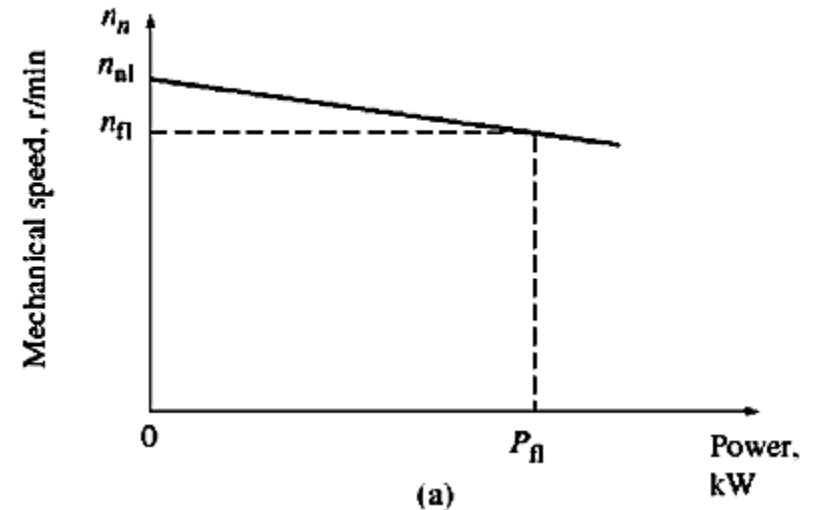- Most generator prime movers have a speed droop of **2 to 4 %**






Frequency-Power characteristics

- Since the shaft of the synchronous generator (*rotor*) is connected to the prime mover, the prime mover speed defines the electrical frequency output of the generator:

prime mover speed

$$f_e = \frac{n_m P}{120}$$

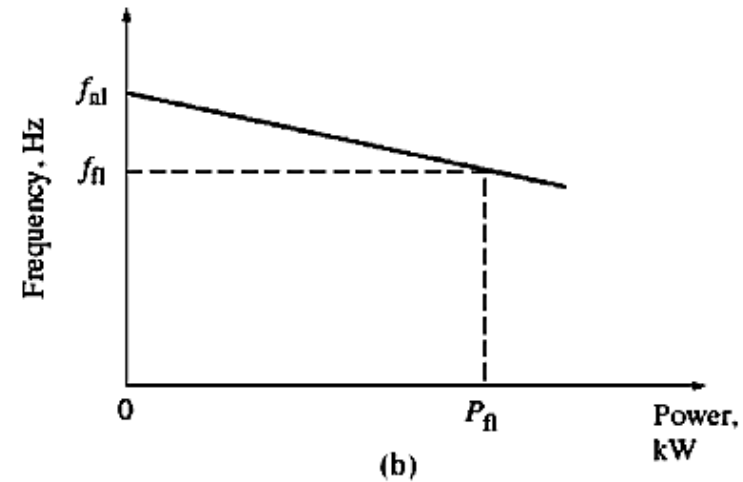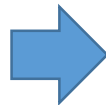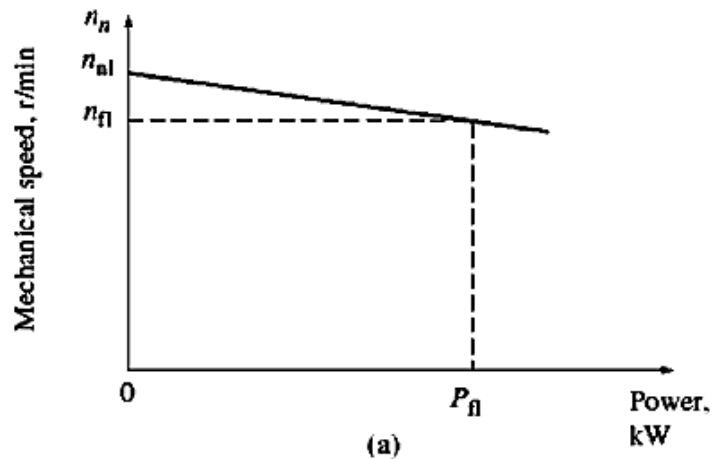

Frequency-Power characteristics

- According to the figure:

P_{fl} is the **full-load power** at frequency f_{fl}

Power output is **0** at frequency f_{nl}

- The equation for this line:


$$P = sp(f_{nl} - f_{sys})$$

P is the **power output** of the generator

f_{nl} is the **no-load frequency** of the generator

f_{sys} is the **operating frequency of the system**

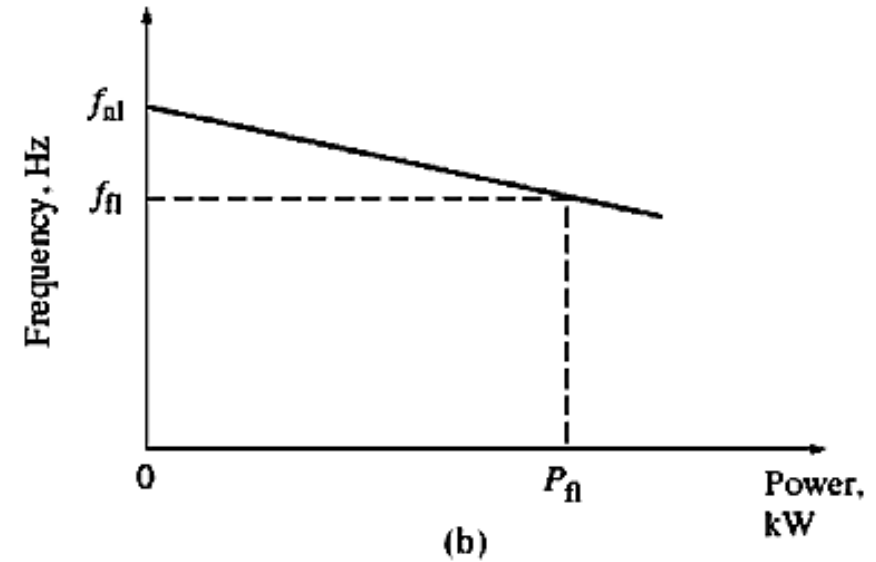sp is the **slope of curve** (kW/Hz or MW/Hz)




Voltage-Reactive power characteristics

- When a **lagging (or unity) power factor load** is connected to a synchronous generator, **terminal voltage drops**.
- When a **leading load** is connected to a synchronous generator, **terminal voltage increases**.
- The equation for this line:

$$Q = m(V_{Tnl} - V_T)$$

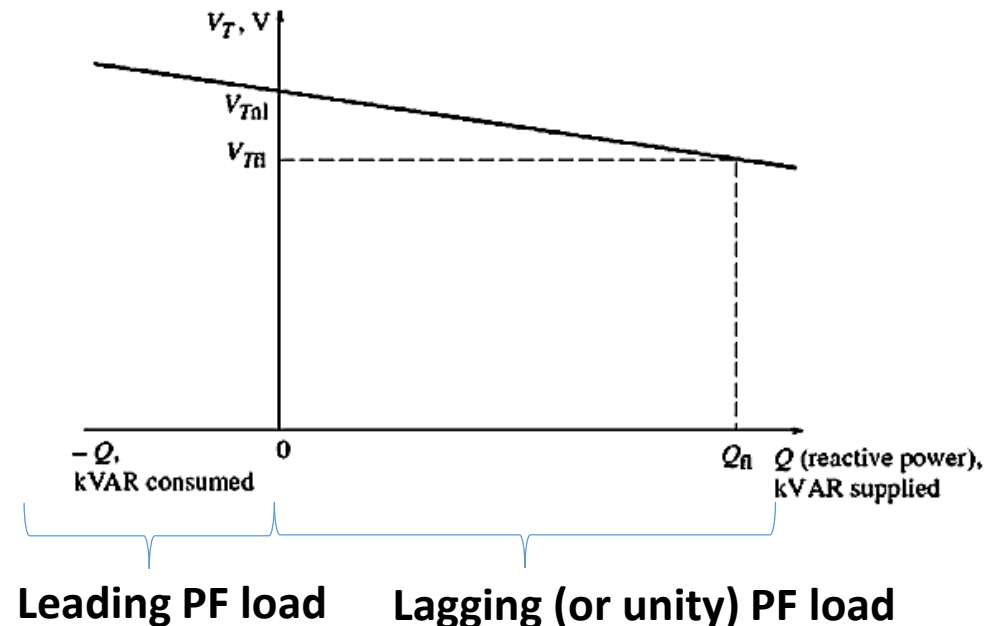
Q is the **reactive power output** of the generator
 V_{Tnl} is the **no-load terminal voltage** of the generator
 V_T is the **terminal voltage of the generator** at the **operating point**
 m is the **slope of curve** (kVAR/Volt or MVAR/Volt)



Example:

Figure shows a generator supplying a load. A second load is to be connected in parallel with the first one. The generator has a no-load frequency of **61.0 Hz** and a slope *sp* of **1MW/Hz**. **Load 1** consumes a real power of **1000 kW** at 0.8 PF lagging, while **Load 2** consumes a real power of **800 kW** at 0.707 PF lagging.

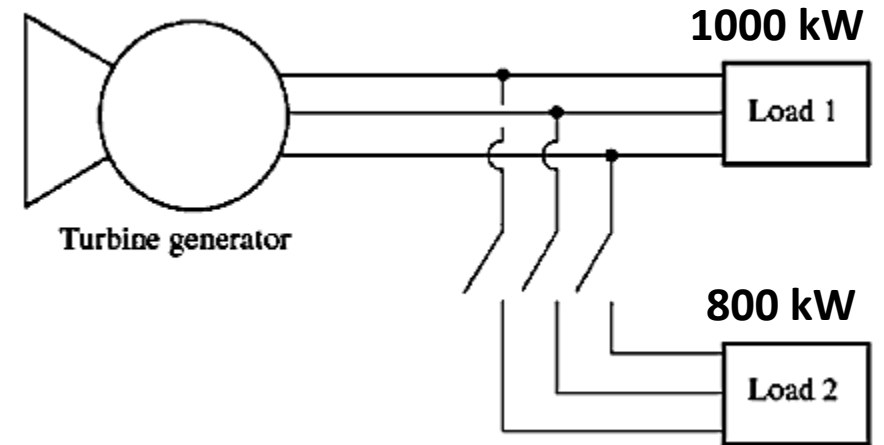- (a) Before the switch is closed, what is the operating frequency of the system?
- (b) After Load 2 is connected, what is the operating frequency of the system?
- (c) After Load 2 is connected, what action could an operator take to restore the system frequency to 60 Hz?





Solution:

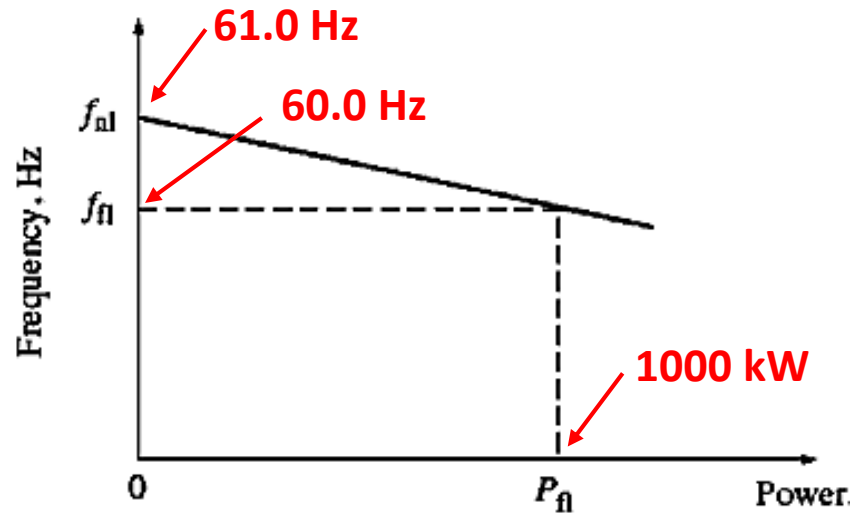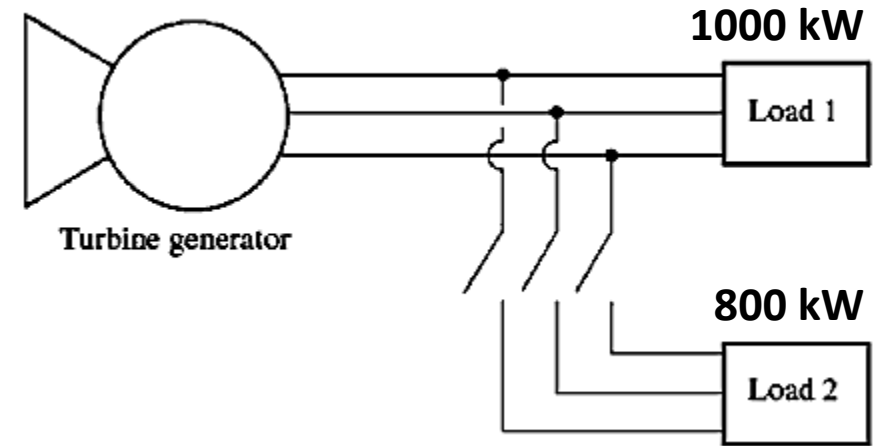(a) Before the switch is closed, the operating frequency of the system is found as follows:

$$P = sp(f_{nl} - f_{sys})$$

$$1000 \text{ kW} = \frac{1 \text{ MW}}{\text{Hz}} (61.0 \text{ Hz} - f_{sys}) \quad \rightarrow \quad f_{sys} = 60 \text{ Hz}$$




Solution:

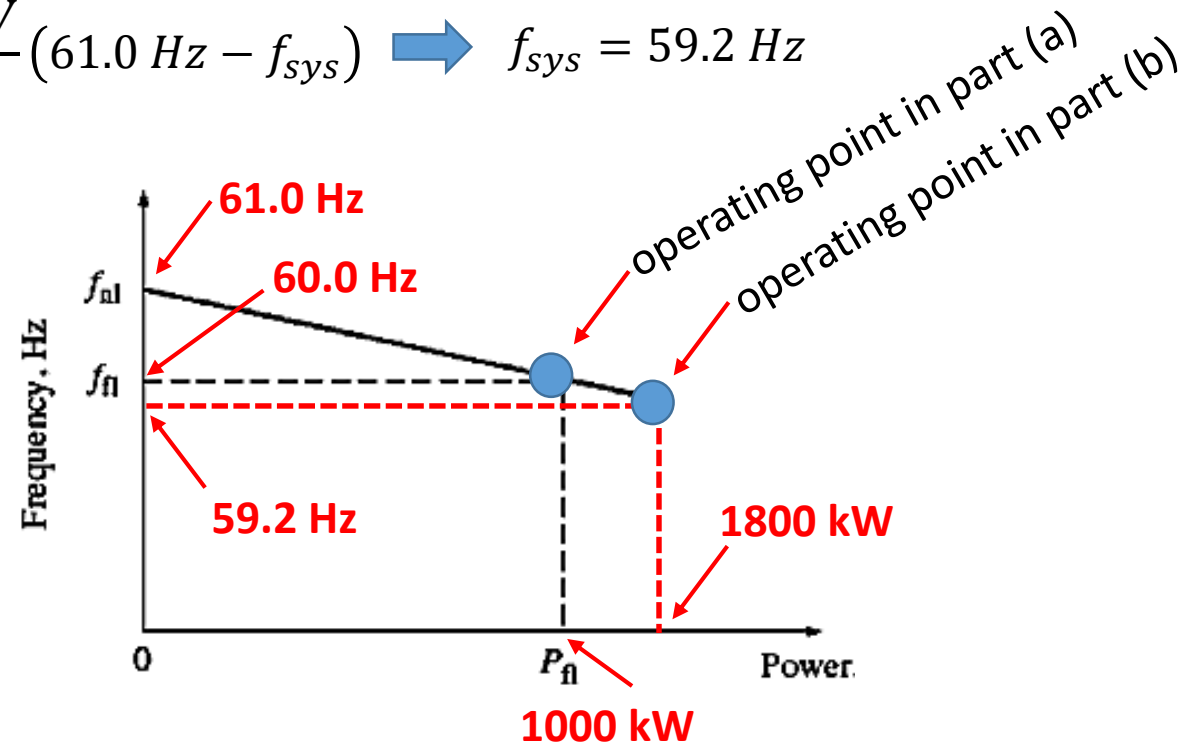(b) After **Load 2** is connected, the operating frequency of the system is found as follows:

$$P = sp(f_{nl} - f_{sys})$$

$$(1000 \text{ kW} + 800 \text{ kW}) = \frac{1 \text{ MW}}{\text{Hz}} (61.0 \text{ Hz} - f_{sys}) \Rightarrow f_{sys} = 59.2 \text{ Hz}$$



As seen, **adding the load decreases the frequency of the system from 60 Hz to 59.2 Hz**

Solution:

(c) After **Load 2** is connected, how can we increase system frequency from **59.2 Hz** to **60.0 Hz** ?

We should **increase the governor no-load set point from 60.0 Hz to 61.8 Hz.**


Let's check it:

$$P = sp(f_{nl} - f_{sys})$$

$$1800 \text{ kW} = \frac{1 \text{ MW}}{\text{Hz}} (61.8 \text{ Hz} - f_{sys})$$

$$(61.8 \text{ Hz} - f_{sys}) = 1.8 \text{ Hz}$$

$$f_{sys} = 60.0 \text{ Hz}$$

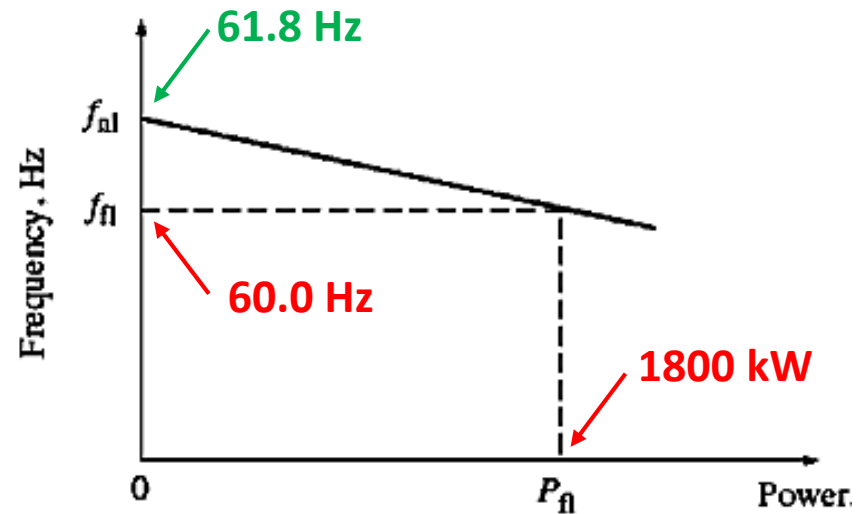


Operation of synchronous generators in parallel with infinite bus

- When a synchronous generator is connected to a huge power system, the power system's capacity is too large so that a connection of a generator does not effect the **voltage** and the **frequency** of the power system.
- An example of this situation is that Turkey's installed power \approx **89000 MW** (@ Jan2019). So if a **100 MW** generator is connected to the system, it can not change the voltage and the frequency of the overall country.

Definition of infinite bus


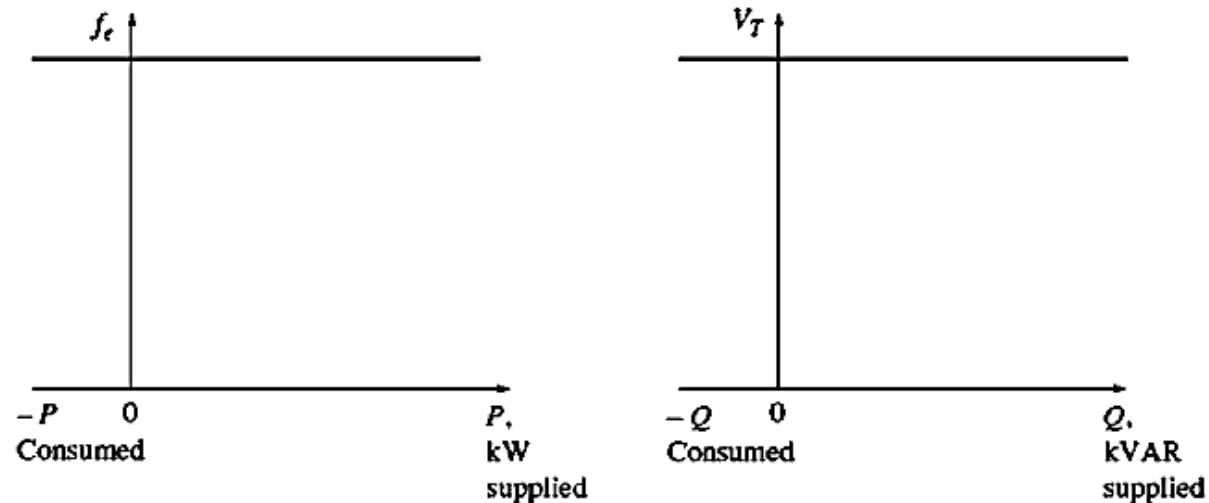
- An **infinite bus** is a power system so large that its **voltage** and **frequency** do not vary regardless of how much **real** and **reactive power** is drawn from or supplied to it.
- The **P - f** and **Q - V** characteristics of an infinite bus are shown below.



Infinite bus

- When a **generator** is connected in parallel with **another generator** or a **large system**, the **frequency** and **terminal voltage** of all the machines must be **same**.
- The **house diagram** is the combination of the **real power versus frequency** characteristics of the **generator** and the **infinite bus**.
- The real **power-frequency characteristics** of the generator and the infinite bus are plotted **back-to-back** with a **common vertical axis**.


$$P_{load} = P_{inf bus} + P_G$$

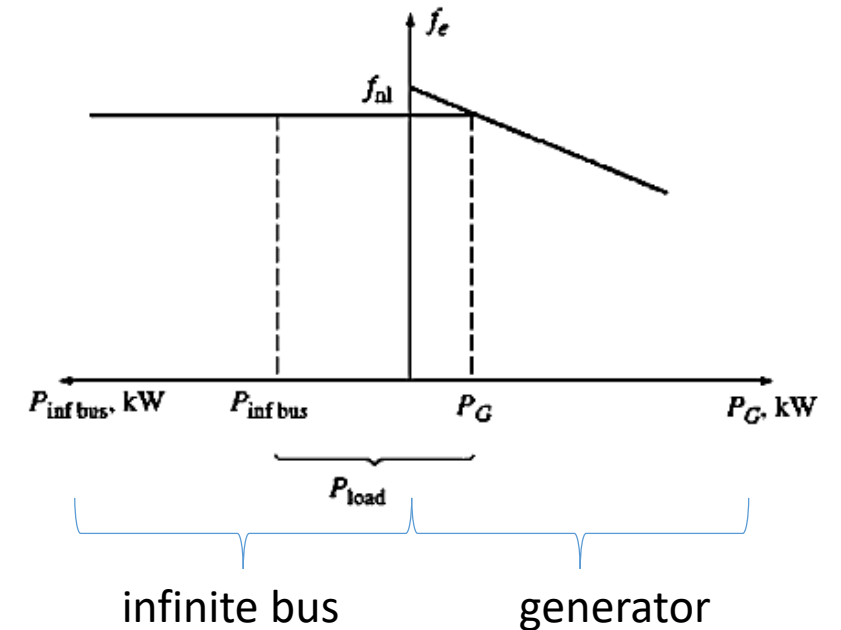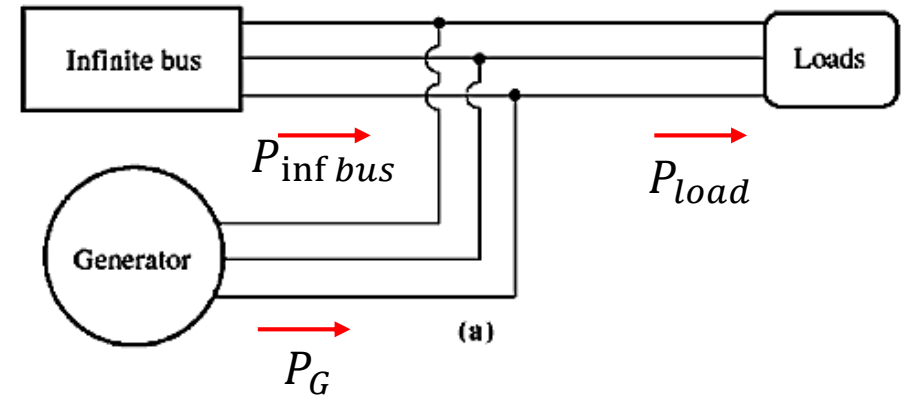

House diagram


Infinite bus

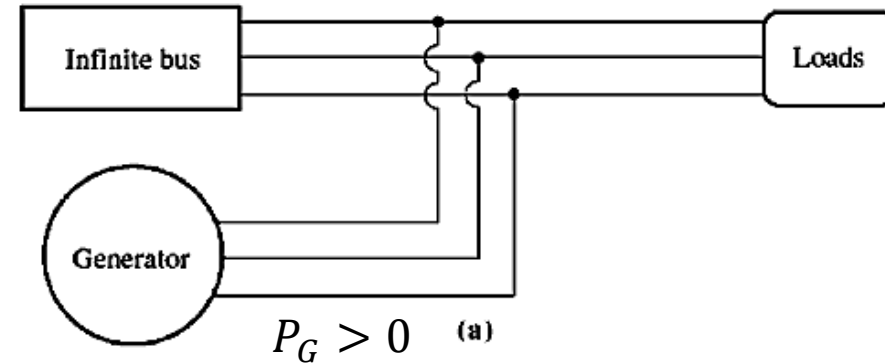- **No-load frequency** of the generator should be **slightly greater** than the **frequency of the infinite bus**. If this is so, the **real power** drawn by the generator becomes **positive** and the synchronous machine is operating like a **generator, supplying real power**



$$f_{nl} > f_{inf bus} \quad \rightarrow \quad P_G > 0$$

$$f_{inf bus} = 50 \text{ Hz}$$

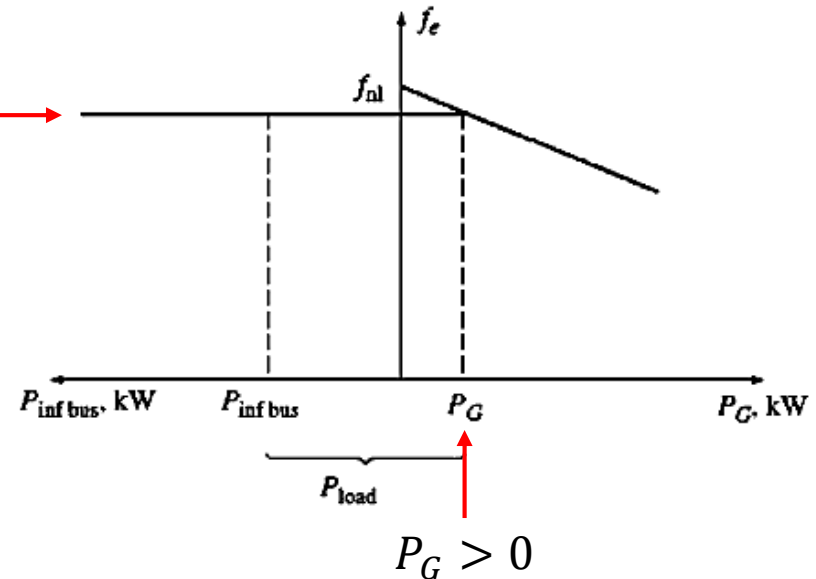


Infinite bus

- If **no-load frequency** of the generator is **smaller** than the **frequency of the infinite bus**, the **real power** drawn by the generator becomes **negative** and the synchronous machine is operating like a **motor, consuming real power**

$$f_{nl} < f_{inf bus} \quad \rightarrow \quad P_G < 0$$

$$f_{inf bus} = 50 \text{ Hz}$$

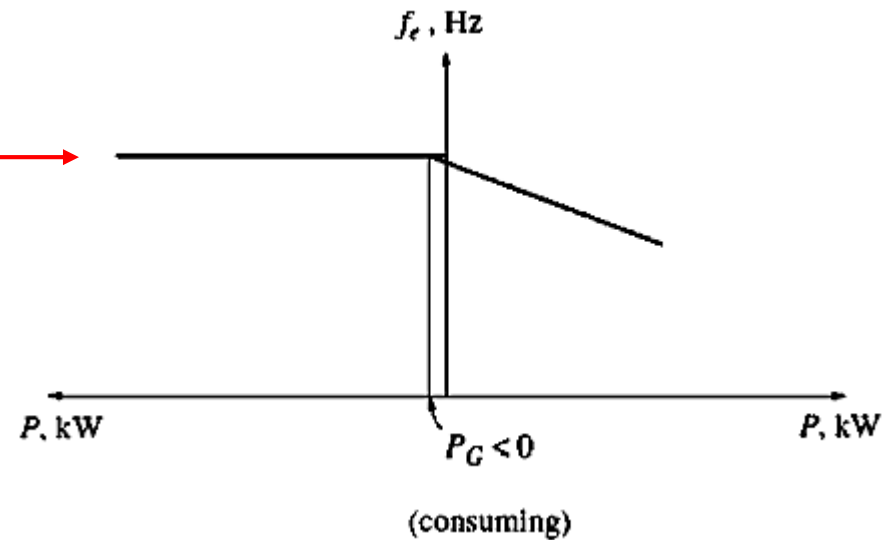

This situation is not desired !

Infinite bus

- Assume that the generator has been connected to infinite bus and supplying real power of P_{G1} , what happens when **its governor set-point is increased**?


1) The **no-load frequency** of the generator **shifts upward**.

$$f_{nl2} > f_{nl1}$$

2) The **real power** supplied by the generator **increases**.

$$P_{G2} > P_{G1}$$

$$f_{inf\ bus} = 50\ Hz$$

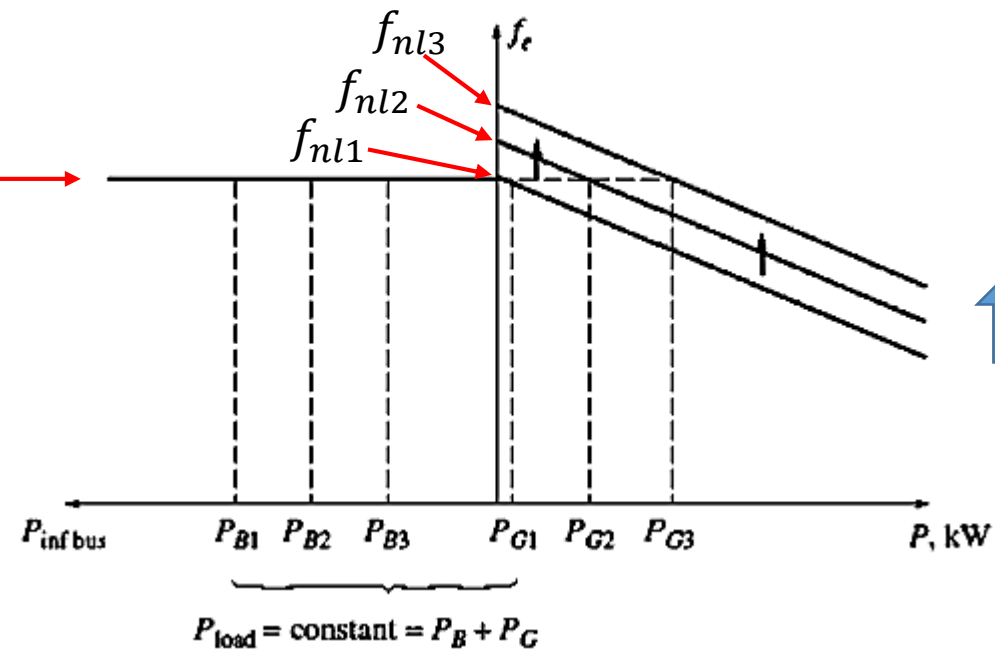

↑ governor set point is increased

- If we further increase the governor set-point:

$$f_{nl3} > f_{nl2}$$


$$P_{G3} > P_{G2}$$

Infinite bus

- Now, what happens to the **phasor diagram** of the generator if its **governor set-point is increased**?
- We know that (*from previous slide*) the **real power** supplied by the generator **increases**.

$$P_{out} = 3V_{\phi} \frac{E_A \sin\delta}{X_S}$$

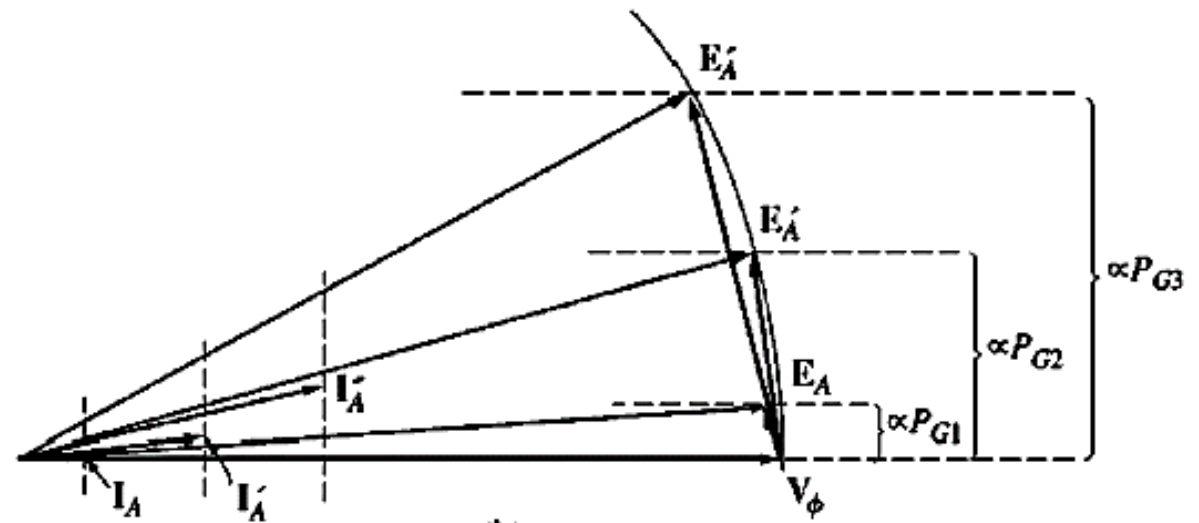constant (above E_A)
 constant (below V_{ϕ})
 constant (right of X_S)
 $\sin\delta$ is circled in red.



- According to this equation, **$\sin\delta$ or torque angle “ δ ” must increase**

$$P_{G3} > P_{G2} > P_{G1}$$

$$\delta_3 > \delta_2 > \delta_1$$

Infinite bus

- What happens now, if the output of the generator is **further increased** so that it **exceeds** the power consumed by the load?

$$P_G > P_{load}$$


- If this occurs, the **extra power** generated by the generator **flows back into the infinite bus**.
- For example;

$$P_{load} = 1000 \text{ kW}$$

$$P_G = 1300 \text{ kW}$$

$$P_{inf bus} = -300 \text{ kW} \text{ (generated)}$$

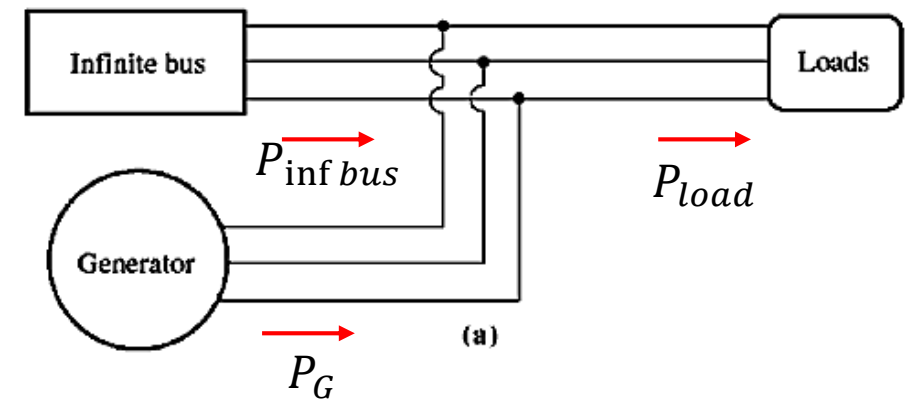- Let's remember the infinite bus, by definition, the infinite can **supply** or **consume any amount of power** without **a change in frequency**, so the **extra power is consumed**.



$$P_{load} = P_{inf bus} + P_G$$

Infinite bus

- So far we have seen that what happens to a synchronous generator connected to infinite bus when the **governor set-point is increased?**
- Now, the next question will be what happens to a synchronous generator connected to infinite bus if **its field current is increased? (governor set-point is unchanged)**


must be constant

$$P_{out} = 3 \cdot V_{\phi} \cdot I_A \cdot \cos\theta$$

constant constant

$$Q_{out} = 3 \cdot V_{\phi} \cdot I_A \cdot \sin\theta$$

constant **increases**

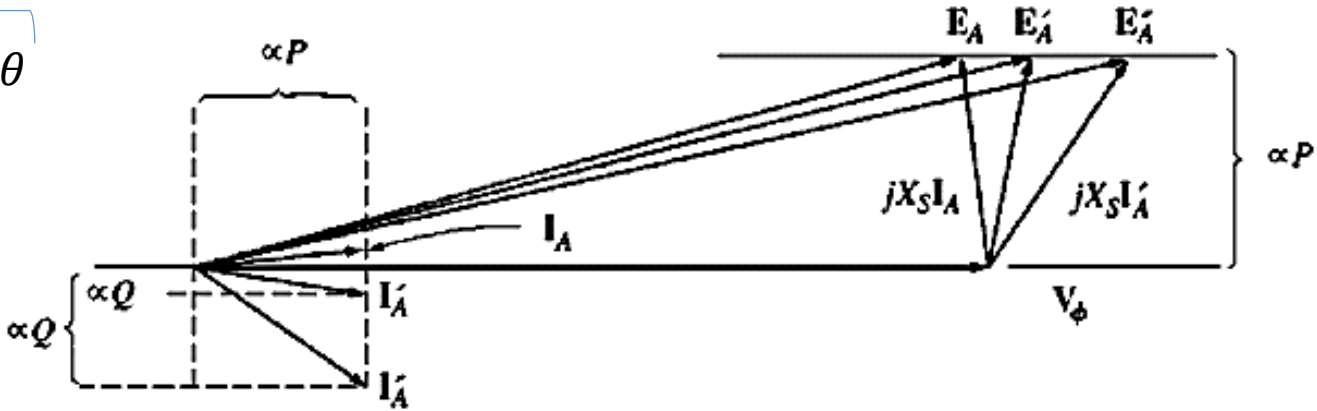

must be constant

$$P_{out} = 3V_{\phi} \frac{E_A \sin\delta}{X_S} \rightarrow \text{constant}$$

constant constant

Infinite bus

- In summary, what happens to a synchronous generator connected to infinite bus if **its field current is increased?** (**governor set-point is unchanged**)
 - The **real power output** of the generator **does not change** (*since governor set-point is unchanged*)
 - Since **real power output** of the generator is **constant** $E_A \sin \delta$ must be **constant**
 - Since **real power output** of the generator is **constant** $I_A \cos \theta$ must be **constant**
 - The **magnitude** (rms) of the armature current $|I_A|$ **increases**
 - Since $|I_A|$ **increases** and $I_A \cos \theta$ is **constant**, then $I_A \sin \theta$ must **increase**
 - Since $I_A \sin \theta$ **increases**, Q_{out} **increases** as well.

So, **as a result:**

- **increasing the field current in a synchronous generator operating in parallel with an infinite bus increases the reactive power output of the generator**

Infinite bus

To summarize;


- **When a single generator is operating alone:**
 - 1) The real and reactive powers supplied by the generator are fixed, and constrained to be equal to the power demanded by the load
 - 2) The frequency and terminal voltage are varied by the governor set points and the field current, respectively.
- **When a generator is operating in parallel with an infinite bus:**
 - 1) The frequency and terminal voltage of the generator are controlled by the system to which it is connected.
 - 2) The governor set points of the generator control the real power supplied by the generator to the system.
 - 3) The field current in the generator controls the reactive power supplied by the generator to the system.

Parallel operation of generators with the same size


- If two generators are connected in parallel as shown in the figure, the real and reactive power of the load is shared between the generators.

$$P_{Load} = P_{G1} + P_{G2}$$

$$Q_{Load} = Q_{G1} + Q_{G2}$$

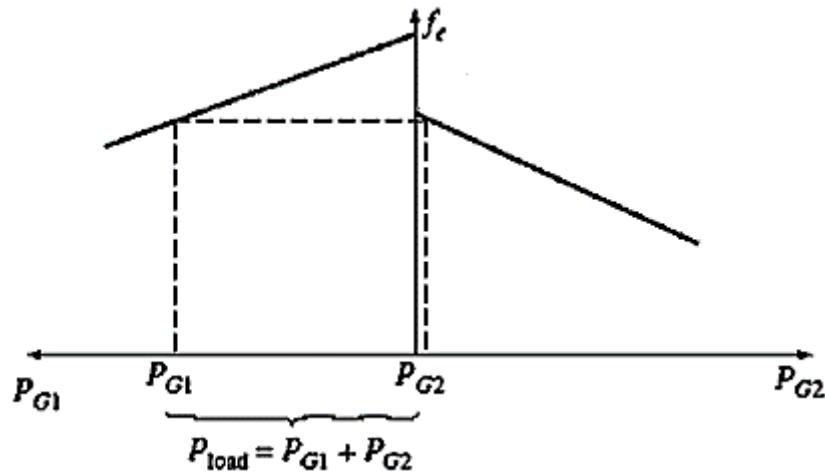


Two house diagrams shown together

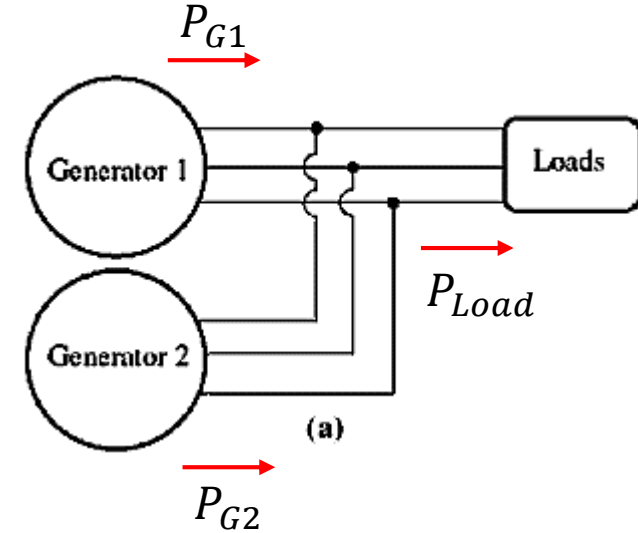

Parallel operation of generators with the same size

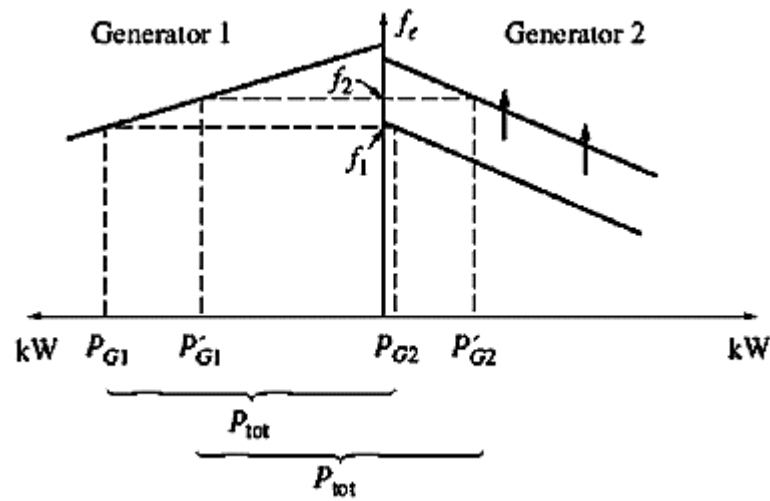- What happens if the **governor set point of Gen-2 is increased**?



- 1) Increases the **real power** supplied by **Gen-2**, while reducing the **real power** supplied by **Gen-1**.


$$P_{Load} = P_{G1} + P_{G2}$$

- 2) Increases overall system frequency.

$$f_2 > f_1$$

Parallel operation of generators with the same size

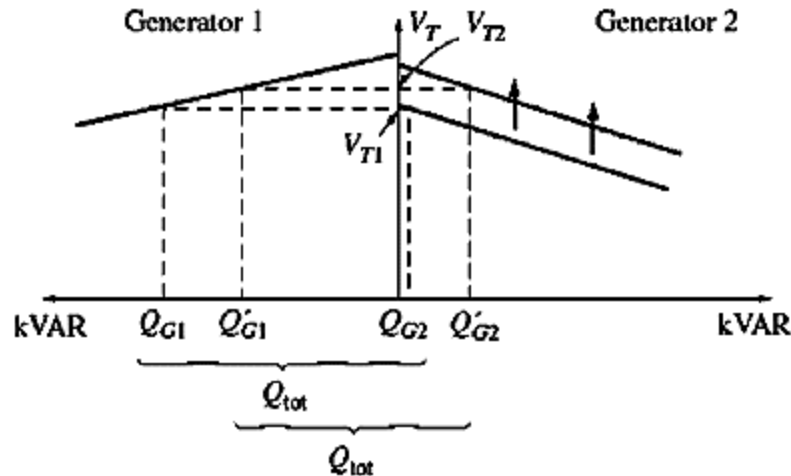- What happens if the **field current of Gen-2 is increased?**



- 1) Increases the **reactive power** supplied by **Gen-2**, while reducing the **reactive power** supplied by **Gen-1**.



$$\overrightarrow{Q_{Load}} = Q_{G1} + Q_{G2}$$

- 2) Increases system terminal voltage.

$$V_{T2} > V_{T1}$$

Example: Parallel operation of generators with the same size

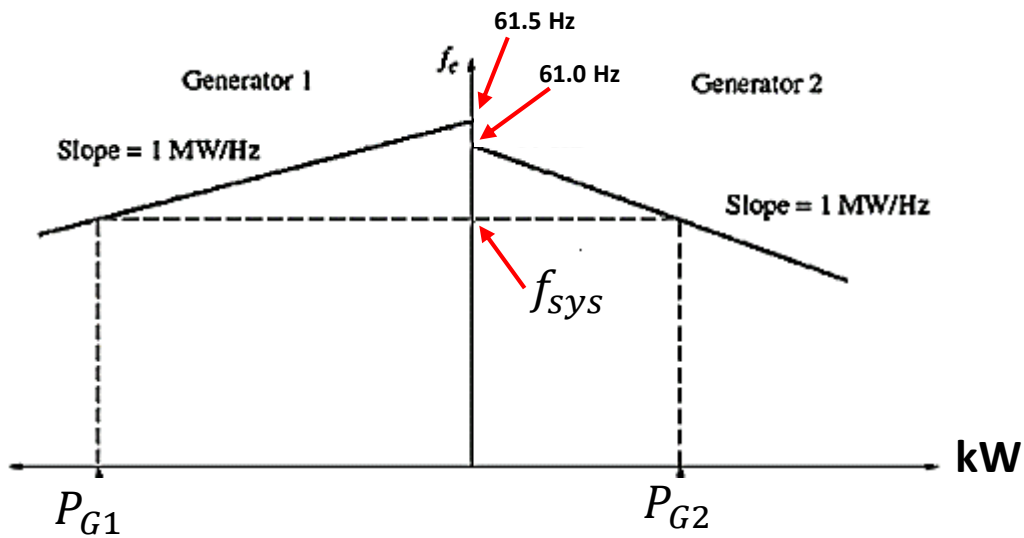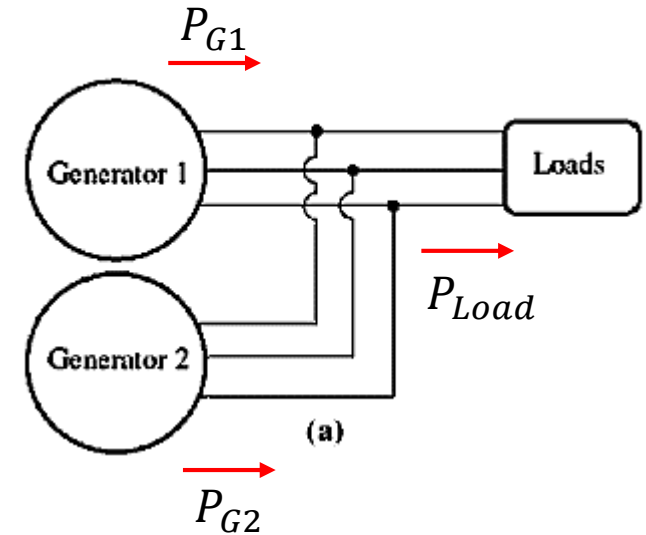Example: The figure shows two generators supplying a load. Generator 1 has a no-load frequency of **61.5 Hz** and a slope **sp1** of **1MW/Hz**. Generator 2 has a no-load frequency of **61.0 Hz** and a slope **sp2** of **1MW/Hz**. The two generators are supplying a load of **2.5 MW** at 0.8 PF lagging. The resulting system power-frequency or house diagram is shown below.



$$P_{Load} = P_{G1} + P_{G2} = 2.5 \text{ MW}$$



$$P_{G1} = sp1(f_{nl1} - f_{sys})$$

$$P_{G2} = sp2(f_{nl2} - f_{sys})$$

Required equations to find f_{sys} , P_{G1} , P_{G2}

Example: Parallel operation of generators with the same size

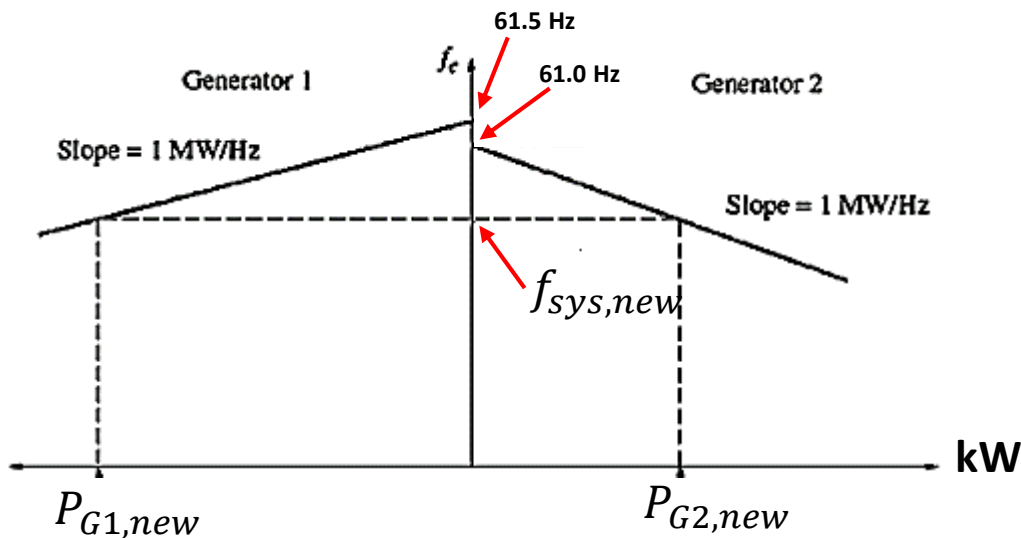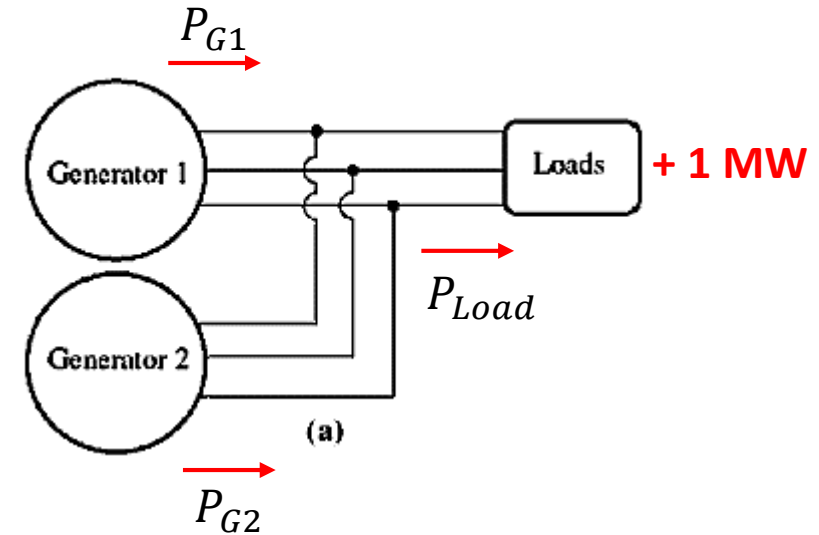Example: (continue): Suppose an **additional 1-MW load** is attached to this power system. What would the new system frequency be, and how much power would G1 and G2 supply now?



$$P_{Load} = P_{G1,new} + P_{G2,new} = 3.5 \text{ MW}$$

$$P_{G1,new} = sp1(f_{nl1} - f_{sys,new})$$

$$P_{G2,new} = sp2(f_{nl2} - f_{sys,new})$$

Required equations to find $f_{sys,new}$

$$P_{G1,new}$$

$$P_{G2,new}$$

Example: Parallel operation of generators with the same size

Example: (continue): With the system in the configuration described in previous condition, what will the system frequency and generator powers be if the governor set point on G2 is increased by **0.5 Hz**?

$$f_{nl2,new} = 61.5 \text{ Hz}$$

$$P_{Load} = P_{G1,new} + P_{G2,new} = 3.5 \text{ MW}$$

$$P_{G1,new} = sp1(f_{nl1} - f_{sys,new})$$


$$P_{G2,new} = sp2(f_{nl2,new} - f_{sys,new})$$

Required equations

to find $f_{sys,new}$


$P_{G1,new}$

$P_{G2,new}$

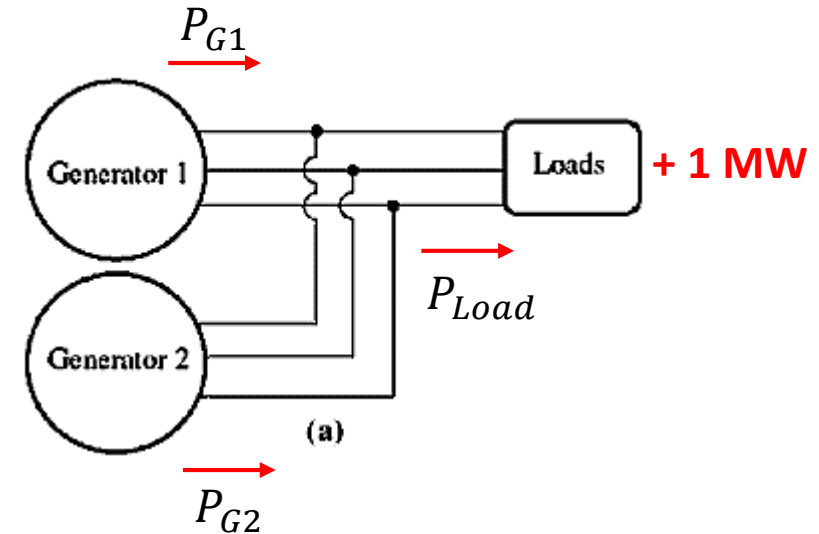

Parallel operation of generators with the same size

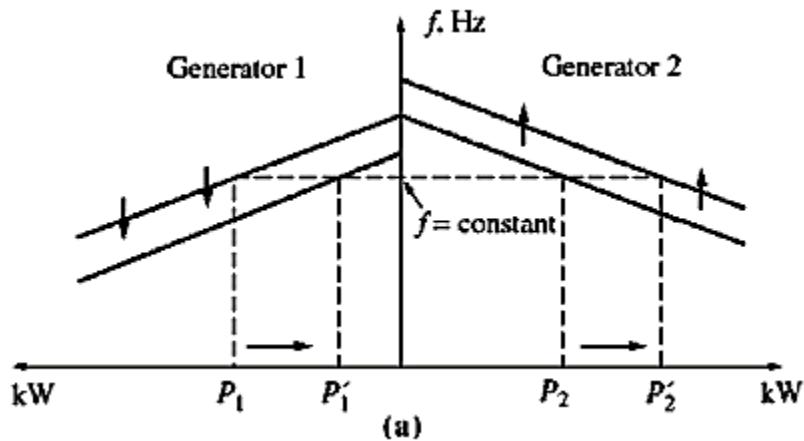- We see that if **governor set point** of one generator is **increased**, the system frequency increases.
- So how can we **adjust the power sharing** of each generator without changing system frequency?
- The solution is
- To **decrease** the **governor set point** of the other generator so as to **keep the system frequency constant**



$$P_{Load} = P_1 + P_2 = \text{constant}$$


$$P_{Load} = P_1' + P_2' = \text{constant}$$

$$P_2' > P_2$$

$$P_1' < P_1$$

Parallel operation of generators with the same size

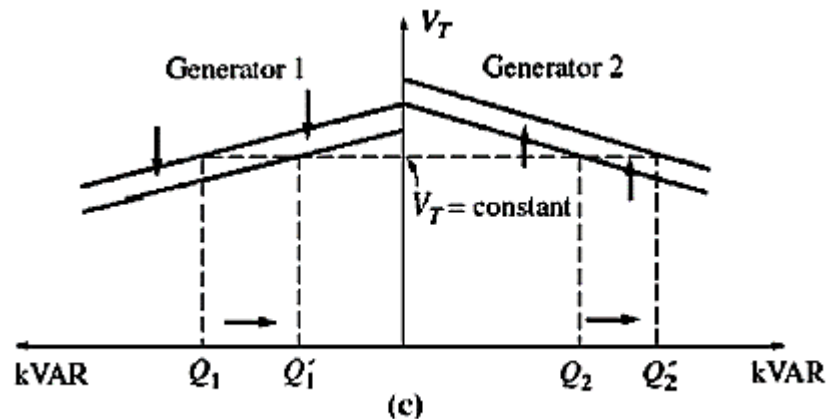- We see that if **field current** of one generator is **increased**, the system voltage increases.
- So how can we **adjust the reactive power sharing** of each generator without changing system voltage?
- The solution is
- To **decrease** the **field current** of the other generator so as to **keep the system voltage constant**



$$Q_{Load} = Q_1 + Q_2 = \text{constant}$$

$$Q_{Load} = Q_1' + Q_2' = \text{constant}$$

$$Q_2' > Q_2$$

$$Q_1' < Q_1$$

Parallel operation of generators with the same size

- The other two cases:
- To **adjust f_{sys} without changing the real power sharing of the generators, simultaneously increase or decrease both generators' governor set points.**
- To **adjust V_T without changing the reactive power sharing of the generators, simultaneously increase or decrease both generators' field currents**

Synchronous generator ratings

- There are certain basic limits to the speed and power that may be obtained from a synchronous generator.
- These limits are expressed as ratings on the machine.
- The purpose of the ratings is to **protect the generator** from **damage due to improper operation**.
- Each machine has a number of ratings listed on a nameplate attached to it (*see figure*).
- Typical ratings of a synchronous machine are **voltage**, **frequency**, **speed**, **apparent power (kilovoltamperes)**, **power factor**, **field current**, and **service factor**.

HYDROGEN COOLED GENERATOR			
TYPE	TFLQQ	FORM	KD
PHASES	3	POLES	2
POWER FACTOR	0.90	CAPACITY	133333 kVA
SPEED	3600 rpm	RATING	120000 kW
VOLTAGE	13800 V	FREQUENCY	60 Hz
EXCITING VOLTAGE	440 V	CURRENT	5578 A
CODE	ANSI C50.13-1977	FIELD CURRENT	1120 A
MFG. NO.	165931-1	INSULATION CLASS	F
		MFG. DATE	1989

Toshiba A. C. GENERATOR			
PHASE	3	TYPE	TAA
POLES	8	kVA	260
VOLTS	160	AMPERES	939
POWER FACTOR	0.9	RATING	CONT.
EXCITATION VOLTS	70	FORM	AS
ARMATURE TEMP. RISE	157 °F	RPM	3600
ARMATURE CONNECTION	Yx4	Hz	240
ARMATURE INSULATION CLASS	B	INLET COOLANT TEMP.	109 °F
STANDARD SPECIFICATION	ANSI C50.10-1977	FIELD AMPERES	21.6
SERIAL NO.	9024012	FIELD TEMP. RISE	148 °F
		FIELD INSULATION CLASS	B
		MANUFACTURED IN	1990

TOSHIBA CORPORATION
TOKYO JAPAN

Frequency rating of synchronous generator

- The **rated frequency** of a synchronous generator **depends on the power system** to which it is connected.
- The commonly used power system frequencies today are **50 Hz** (*in Europe, Asia, etc.*), **60 Hz** (*in the USA, Canada*), and **400 Hz** (*in special purpose and control applications*).
- If the **operating frequency is known**, there is **only one possible rotational speed** for a given **number of poles**.

$$n_m = \frac{120f_e}{P}$$

- is it possible to operate a **60-Hz generator** at **50-Hz system**?

$$\left. \begin{array}{l} E_A = K\Phi\omega \\ \omega = 2\pi f \end{array} \right\} \begin{array}{l} \swarrow \\ E_A = K\Phi 2\pi f \\ \swarrow \end{array}$$

- The answer is **Yes**. But we have to **derate** (*reduce*) the **voltage rating of the generator**.
- Otherwise in order to get the same voltage, we need **more flux**. That can cause **saturation** of the machine.

Apparent power and power-factor ratings

- The **maximum allowable armature current** $|I_{A(max)}|$ is determined by the **maximum current carrying capacity** of the **conductors in stator**. So;

$$0 \leq |I_A| \leq |I_{A(max)}|$$


- This current limit defines **apparent power rating** of the generator. That is;

$$S_{rated} = 3V_{\phi,rated}I_{A(max)}$$

- Similarly, the **maximum allowable field current** $|I_{F(max)}|$ is determined by **maximum current carrying capacity** of the **conductors in rotor**. So;


$$0 \leq |I_F| \leq |I_{F(max)}|$$

Apparent power and power-factor ratings

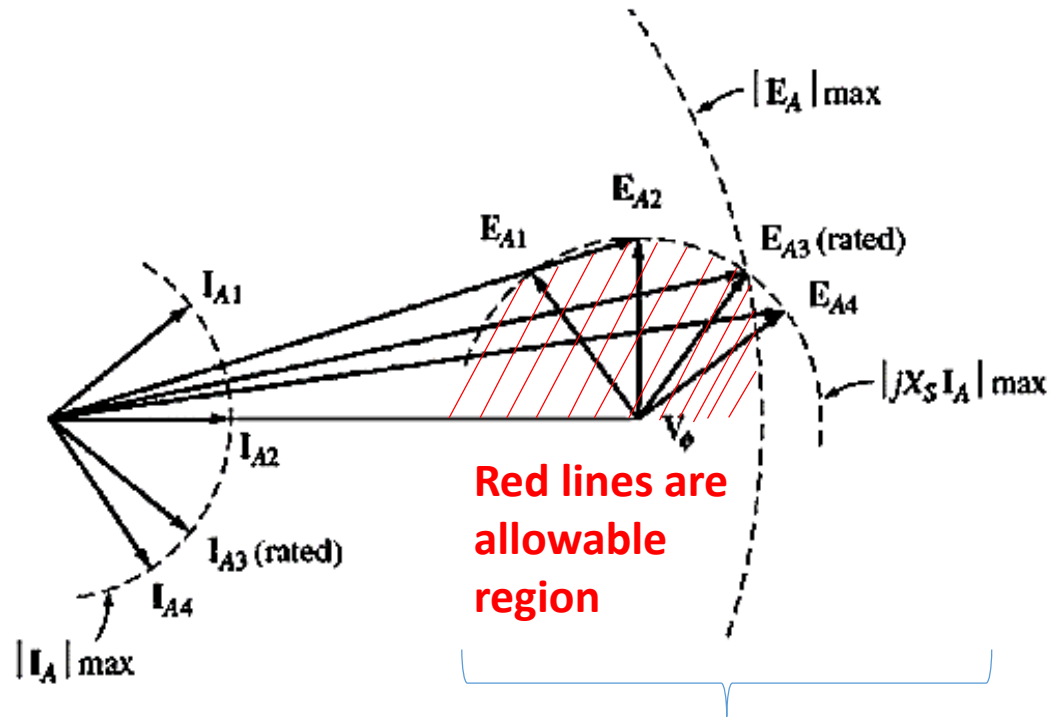

The intersection of small and big circles defines the phase angle that armature current can have

Apparent power and power-factor ratings

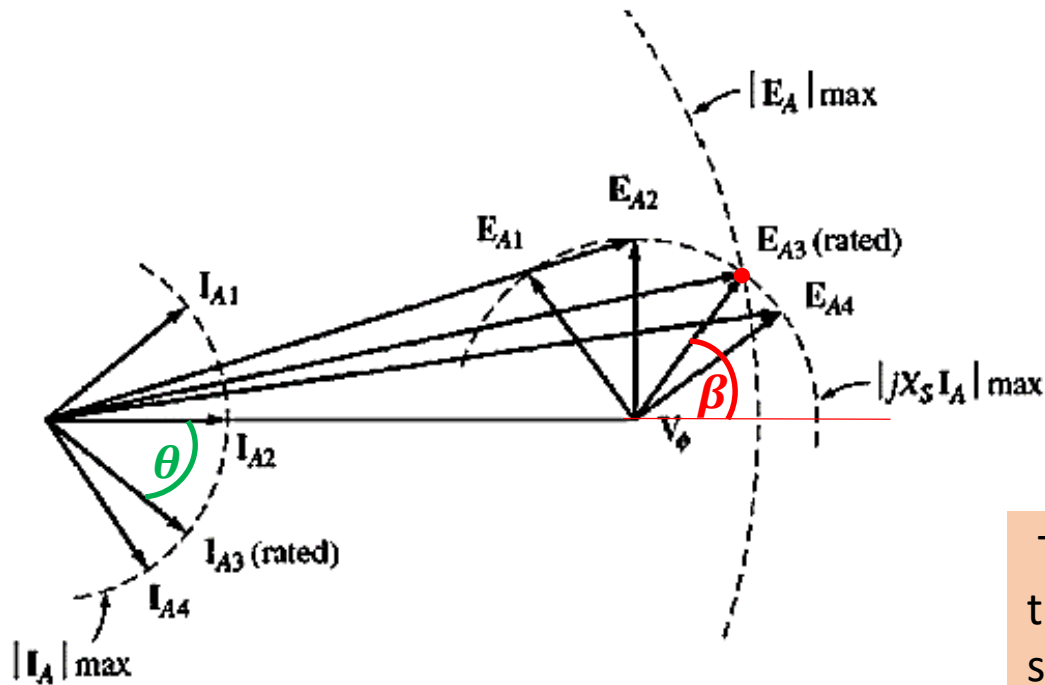

The angle β can not be decreased further (minimum limit) without reducing $|I_{A(max)}|$

- Since;

$$\beta = 90^\circ - \theta$$

$$\theta_{max} = 90^\circ - \beta_{min}$$



The possible maximum value of the power factor angle of the synchronous generator

$$\Rightarrow PF_{min} = \cos(\theta_{max})$$






The possible minimum value of the **(lagging)** power factor of the synchronous generator

Synchronous generator capability curve

- **Capability curve** of a synchronous generator is a plot of the **complex power ($S=P+jQ$)** of the generator.
- **Capability curve** is derived from the **phasor diagram** of the generator.
- We assume that;
 - Phase voltage of the generator (V_ϕ) is **constant** (generator is connected to infinite bus)
 - Armature resistance R_A is **ignored**
 - Power factor of the load is **lagging**


Synchronous generator capability curve

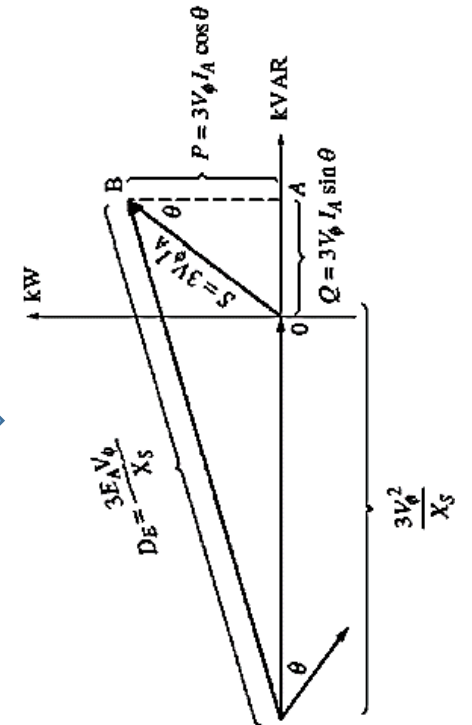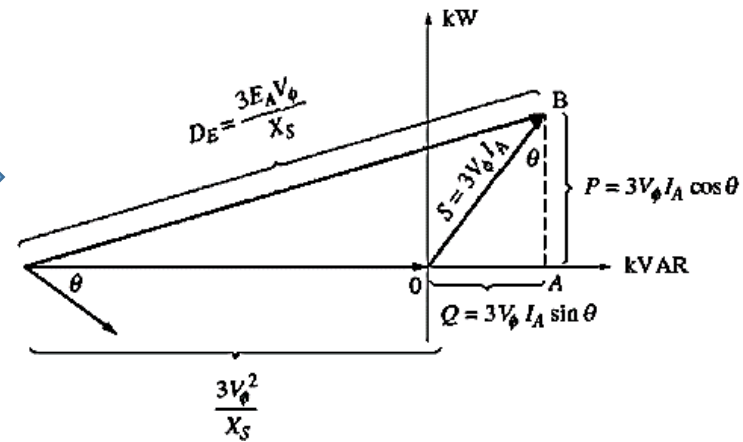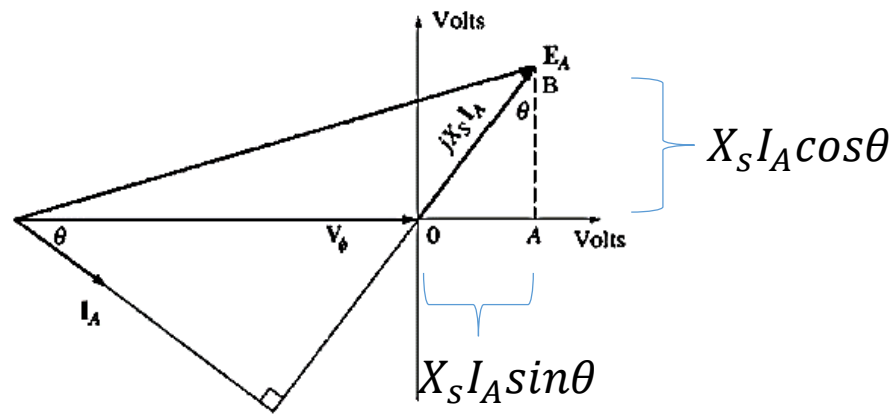


$$X_S I_A \cos \theta \times \frac{3V_\phi}{X_S} \Rightarrow P = 3V_\phi I_A \cos \theta$$

$$X_S I_A \sin \theta \times \frac{3V_\phi}{X_S} \Rightarrow Q = 3V_\phi I_A \sin \theta$$

Synchronous generator capability curve

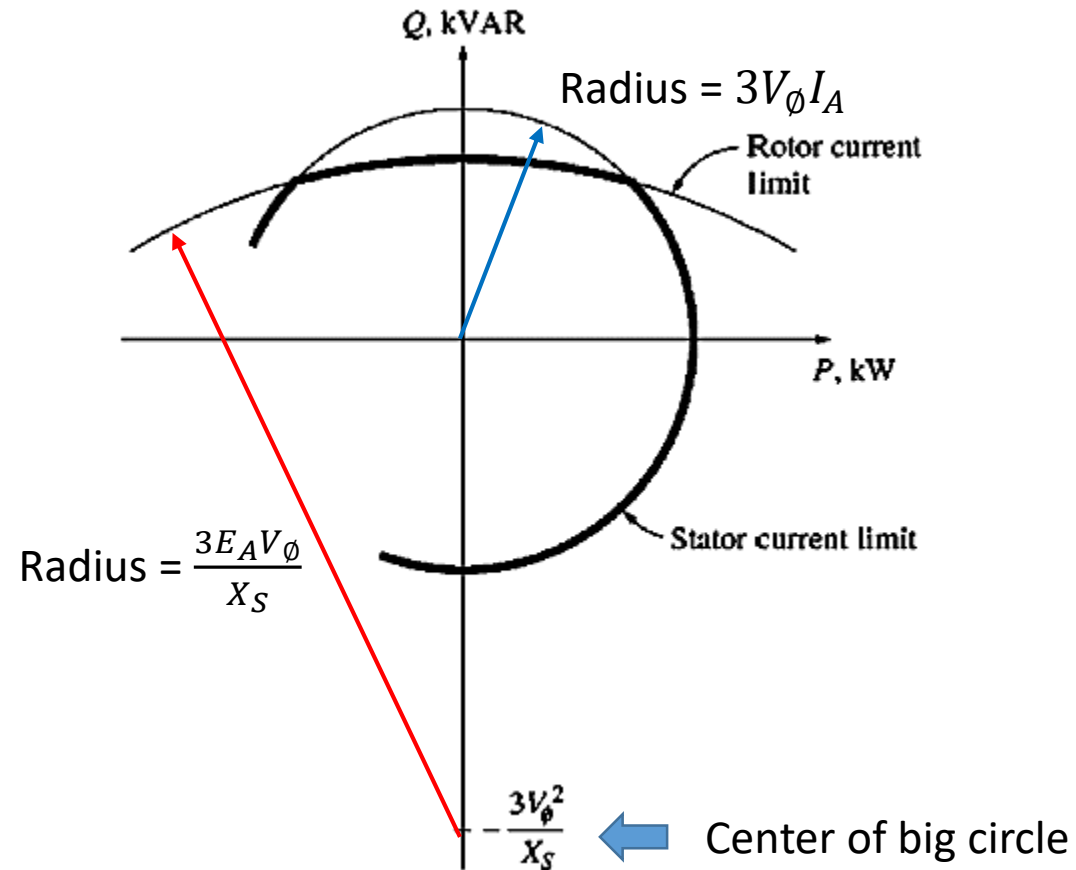

Synchronous generator capability curve

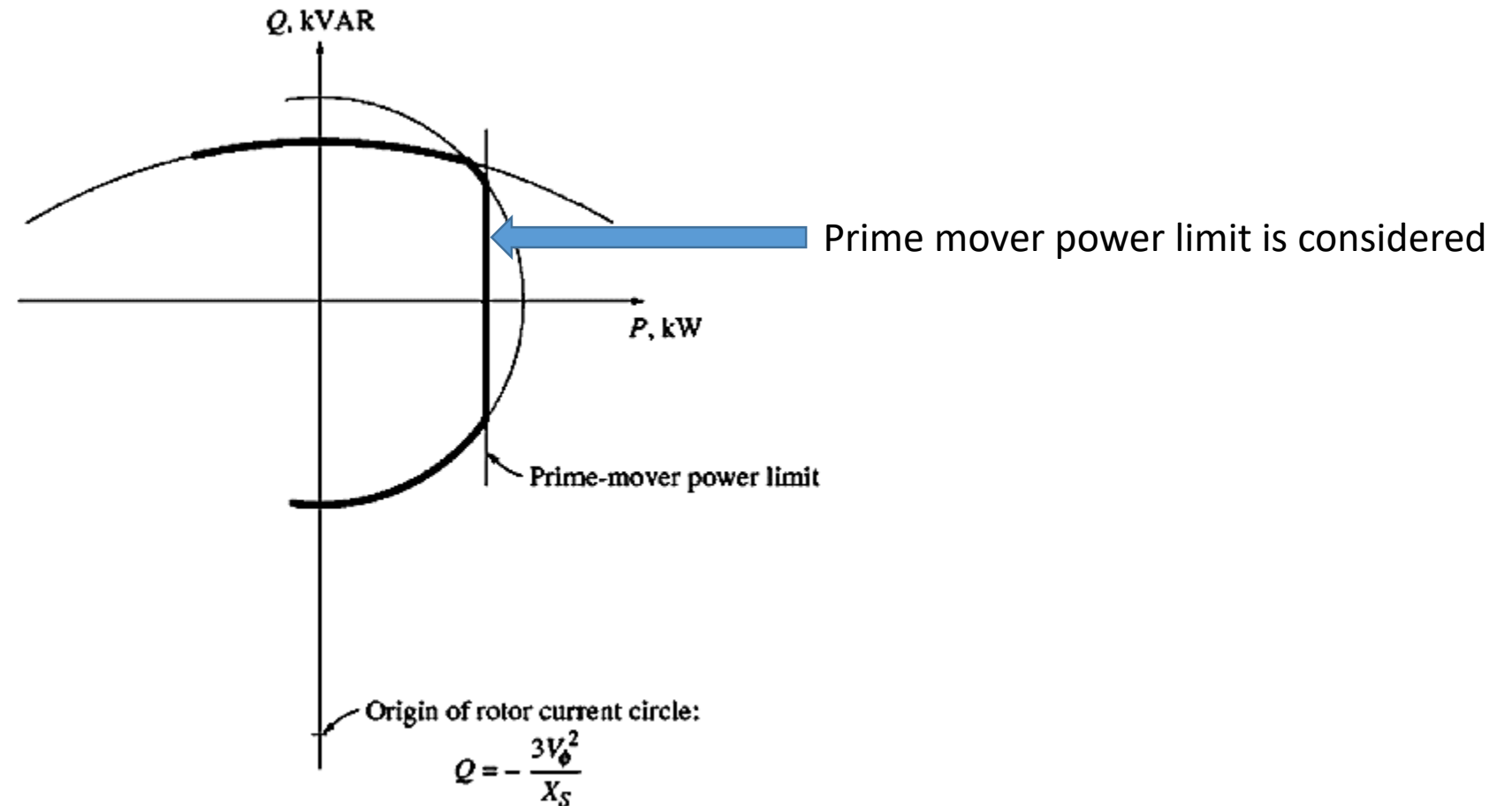


Example: Synch. generator capability curve

Example: A 480-V, 50-Hz, Y-connected, six-pole synchronous generator is rated at 50 kVA at 0.8 PF lagging. It has a synchronous reactance of 1.0 ohm per phase. Assume that this generator is connected to a steam turbine capable of supplying up to 45 kW. The friction and windage losses are 1.5 kW, and the core losses are 1.0 kW.

Answer the following questions:

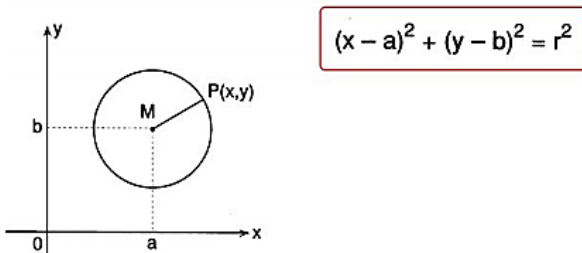- (a) Sketch the capability curve for this generator, including the prime-mover power limit.
- (b) Can this generator supply a line current of 56A at 0.7 PF lagging? Why or why not?
- (c) What is the maximum amount of reactive power that this generator can produce?
- (d) If the generator supplies 30 kW of real power, what is the maximum amount of reactive power that can be simultaneously supplied? (**Hint:** Use circle equation)



Example: Synch. generator capability curve

Solution a) The maximum armature current of the generator is found from:

$$S_{rated} = 3V_{\phi}I_{A(max)}$$


$$V_{\phi} = \frac{480}{\sqrt{3}} = 277 \text{ V}$$

$$I_{A(max)} = \frac{S_{rated}}{3V_{\phi}} = \frac{50kVA}{3(277V)} = 60 \text{ A}$$

The maximum size of E_A is given by

$$\begin{aligned} E_A &= V_{\phi} + jX_S I_A \\ &= 277 \angle 0^{\circ} \text{ V} + (j1.0 \Omega)(60 \angle -36.87^{\circ} \text{ A}) \\ &= 313 + j48 \text{ V} = 317 \angle 8.7^{\circ} \text{ V} \end{aligned}$$

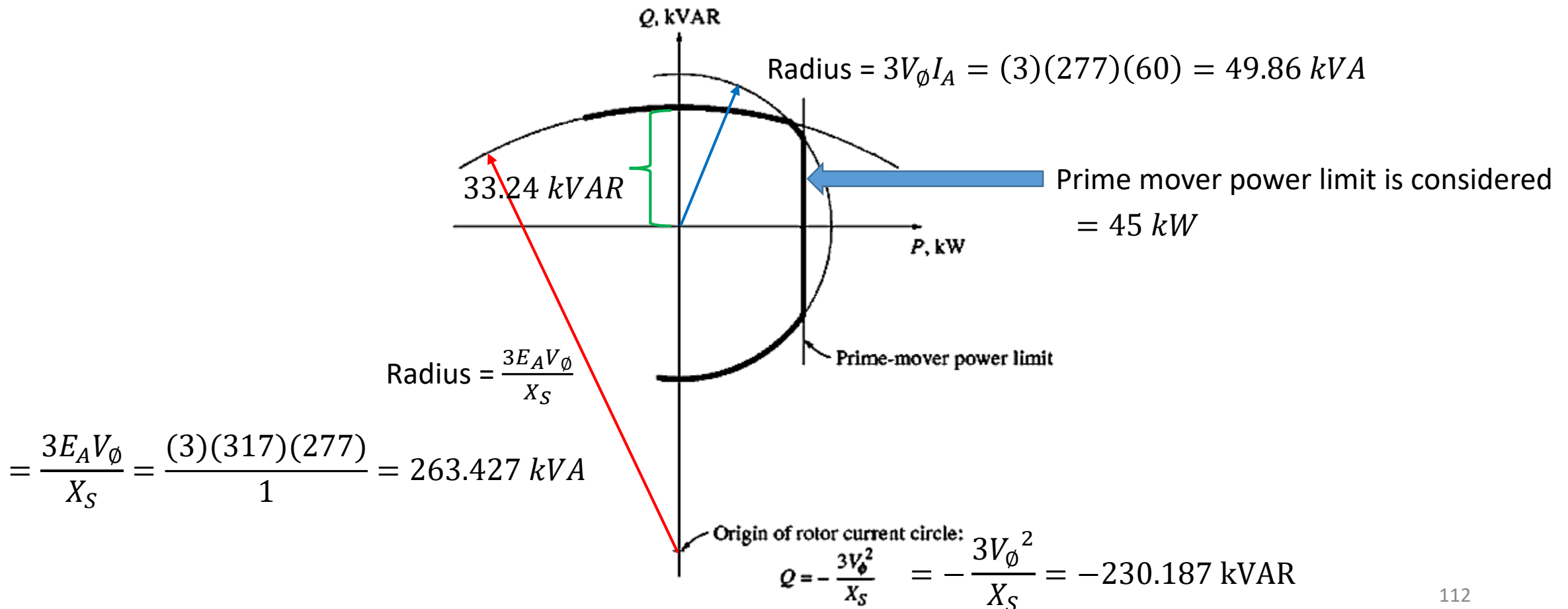Example: Synch. generator capability curve



Example: Synch. generator capability curve

Solution b):

A current of 56 A at 0.7 PF lagging produces a real power of


$$P = 3V_{\phi} I_A \cos \theta$$

$$= 3(277 \text{ V})(56 \text{ A})(0.7) = 32.6 \text{ kW}$$

and a reactive power of

$$Q = 3V_{\phi} I_A \sin \theta$$
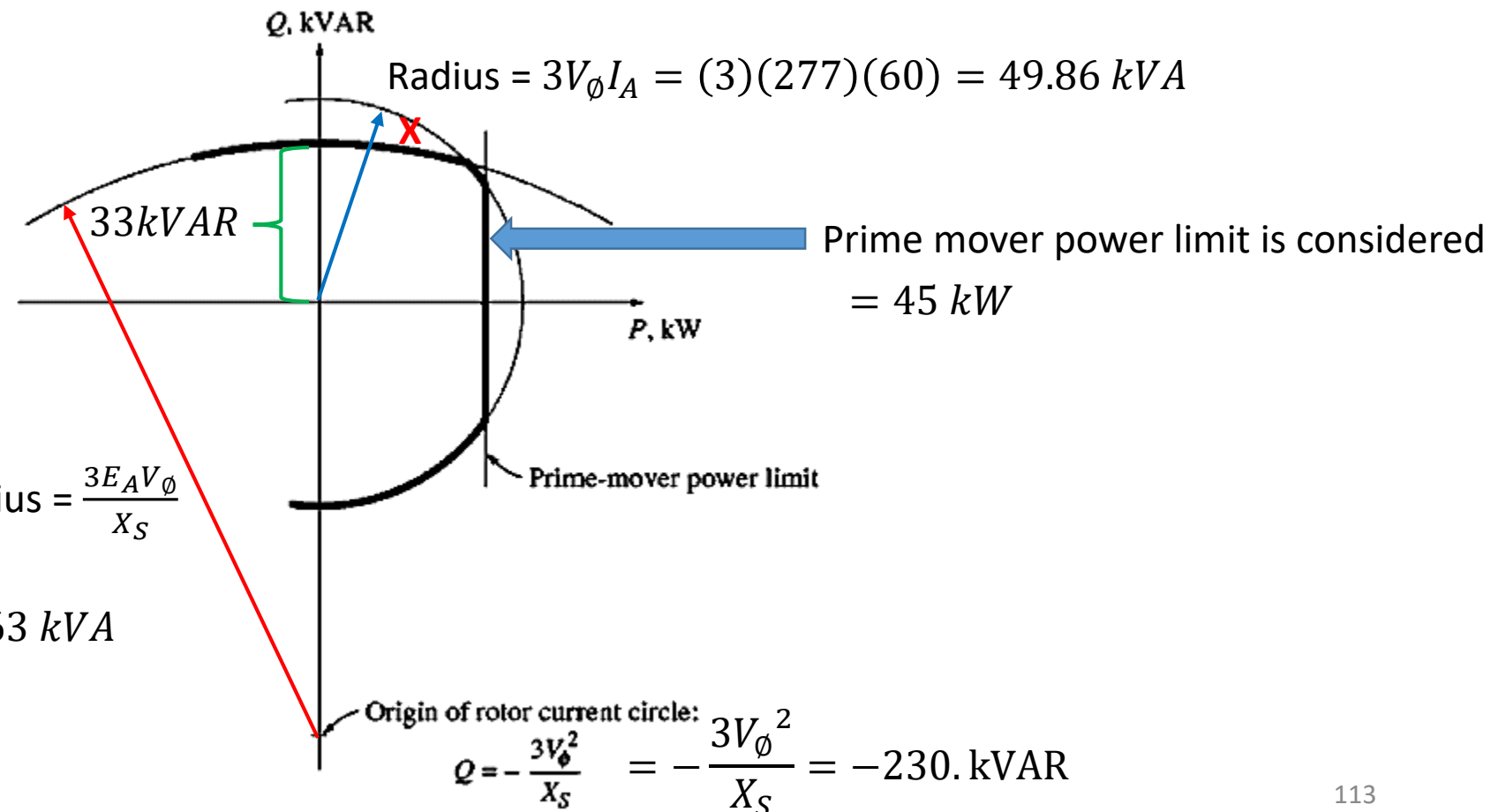
$$= 3(277 \text{ V})(56 \text{ A})(0.714) = 33.2 \text{ kVAR}$$



$$\text{Radius} = \frac{3E_A V_{\phi}}{X_S}$$


$$= \frac{3E_A V_{\phi}}{X_S} = \frac{(3)(317)(277)}{1} = 263 \text{ kVA}$$

Example: Synch. generator capability curve

Solution c):

When the real power supplied by the generator is zero, the reactive power that the generator can supply will be maximum. This point is right at the peak of the capability curve. The Q that the generator can supply there is
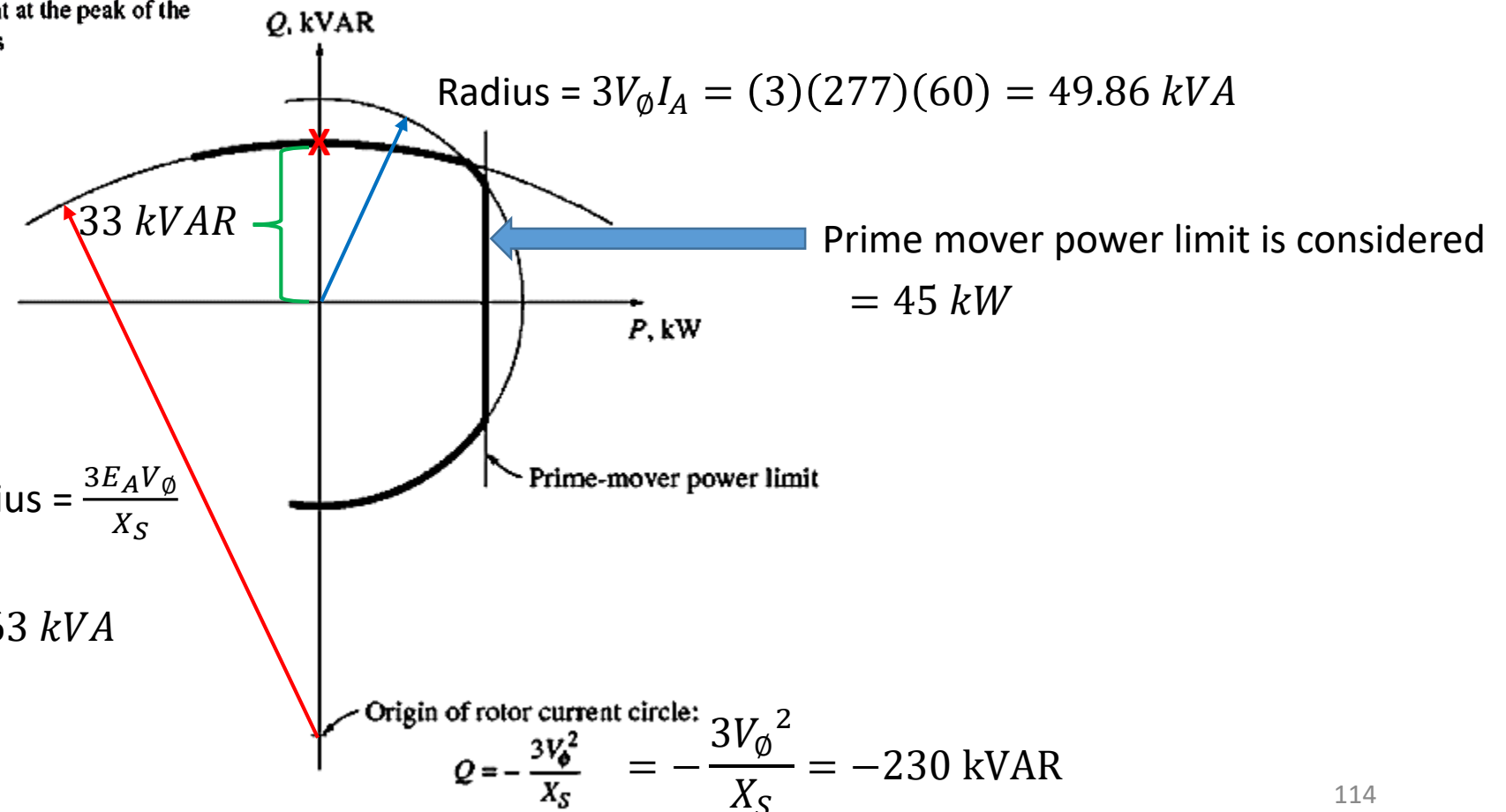
$$Q = 263 \text{ kVAR} - 230 \text{ kVAR} = 33 \text{ kVAR}$$



$$= \frac{3E_A V_{\phi}}{X_S} = \frac{(3)(317)(277)}{1} = 263 \text{ kVA}$$

END OF CHAPTER 2

SYNCHRONOUS GENERATORS