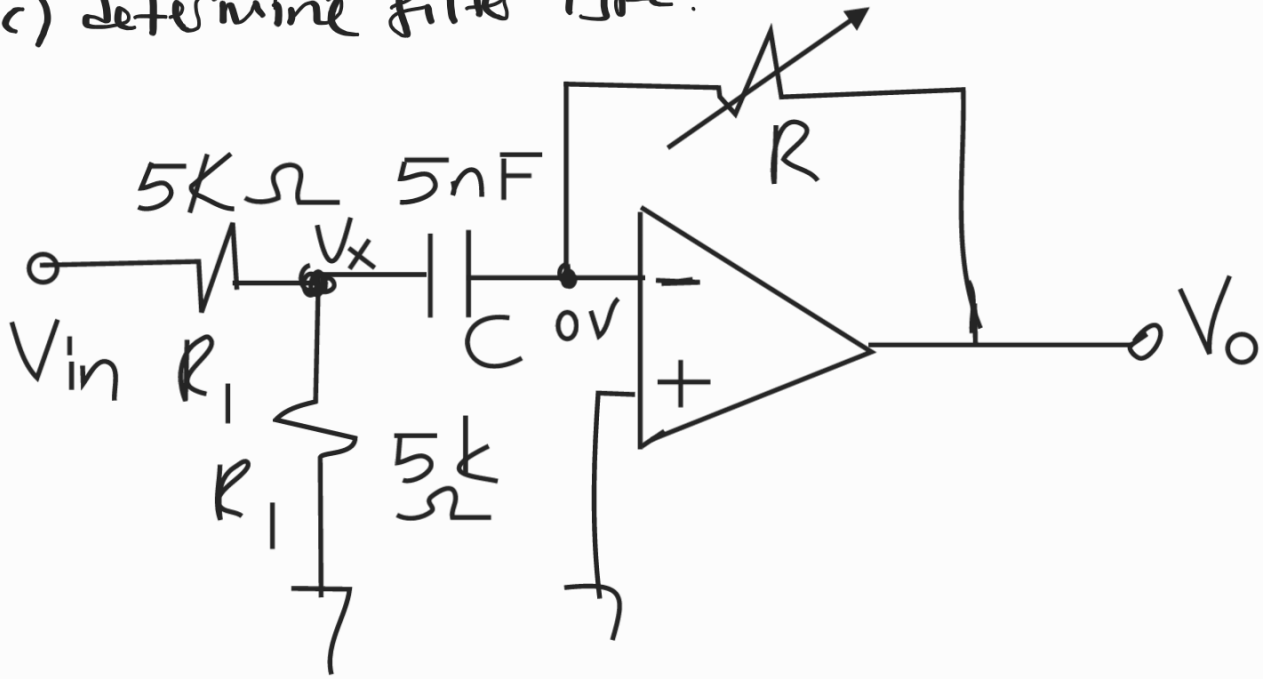


- a) obtain transfer function in s-domain
 or frequency domain b) compute ω_c
 c) determine filter type.



$$\frac{V_x}{\frac{1}{sC}} + \frac{V_x - V_{in}}{R_1} + \frac{V_x}{R_1} = 0 \quad ; \quad V_x = \frac{V_{in}}{(sCR_1 + 2)}$$

$$\frac{0 - V_x}{\frac{1}{sC}} + \frac{0 - V_o}{R} = 0$$

$$V_o = -sRCV_x = \frac{-sRCV_{in}}{(sCR_1 + 2)}$$

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{-sR/R_1}{s + \frac{2}{CR_1}}$$

$$H(s) = \frac{-sR}{(s + 8 \times 10^4) 5 \times 10^3}$$

$$H(j\omega) = \frac{-j\omega R 2 \times 10^{-4}}{j\omega + 8 \times 10^4}$$

$$|H(j\omega)| = \frac{\omega R 2 \times 10^{-4}}{\sqrt{\omega^2 + 64 \times 10^8}}$$

a) R controls only gain.

It doesn't have effect on ω_c .

$$b) |H(j\omega_c)| = \frac{\omega_c R 2 \times 10^{-4}}{\sqrt{\omega_c^2 + 64 \times 10^8}}$$

$$|H(j\infty)| = \frac{\omega_c R 2 \times 10^{-4}}{\sqrt{1 + \frac{64 \times 10^8}{\omega_c^2}}} \omega_c$$

$$|H|_{\max} = |H(j\infty)| = 2 \times 10^{-4} R$$

To find ω_c , establish the following eqn.

$$\frac{\omega_c R 2 \times 10^{-4}}{\sqrt{\omega_c^2 + 64 \times 10^8}} = \frac{2 \times 10^{-4} R}{\sqrt{2}}$$

$$\omega_c^2 + 64 \times 10^8 = 2 \omega_c^2$$

$$\omega_c = \sqrt{64 \times 10^8} = 8 \times 10^4 \text{ r/s}$$

$$c) |H(j0)| = 0$$

$$|H(j\omega)| = 2 \times 10^{-4} R$$

high pass filter

